

---

# EEDG/CE 6303: Testing and Testable Design

*Mehrdad Nourani*


**Dept. of ECE  
Univ. of Texas at Dallas**

---

## Session 03

# **Test Generation for Combinational Circuits**

# Fault Analysis System (Review)

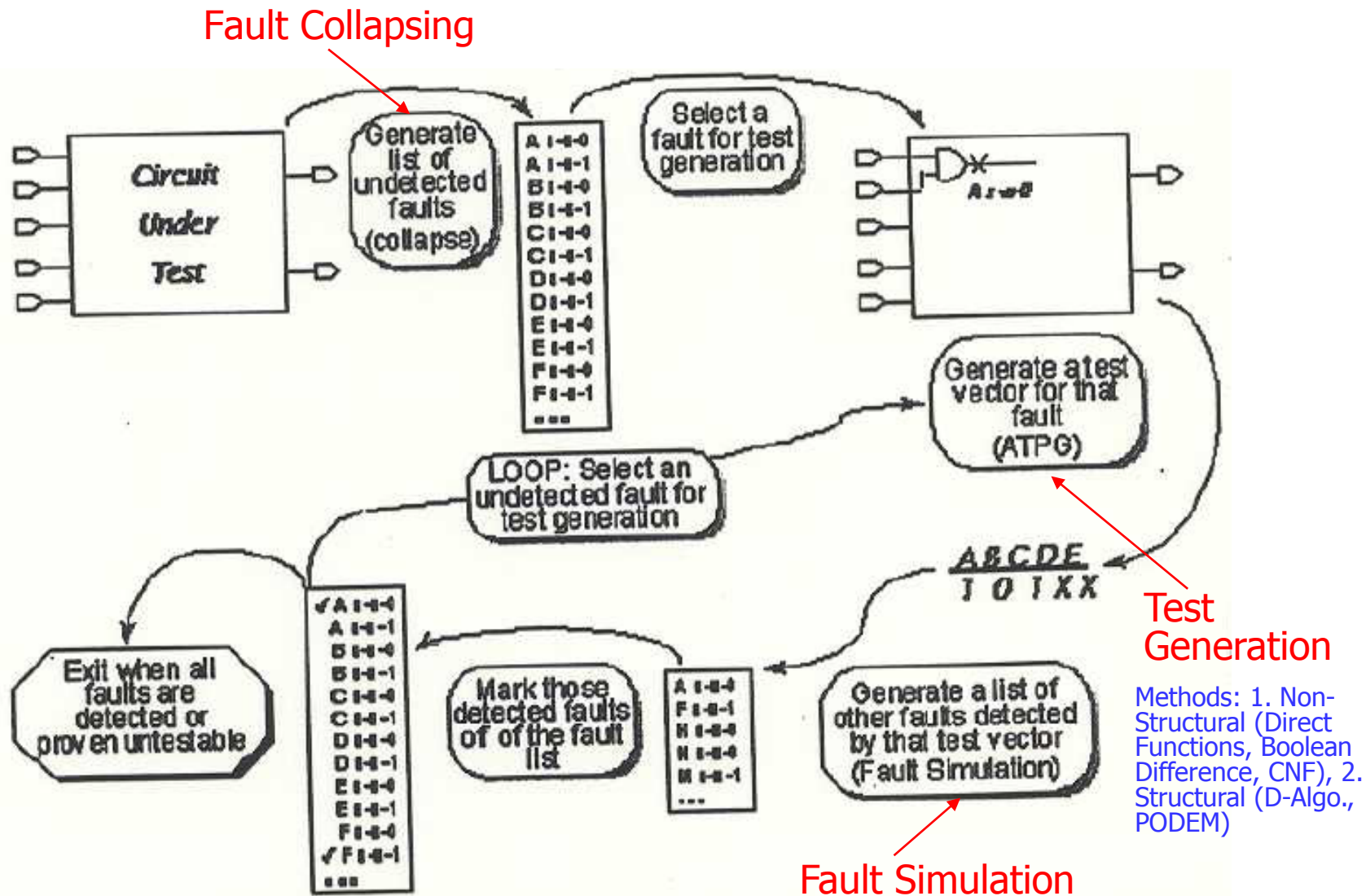

# Test Generation Techniques

---


- There are two main test vector generation techniques
  1. Non-Structural (Analytical)
    - Analyzes the gate-level description of a circuit and implicitly enumerate all possible input combinations to find a test vector for a target fault.
    - Methods: (i) Direct Function, (ii) Boolean Difference, (iii) CNF (product-of-sum form), ...
  2. Structural
    - Analyzes the structure of a given circuit to generate a test vector for a given target fault, or declare it untestable.
    - Methods: (i) D-Algorithm, (ii) PODEM, ...

---

# **Non-Structural Test Generation**
 
# Fault Detection in Combinational Circuits

- A test (vector)  $t$  detects a fault  $f$  if and only if  $Z_f(t) \neq Z(t)$  (i.e., at least one of the outputs are different in  $N$  and  $N_f$ ).
- For a single output circuit  $Z_f(t) \neq Z(t)$  is equivalent to  $Z_f(t) \oplus Z(t) = 1$
- Example: find tests to detect s-a-0 at  $x_4$ .



## Fault Detection – Formalization I

---

- Fault-free output:  $Z = (x_2 + x_3) \cdot x_1 + \bar{x}_1 \cdot x_4$
- Faulty output:  $Z_f = (x_2 + x_3) \cdot x_1$
- $Z \oplus Z_f = [(x_2 + x_3) \cdot x_1 + \bar{x}_1 \cdot x_4] \oplus [(x_2 + x_3) \cdot x_1] = \dots = \bar{x}_1 \cdot x_4$
- Test vectors to detect s-a-0 at  $x_4$  satisfy  $\bar{x}_1 x_4 = 1$  that are:

$x_1$	$x_2$	$x_3$	$x_4$	$\equiv$	$x_1$	$x_2$	$x_3$	$x_4$
0	x	x	1		0	0	0	1
					0	0	1	1
					0	1	0	1
					0	1	1	1

# Boolean Difference

---

- Consider a Boolean function  $f(x)$  where  $x=(x_1,x_2,\dots,x_i,\dots,x_n)$  is the input vector.

- Cofactors of  $f$ :
$$\begin{cases} f_{x_i} = f|_{x_i=1} = f(x_1,\dots,x_i=1,\dots,x_n) \\ f_{\bar{x}_i} = f|_{x_i=0} = f(x_1,\dots,x_i=0,\dots,x_n) \end{cases}$$

- Shannon Expansion Theorem:

$$\begin{cases} f(x) = x_i \cdot f_{x_i} + \bar{x}_i \cdot f_{\bar{x}_i} \\ f(x) = (x_i + f_{\bar{x}_i}) \cdot (\bar{x}_i + f_{x_i}) \end{cases}$$

- Boolean Difference:  $\frac{df}{dx_i} = f_{x_i} \oplus f_{\bar{x}_i}$



# Fault Detection – Formalization II

---

- Definition of Boolean difference:

$$\frac{df}{dx_i} = f_{x_i} \oplus f_{\bar{x}_i}$$


- $\frac{df}{dx_i} = 0$  means s-a-0 or s-a-1 at  $x_i$  cannot be observed at the output. In other words, s-a-f at  $x_i$  is undetectable.
- If  $\frac{df}{dx_i} = 1$  then:
  - $\frac{df}{dx_i} \cdot x_i = 1$  gives all test vectors that can detect s - a - 0 at  $x_i$
  - $\frac{df}{dx_i} \cdot \bar{x}_i = 1$  gives all test vectors that can detect s - a - 1 at  $x_i$

Propagate the fault effect

Stimulate the fault

# Boolean Difference – Formalization II (cont'd)

- Example:

 

$$f = \overline{a}b \cdot (a + p)$$

$$\frac{df}{dp} = f|_{p=0} \oplus f|_{p=1} = [\overline{a}b \cdot a] \oplus [\overline{a}b] = [(ab + \overline{a}) \cdot \overline{a}b] + (\overline{a}b \cdot a) \cdot ab$$

$$= ab \cdot \overline{a}b + (\overline{a} \cdot \overline{a}b) = \overline{a} \cdot (\overline{a} + b) = \overline{a}$$

$$\Rightarrow \frac{df}{dp} \cdot p = \overline{a} \cdot b = 1 \Rightarrow ab = 01$$

- So,  $ab=01$  is the only test vector that can detect s-a-0 at line p.

# Generalization – Formalization III

---

- There are systematic approaches that generalize ATPG (automatic test pattern generation) analytically.
- ATPG using **satisfiability** requires two independent steps
  1. extraction of the CNF (**conjunctive normal form**, i.e. AND of OR-clauses) formula
  2. identification of a satisfying assignment

# CNF for Test Generation

---

- The complete CNF is made of three CNF terms corresponding to
  1. The fault-free circuit ( $CNF_g$ )
  2. Faulty circuit ( $CNF_f$ )
  3. Condition for fault detection in a single-output circuit ( $CNF_d$ )

# ATPG Using Satisfiability

---

- **Step 1**
  - extraction of the CNF (conjunctive normal form – i.e. AND of OR-clauses) formula

# 0. CNF for the Fault-Free Gates

- Example (a 2-input AND):

$$v(c_j) = v(c_{i1}) \cdot v(c_{i2})$$

$$[v(c_{i1}) \cdot v(c_{i2})] \oplus v(c_j) = 0$$

$$\overline{v(c_{i1})} \cdot v(c_j) + \overline{v(c_{i2})} \cdot v(c_j) + v(c_{i1}) \cdot v(c_{i2}) \cdot \overline{v(c_j)} = 0$$

$$[v(c_{i1}) + \overline{v(c_j)}][v(c_{i2}) + \overline{v(c_j)}][\overline{v(c_{i1})} + \overline{v(c_{i2})} + v(c_j)] = 1$$

$c_{i1}$	$c_{i2}$	$c_j$	CNF (Fault-Free)
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	1


$c_{i1}$	$c_{i2}$	$c_j$	CNF (Faulty)
0	0	1	0
0	1	1	0
1	0	1	0
1	1	0	0

**Table 4.4.** CNF formulae for fault-free primitive gates and fanout system

Circuit element	CNF formula
NOT	$[v(c_{i1}) + v(c_j)][\overline{v(c_{i1})} + \overline{v(c_j)}]$
AND	$[v(c_{i1}) + \overline{v(c_j)}][v(c_{i2}) + \overline{v(c_j)}][\overline{v(c_{i1})} + \overline{v(c_{i2})} + v(c_j)]$
NAND	$[v(c_{i1}) + v(c_j)][v(c_{i2}) + v(c_j)][\overline{v(c_{i1})} + \overline{v(c_{i2})} + \overline{v(c_j)}]$
OR	$[\overline{v(c_{i1})} + v(c_j)][\overline{v(c_{i2})} + v(c_j)][v(c_{i1}) + v(c_{i2}) + \overline{v(c_j)}]$
NOR	$[\overline{v(c_{i1})} + \overline{v(c_j)}][\overline{v(c_{i2})} + \overline{v(c_j)}][v(c_{i1}) + v(c_{i2}) + v(c_j)]$
Fanout system	$[v(c_i) + \overline{v(c_{j1})}][\overline{v(c_i)} + v(c_{j1})]$ , for each branch $c_{j1}$
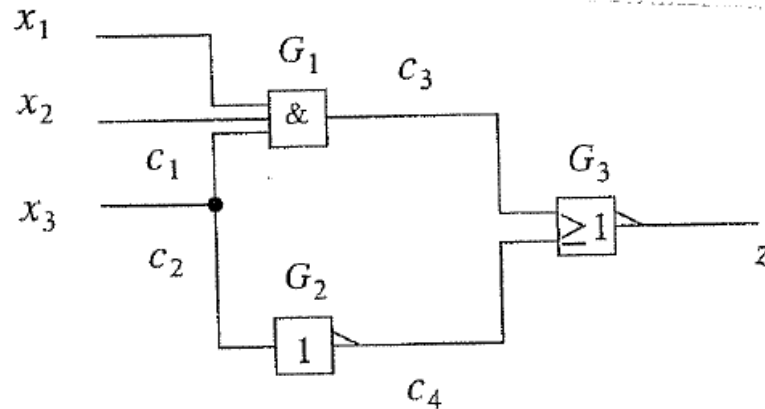
# 1. CNF for the Fault-Free Circuit


- Concatenate CNFs for each individual gate and fanout branches



$$\begin{aligned}
 CNF_g = & [\overline{v(x_3) + v(c_1)}][\overline{v(x_3) + v(c_1)}] \quad \text{fanout branch } c_1 \\
 & [\overline{v(x_3) + v(c_2)}][\overline{v(x_3) + v(c_2)}] \quad \text{fanout branch } c_2 \\
 & [\overline{v(c_{x1}) + v(c_3)}][\overline{v(c_{x2}) + v(c_3)}][\overline{v(c_1) + v(c_3)}][\overline{v(c_{x1}) + v(c_{x2}) + v(c_1) + v(c_3)}] \quad \text{AND } G1 \\
 & [\overline{v(c_2) + v(c_4)}][\overline{v(c_2) + v(c_4)}][\overline{v(c_3) + v(z)}][\overline{v(c_4) + v(z)}][\overline{v(c_3) + v(c_4) + v(z)}] \\
 & \quad \leftarrow \text{NOT } G2 \quad \quad \quad \leftarrow \text{NOR } G3
 \end{aligned}$$
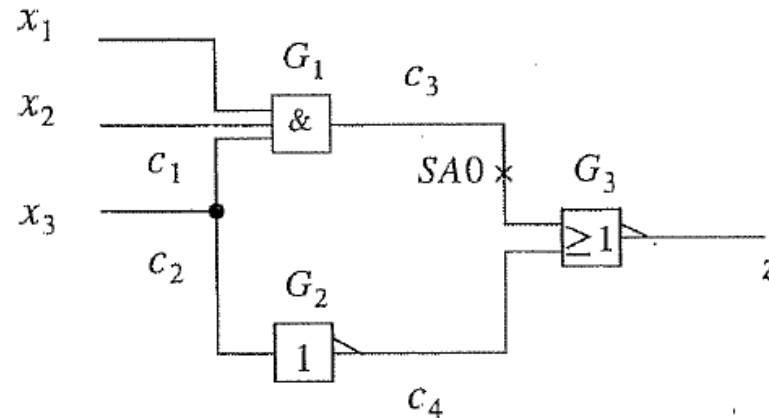
## 2. CNF for the Faulty Circuit

- It includes only the clause for the faulty gate.
  - The  $v'$  variables are introduced to indicate that lines may have different values in the fault-free and faulty circuits.



$$CNF_f = [\overline{v'(c_3)} + \overline{v'(z)}][\overline{v(c_4)} + \overline{v'(z)}][v'(c_3) + v(c_4) + v'(z)]$$


 Faulty NOR G3



### 3. CNF for Fault Detection Condition

- We define  $a(c_j)$  as an **active variable** for the transitive fanout (e.g. circuit outputs) of the fault site. If a fault effect appears at  $c_j$ , then it implies the fault-free and faulty values are complement of each other and can be detected at  $c_j$  (e.g. a circuit output). Note that:  $(p \rightarrow q)'$  and  $p \cdot q'$  are equivalent.

$$a(c_j) \Rightarrow v(c_j) \neq v'(c_j)$$

$$a(c_j) \Rightarrow v(c_j) \oplus v'(c_j)$$

$$a(c_j) \cdot \overline{[v(c_j) \oplus v'(c_j)]}$$

$$a(c_j) \cdot [v(c_j) \cdot v'(c_j) + \overline{v(c_j)} \cdot \overline{v'(c_j)}]$$

$$[a(c_j) \cdot \overline{v(c_j)} \cdot \overline{v'(c_j)}] + [a(c_j) \cdot v(c_j) \cdot v'(c_j)]$$

- Finally, complementing it again:

$$CNF_a(c_j) = [\overline{a(c_j)} + v(c_j) + v'(c_j)][\overline{a(c_j)} + \overline{v(c_j)} + \overline{v'(c_j)}]$$

### 3. CNF for Fault Detection Condition (cont.)

- The condition under which the fault effect appears in the output  $z$  requires an active clause that says the faulty and fault-free values on  $z$  will be different.

$$\begin{aligned} \text{Necessary Condition (in output } v(z) \# v'(z)) \quad & \text{Sufficient Condition (Activate \& propagate to } z) \\ \text{CNF}_d = \overbrace{\text{CNF}_a(z)}^{\text{Necessary Condition}} \cdot \underbrace{a(z)}_{\text{Sufficient Condition}} \\ = [\overline{a(z)} + v(z) + v'(z)] [\overline{a(z)} + \overline{v(z)} + \overline{v'(z)}] \cdot a(z) \end{aligned}$$

- Overall, any assignment of primary inputs that satisfies this CNF formula is a test vector for the target fault in the single-output circuit.

$$\text{CNF}_g \cdot \text{CNF}_f \cdot \text{CNF}_d$$

### 3. CNF for Fault Detection Condition (cont.)

---

- Extension to multi-output circuit is straightforward.
- The only part that needs change is  $CNF_d$

$$CNF_d = CNF_a(z_1) \cdot CNF_a(z_2) \cdots CNF_a(z_m) [a(z_1) + a(z_2) + \cdots + a(z_m)]$$

- Again, any assignment of primary inputs that satisfies this CNF formula is a test vector for the target fault in the multi-output circuit.

$$CNF_g \cdot CNF_f \cdot CNF_d$$

# A Small Example of CNF


---

- Consider a NOR gate (as a small circuit)
  - After collapsing, there are 3 faults: x sa0, y sa0, y sa1.
- For fault x sa0:

$$CNF_g = [\bar{x} + \bar{z}][\bar{y} + \bar{z}][x + y + z]$$

$$CNF_f = [\bar{x}' + \bar{z}'][\bar{y} + \bar{z}'][x' + y + z']$$
 
$$CNF_d = [\bar{a} + z + z'][\bar{a} + \bar{z} + \bar{z}'][a]$$



- To find the pattern we need to satisfy:

$$CNF_g \cdot CNF_f \cdot CNF_d = 1$$

- Only: a=1, **x=1**, x'=0, **y=0**, z=0, z'=1 satisfies this CNF, which means there is only one pattern **xy=10**.

# ATPG Using Satisfiability

---

- **Step 2**
  - identification of a satisfying assignment
  - Binary Decision Diagram (BDD) is often used