

---

# EEDG/CE 6303: Testing and Testable Design

*Mehrdad Nourani*


**Dept. of ECE  
Univ. of Texas at Dallas**

---

# Session 04

## **Fault Simulation**

# Fault Analysis System (Review)

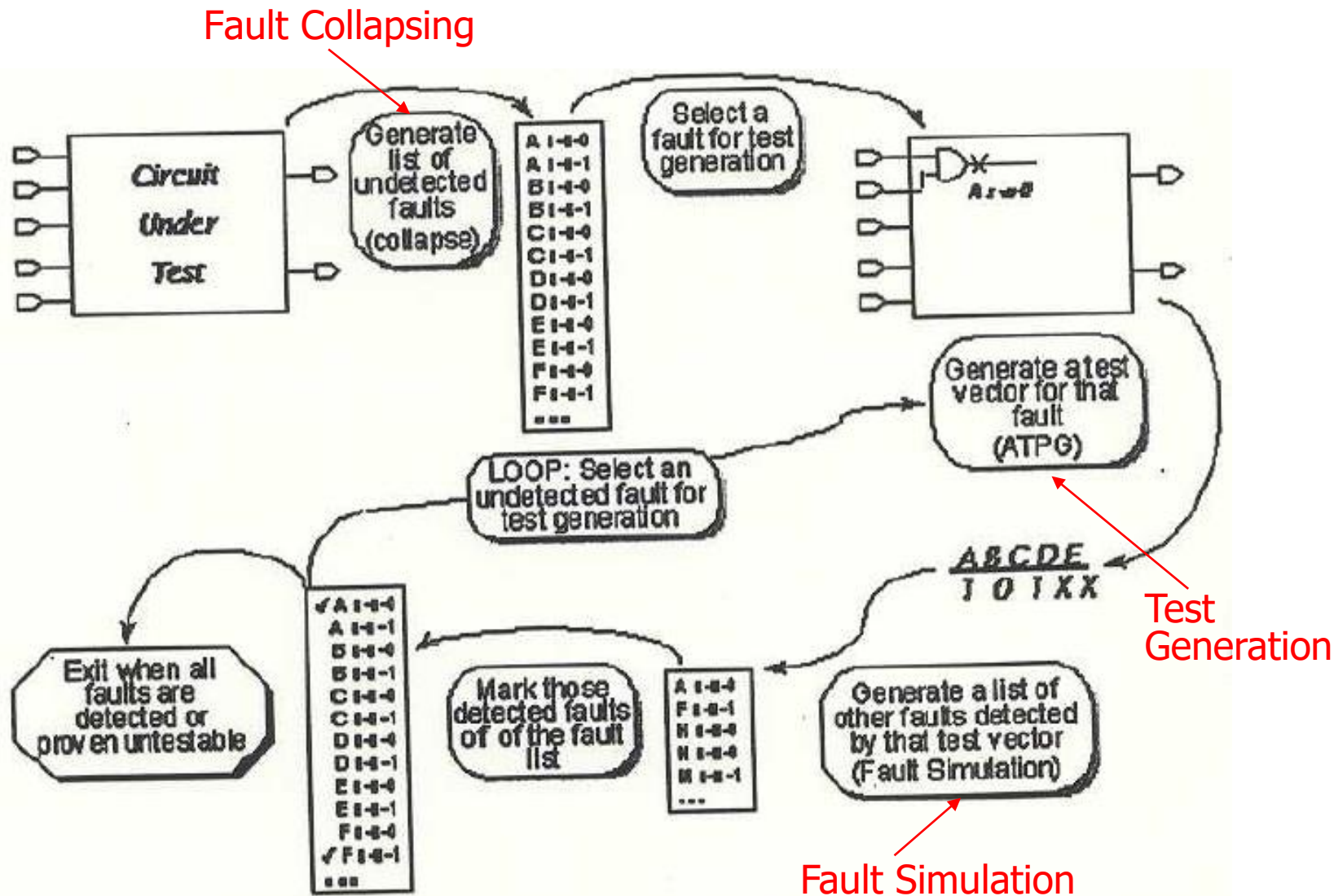

---

# **Logic Simulation**

# Logic Simulation

---

- **Logic simulation** for a combinational logic circuit is the determination of steady-state logic values implied at each circuit line by the vector applied to its primary inputs
  - **Two-valued** logic simulation: When each component of the vector applied  $P = (p_1, p_2, \dots, p_n)$  is fully-specified, i.e., can take only two values – 0 and 1
  - **Three-valued** logic simulation: When one or more component of vector applied is incompletely specified, i.e., has the value  $x$
  - There are 5, 7, 9, even 41-level logic simulation where more detailed information is processed and provided.


## Logic Simulation (cont'd)

---

- Such simulators implicitly assume that the details of delays are unimportant in determining the steady state values implied by this vector
  - Are hence called **cycle-based** or **zero delay** simulators
  - If used to verify correctness of a circuit design, such simulation must be complemented by **timing analysis**
- A simple logic simulator must
  - Read vector to be simulated and assign the values to corresponding inputs
  - Compute the value implied by the vector at each circuit line
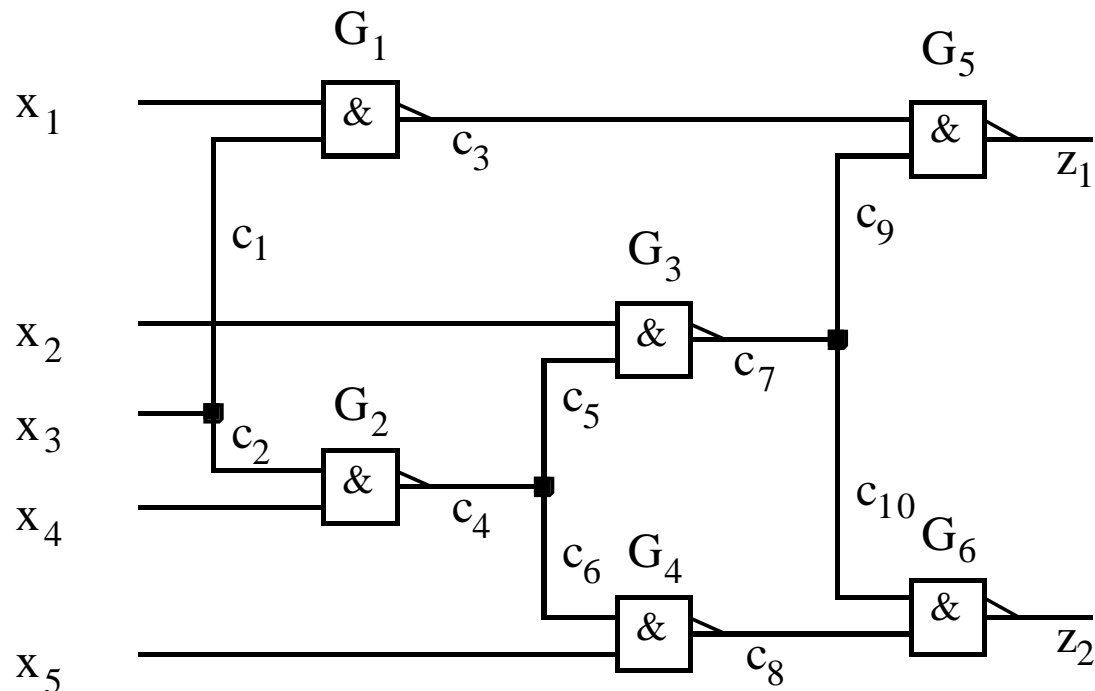
## Logic Simulation (cont'd)

- However, the value at a line must be computed **after** the values at all its fanins are computed
  - E.g., value at  $c_7$  must be computed after those at both its fan-ins,  $x_2$  and  $c_5$ , are computed



# Level-Based Logic Simulation

---

- For combinational circuits, lines can be ordered a priori to ensure correct logic simulation
  - **Input level** of line  $c_i$  in a combinational circuit,  $\eta_{\text{inp}}(c_i)$ , is the maximum number of circuit elements traversed along any path from any of the circuit inputs to the line
  - Circuit lines can then be considered during simulation in non-decreasing order in terms of the values of their input levels



# Level-Based Logic Simulation (cont'd)


- Procedure **InputLevelize()** can compute  $\eta_{inp}(c_i)$  for all lines

## Procedure 3.2: InputLevelize()

1. *Initialization* : For each circuit line  $c$ ,  $\eta_{inp} = \text{undefined}$ .
  2. For each primary input  $x_i$ ,  $\eta_{inp} = 0$ .
  3. While there exists one or more logic elements such that (i)  $\eta_{inp}$  is defined for each of the element's inputs, and (ii)  $\eta_{inp}$  is undefined for any of its outputs, select one such element.
    - (a) If the selected element is a gate with inputs  $c_{i_1}, c_{i_1}, \dots, c_{i_\alpha}$  and output  $c_j$ , then assign  $\eta_{inp}(c_j) = \max[\eta_{inp}(c_1), \eta_{inp}(c_2), \dots, \eta_{inp}(c_\alpha)] + 1$ .
    - (b) If the selected element is a fanout system with stem  $c_i$  and branches  $c_{j_1}, c_{j_2}, \dots, c_{j_\beta}$ , then for each output  $c_{j_l}$ , where  $l = 1, 2, \dots, \beta$ , assign  $\eta_{inp}(c_{j_l}) = \eta_{inp}(c_i) + 1$ .
- Note that Step 3 of above procedure can be implemented more efficiently
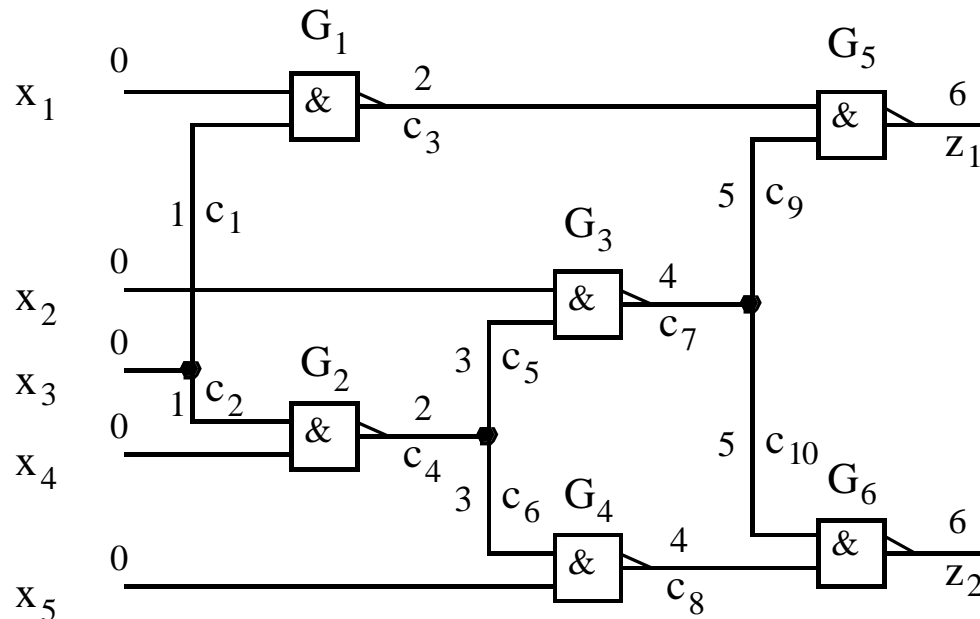
## Level-Based Logic Simulation (cont'd)

- Once  $\eta_{\text{inp}}$  is computed for each line, the lines can be sorted in ascending order of their  $\eta_{\text{inp}}$  values in an **ordered list**  $Q_{\eta_{\text{inp}}}$ .
- Example of computing  $\eta_{\text{inp}}$  :




# Level-Based Logic Simulation (cont'd)

- Once the  $\eta_{inp}$  values are computed, the lines can be ordered as:

$$Q_{\eta_{inp}} = (x_1, x_2, x_3, x_4, x_5, c_1, c_2, c_3, c_4, c_5, c_6, c_7, c_8, c_9, c_{10}, z_1, z_2)$$

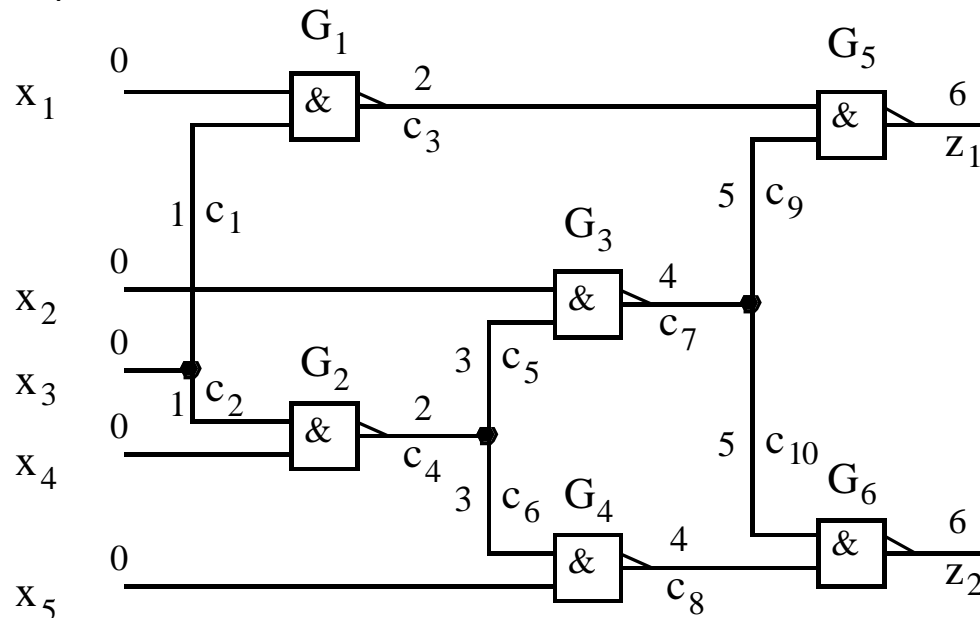- Note that  $Q_{\eta_{inp}}$  is not unique in this case
- Circuit lines can be considered in the sequence given by  $Q_{\eta_{inp}}$  during logic simulation



# Level-Based Logic Simulation (cont'd)

- 2-level logic simulation of primitive gates:

$v(c_{i_1})$		$v(c_{i_2})$		$v(c_{i_1})$		$v(c_{i_2})$						
0	1	0	1	0	1	0	1	$v(c_i)$	$v(c_{j_1})$	$\dots$	$v(c_{j_l})$	$\dots$
1	0	1	1	1	0	1	0	0	0	$\dots$	0	$\dots$
								1	1	$\dots$	1	$\dots$
NOT		NAND		XOR								

Gate driving line $c_j$	Logic expression $\mathcal{G}_j^2()$
NOT	$v(c_j) = \text{not } v(c_{i_1})$
AND	$v(c_j) = v(c_{i_1}) \text{ and } v(c_{i_2})$
NAND	$v(c_j) = \text{not } [v(c_{i_1}) \text{ and } v(c_{i_2})]$
OR	$v(c_j) = v(c_{i_1}) \text{ or } v(c_{i_2})$
NOR	$v(c_j) = \text{not } [v(c_{i_1}) \text{ or } v(c_{i_2})]$
XOR	$v(c_j) = \{v(c_{i_1}) \text{ and } [\text{not } v(c_{i_2})]\} \text{ or } \{[\text{not } v(c_{i_1})] \text{ and } v(c_{i_2})\}$

# Level-Based Logic Simulation (cont'd)

- 3-level logic simulation of primitive gates:

																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																					</
--	--	--	--	----

# Level-Based Logic Simulation (cont'd)

---


- Simple logic simulation:

## Procedure 3.3: SimpleLogicSimulation()

1. *Preprocessing* : Use Procedure InputLevelize() to compute the input level  $\eta_{inp}(c_i)$  of each line and to obtain  $\mathcal{Q}_{\eta_{inp}}$ , the ordered list of circuit lines.
2. While there exists a vector to be simulated, read a vector  $P = (p_1, p_2, \dots, p_n)$ .
  - (a) For each primary input  $x_i$ , assign  $v(x_i) = p_i$ .
  - (b) In the order in which lines appear in  $\mathcal{Q}_{\eta_{inp}}$ , for each line  $c_i$  in  $\mathcal{Q}_{\eta_{inp}}$ , compute the value  $v(c_i)$ .
    - i. If  $c_j$  is the output of a gate, then use following equation.
$$v(c_j) = \mathcal{G}_j^2(v(c_{i_1}), v(c_{i_1}), \dots, v(c_{i_\alpha}))$$
    - ii. If  $c_j$  is a branch of a fanout system, then use the following equation.
$$v(c_j) = \mathcal{G}_j^2(v(c_i))$$


# Level-Based Logic Simulation (cont'd)

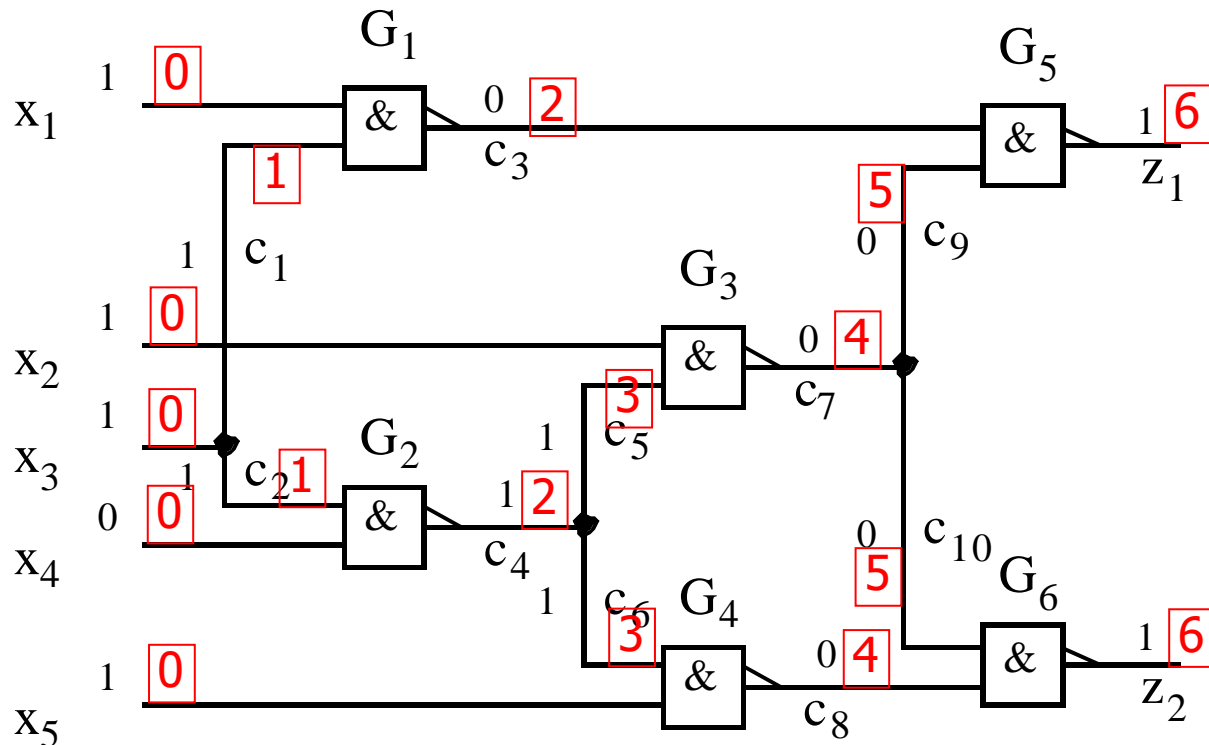- Example of simulation:
  - Vector  $P = (1, 1, 1, 0, 1)$
  - $Q_{\eta_{inp}} = (x_1, x_2, x_3, x_4, x_5, c_1, c_2, c_3, c_4, c_5, c_6, c_7, c_8, c_9, c_{10}, z_1, z_2)$


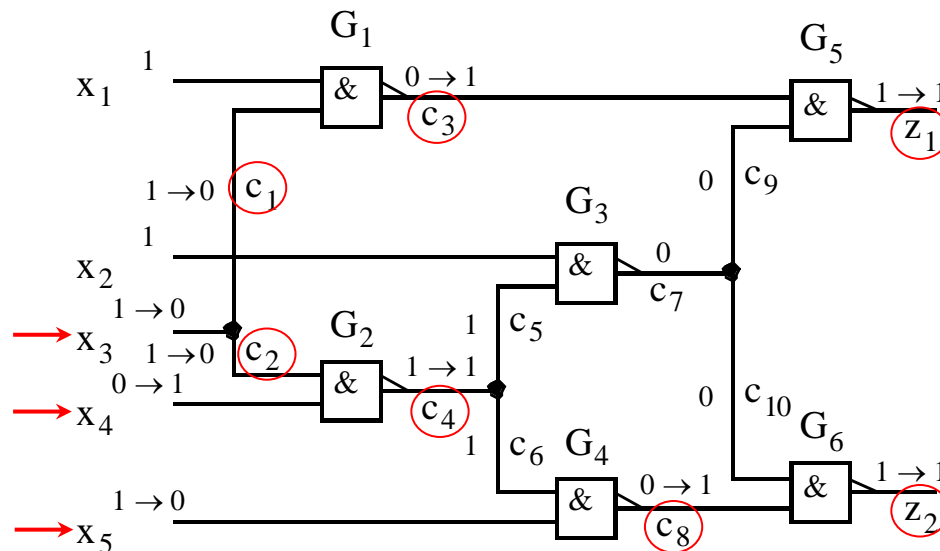
# Event-Driven Logic Simulation

- **Event-driven** logic simulation takes advantage of the fact that subsequent vectors simulated may imply the identical values at many circuit lines.
- $P = (x_1, x_2, x_3, x_4, x_5) = (1, 1, 1, 0, 1) \rightarrow P = (1, 1, 0, 1, 0)$



- When the second vector is simulated, values are recomputed at only 7 (out of 12) lines



## **Event-Driven Logic Simulation (cont'd)**

---


- An **event** is said to occur at a circuit line during the simulation of the current vector if the value implied at the line by the current vector is different from that implied by the previous vector simulated.
- Value at line  $c_j$  is recomputed only if an event occurs at one or more lines in its fanin
  - Sometimes the value recomputed for the current vector may turn out to be identical to that implied by the previous vector

# Event-Driven Logic Simulation (cont'd)

---

- Identification, recording, and use of events
  - The value implied at a line by the current vector compared with that for the previous vector
    - If the two are identical, no event
    - Otherwise, an event is identified
    - If necessary, the value at the line is updated
  - If an event is identified at  $c_i$ , then each line  $c_j$  in fanout of  $c_i$  is added to a list  $Q_{n_{inp}}(c_j)$  *if it does not already belong to the list*
    - At each step of the algorithm, the first non-empty list  $Q_i$  is identified
    - A line  $c_j$  is removed from  $Q_i$
    - Values implied at  $c_i$  by current vector is computed, presence or absence of event at  $c_j$  identified, value at  $c_i$  is updated, and any event at  $c_i$  is handled as above
    - Simulation for current vector stops when all  $Q_i$  are empty

# Event-Driven Logic Simulation (cont'd)

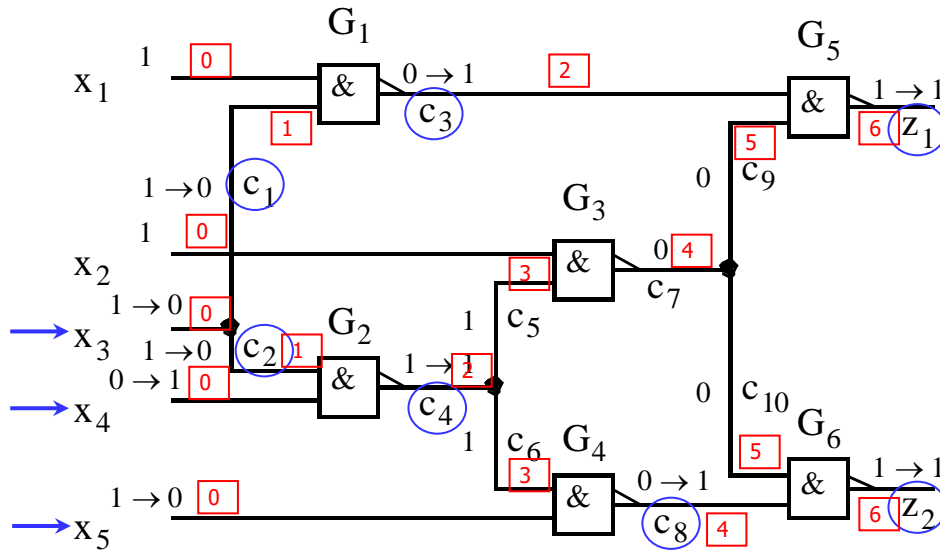

- If an event is identified at  $c_i$ , then each line  $c_j$  in fanout of  $c_i$  is added to a list  $Q_{n_{inp}}(c_j)$  if it does not already belong to the list
  - At each step of the algorithm, the first non-empty list  $Q_i$  is identified
  - A line  $c_j$  is removed from  $Q_i$
  - Values implied at  $c_i$  by current vector is computed, presence or absence of event at  $c_j$  identified, value at  $c_i$  is updated, and any event at  $c_i$  is handled as above
  - Simulation for current vector stops when all  $Q_i$  are empty

List	Lines	List	Lines	List	Lines	List	Lines	List	Lines	List	Lines	List	Lines	List	Lines	List	Lines
Q0	<b>x3</b> , x4, x5	Q0	<b>x4</b> , x5	Q0	<b>x5</b>	Q0		Q0		Q0		Q0		Q0		Q0	
Q1		Q1	c1, c2	Q1	c1, c2	Q1	<b>c1</b> , c2	Q1	<b>c2</b>	Q1		Q1		Q1		Q1	
Q2		Q2		Q2	c4	Q2	c4	Q2	c4, c3	Q2	<b>c4</b> , c3	Q2	<b>c3</b>	Q2		Q2	
Q3		Q3		Q3		Q3		Q3		Q3		Q3		Q3		Q3	
Q4		Q4		Q4		Q4	c8	Q4	c8	Q4	c8	Q4	c8	Q4	<b>c8</b>	Q4	
Q5		Q5		Q5		Q5		Q5		Q5		Q5		Q5		Q5	
Q6		Q6		Q6		Q6		Q6		Q6		Q6		Q6	z1	Q6	<b>z1, z2</b>

- The table is filled and values are assessed in breath-first (first-in first out) fashion.
  - **BLUE:** An event (a transition is assessed; one at a time)
  - **RED:** No event (transition stops; no need to traverse further)

# Fault Simulation

---

- **Goal:** to determine the list of faults in a CUT (Circuit Under Test) and to simulate the fault-free and faulty circuits efficiently to determine if their outputs are different
- Five tasks involved:
  1. Fault-free (good) circuit simulation
  2. Fault specification (fault list generation and collapsing)
  3. Fault insertion (fault selection to be simulated and tracing the presence of the faults)
  4. Fault effect generation and propagation
  5. Fault detection and discarding