
EEDG/CE 6303: Testing and Testable Design

Mehrdad Nourani

**Dept. of ECE
Univ. of Texas at Dallas**

Session 06


Test Generation for Sequential Circuits

Main Concept & Strategy

Sequential Circuits


- A sequential circuit has memory (e.g. flip-flops) in addition to combinational logic.
 - As the combinational part is much larger than the memory/feedback part, most approaches (e.g. DFT techniques) deal only with the combinational part.
- Test for a fault in a sequential circuit is a sequence of vectors, which
 - Initializes the circuit to a known state
 - Activates the fault, and
 - Propagates the fault effect to a primary output
- Methods of sequential circuit ATPG
 - Time-frame expansion methods
 - Simulation-based methods

Taxonomy

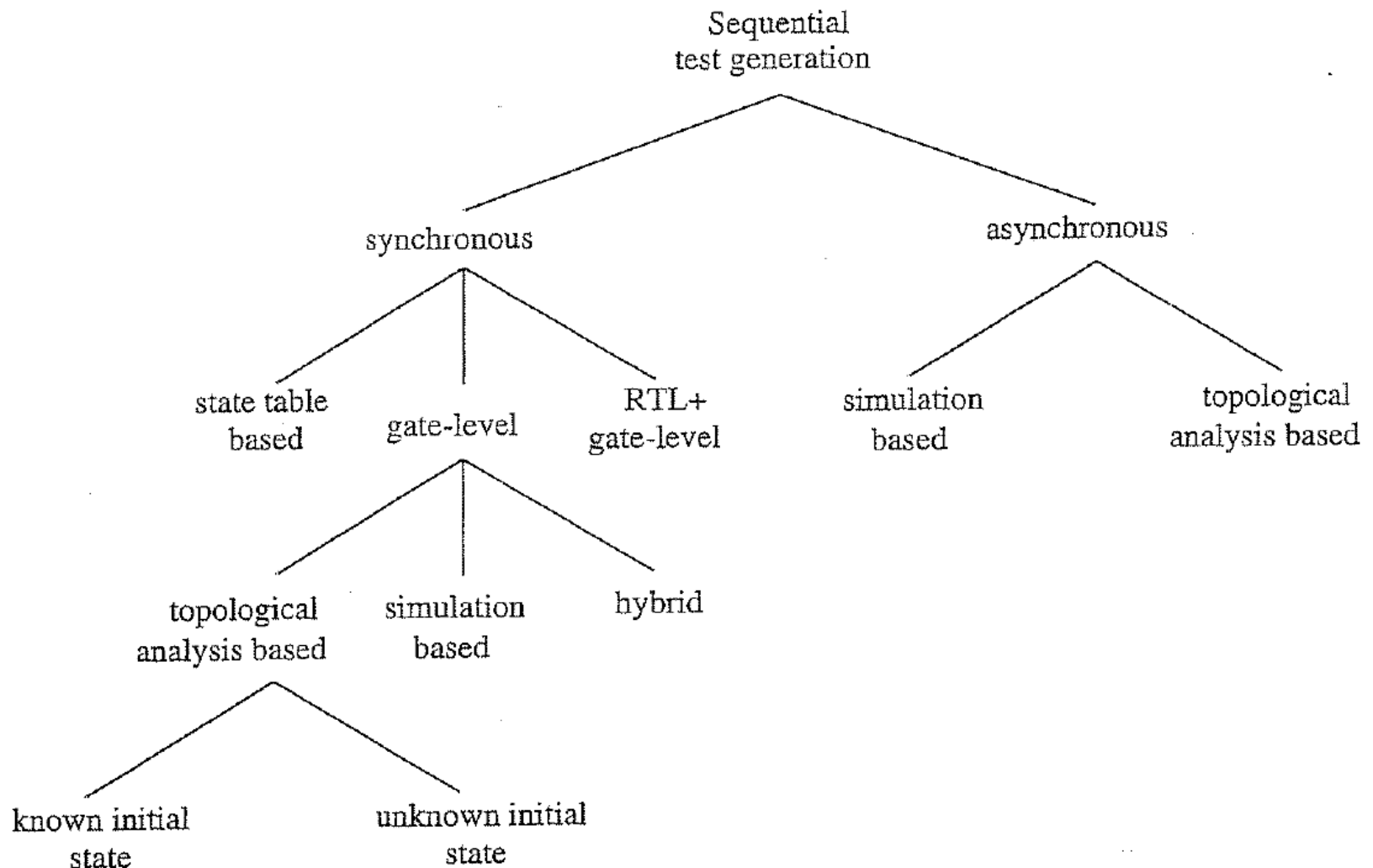



Concept of Time-Frames

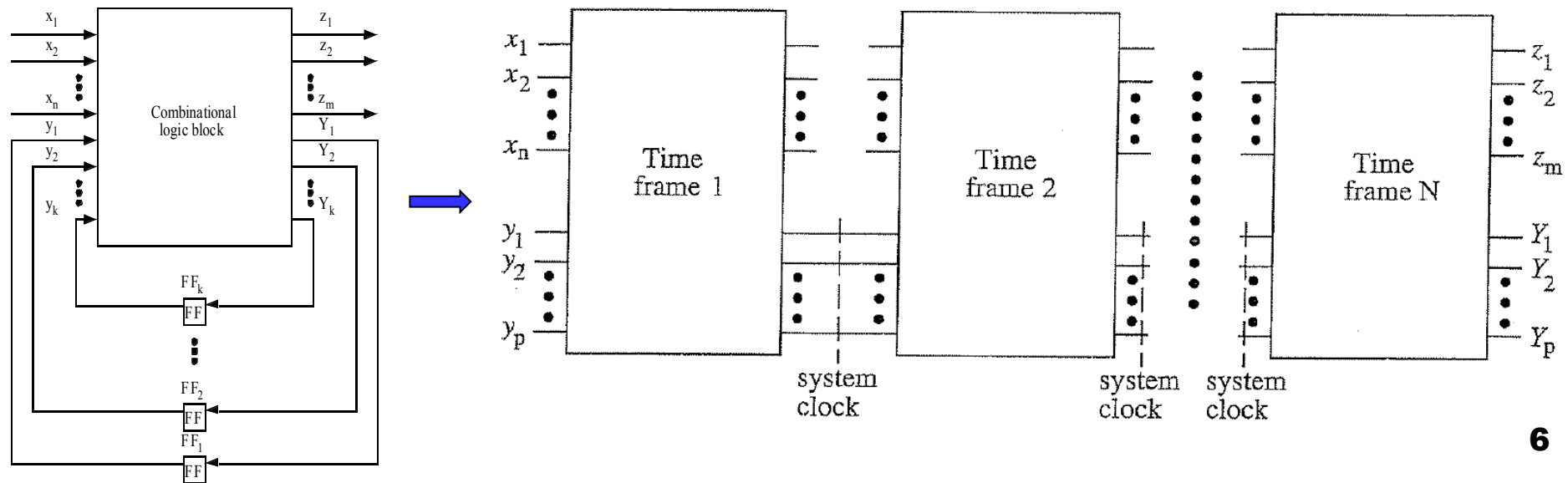- Most sequential test generation techniques are based on a combinational iterative array model
 - Feedback signals are generated from the copies of the combinational logic in the previous **time frames**
 - A clock pulse is applied between each pair of successive time frames to update the logic values
 - A single s-a-f corresponds to the fault in all time frames




Concept of Time-Frames (cont.)

  - If the effect of fault f does not propagate to the next-state line in a particular time frame, then the faulty and fault-free values of the corresponding present-state lines are the same in those time frames.
- A single event fault at one time frame may become a multiple-event fault in another time frame.



Concept of Time-Frames (cont.)

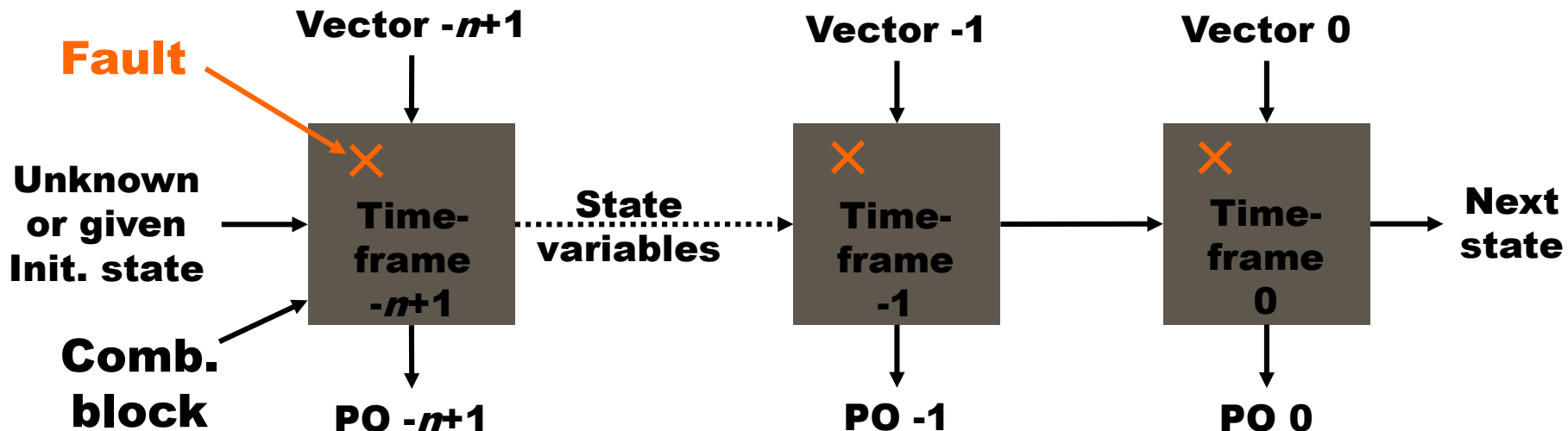- If the test sequence for a single stuck-at fault contains n vectors,
 - Replicate combinational logic block n times
 - Place fault in each block
 - Generate a test for the multiple stuck-at fault using combinational ATPG with 9-valued logic



Review: 5- and 9-Valued Calculus

- Roth's 5-Valued and Muth's 9-Valued Algebra

| Symbol | Meaning | Fault-Free (Good) | Faulty (Bad) |
|----------------|---------|----------------------|-----------------|
| 0 | 0/0 | 0 | 0 |
| 1 | 1/1 | 1 | 1 |
| D | 1/0 | 1 | 0 |
| \overline{D} | 0/1 | 0 | 1 |
| X | X/X | X | X |
| G0 | 0/X | 0 | X |
| G1 | 1/X | 1 | X |
| F0 | X/0 | X | 0 |
| F1 | X/1 | X | 1 |

5-Valued

9-Valued

Extended D-Algorithm


- Start with time frame 0 and use the D-algorithm to generate a test vector for this time frame
 - If the error propagates to at least one primary output in time frame 0, it's done (test vector is found)
 - If the error propagates only to the **next-state lines**, **a new time frame is added** as the next time frame to further propagate the error. This process continues until the error reaches at least one of the primary outputs.
 - If the test vector requires particular logic values at the **present-state lines** in time frame 0, **a new time frame is added at the previous time frame**. State justification is then performed backward through the previous time frame. The process continues until no specific logic values are required at the present-state lines.

Two Alternative Approaches


- In terms of mechanical process, we have two alternatives:
 1. Forward/Backward time frame expansion
 - Stimulate the fault and add time frames forward/backward
 - Propagating the fault effect and add time frames forward/backward
 - See Example I and II
 2. Backward time frame expansion
 - Start by assuming D (1/0) or D' (0/1) in one of the outputs in time frame 0
 - Only work backward until you find the answer (sequence of test patterns) or you run out of options
 - See Example III

Example I

- The circuit:

 


- Use 5-valued logic

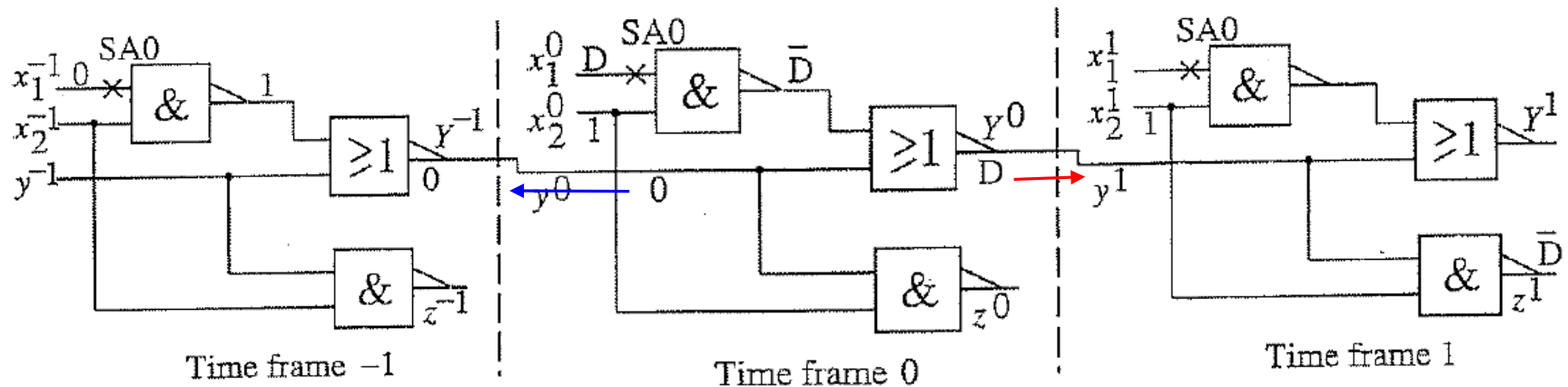


- Test Sequence: $(x_1 x_2) = \{(0x), (11), (x1)\}$ or $\{(x0), (11), (x1)\}$ 12

Example II: A Serial Adder

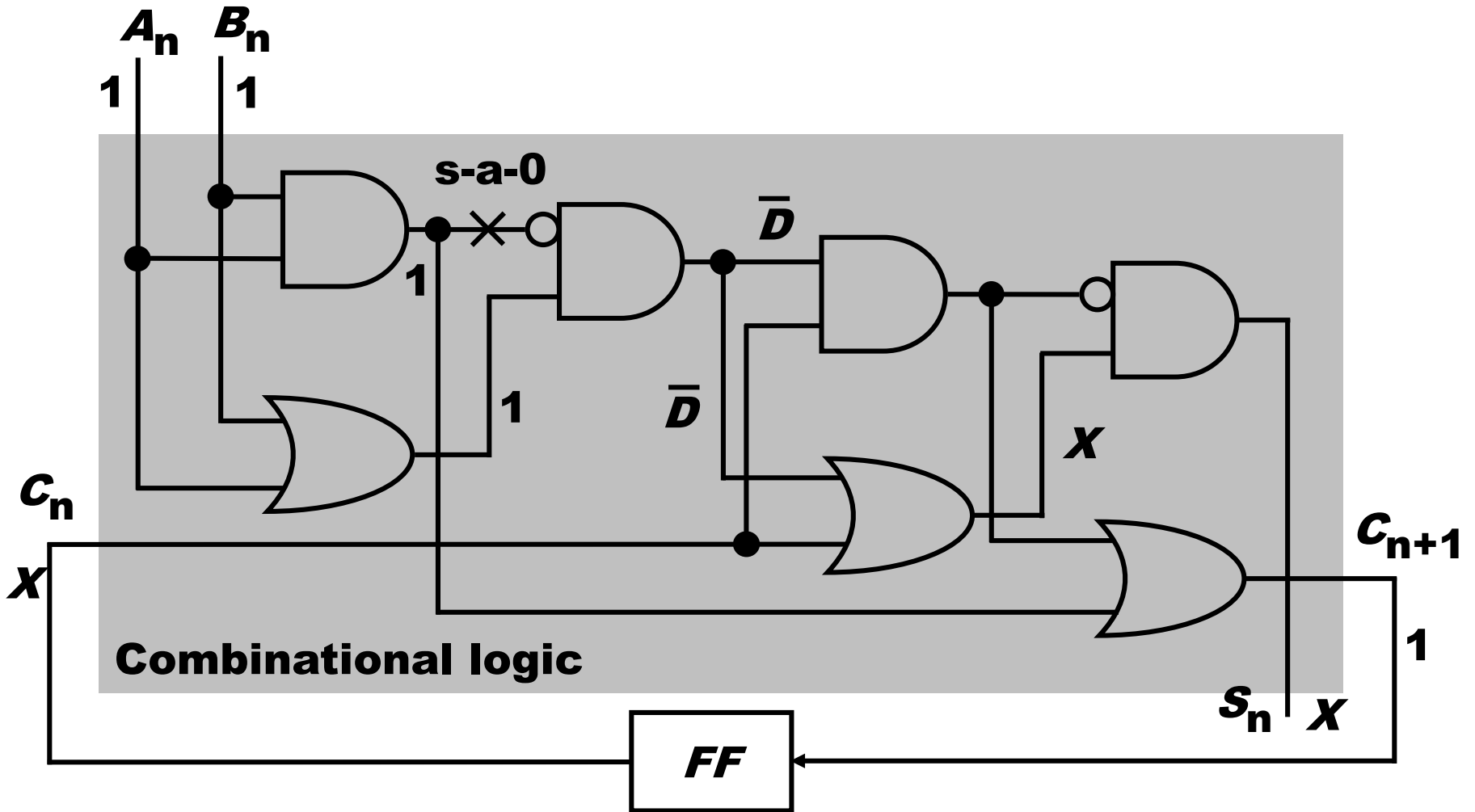

Example II

 


- Test Sequence: $(AB) = \{(11), (11)\}$

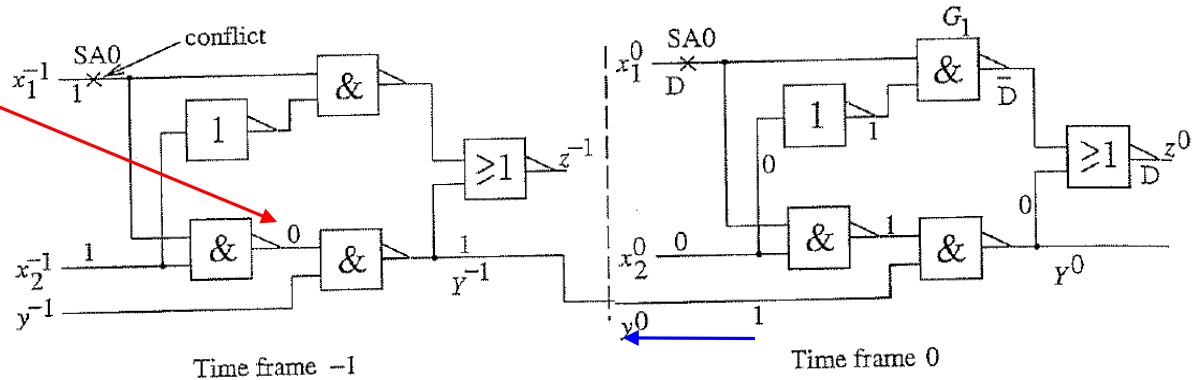Example - 5- vs. 9- Valued Logic


- Using 5-valued logic:

No pattern is found as "0" here is not guaranteed.




- Using 9-valued logic:

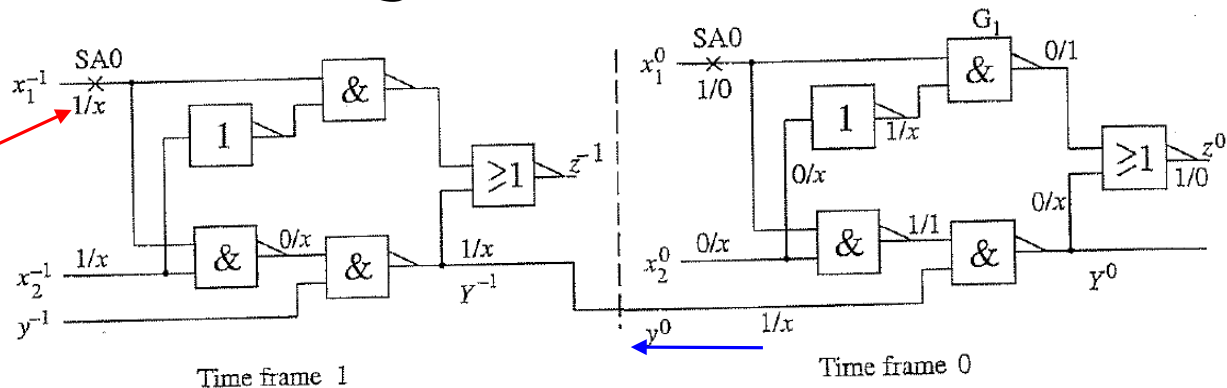Relaxed Requirement (more information processed)




- Test Sequence: $(x_1 x_2) = \{(11), (10)\}$

Example for Logic Systems

 


5-Valued Logic (Roth) 0, 1, D , \bar{D} , \bar{X}

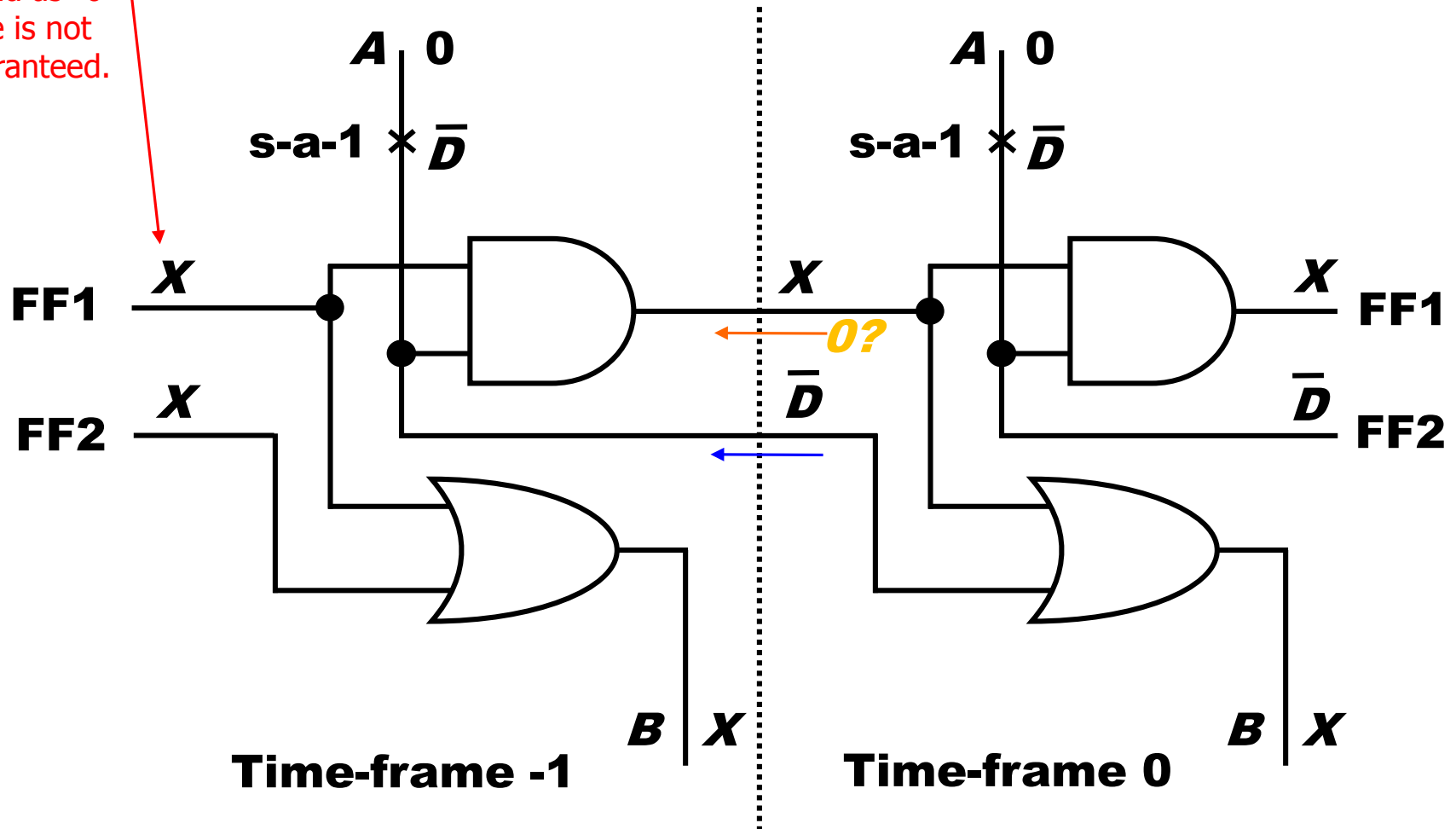No pattern is found as "0" here is not guaranteed.



- Test Sequence: Not Found.

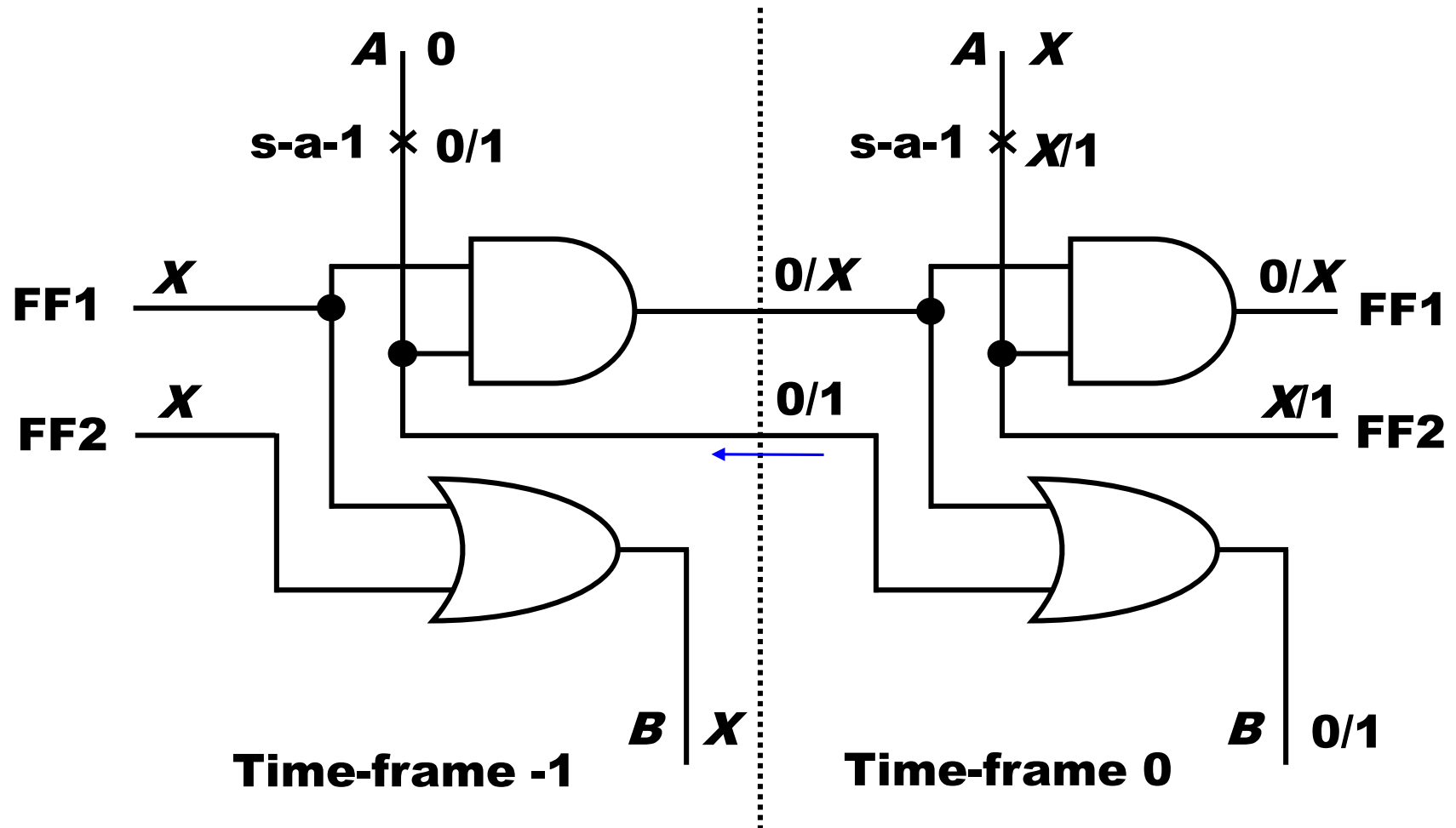9-Valued Logic (Muth) 0,1,1/0,0/1,1/X,0/X,X/0,X/1,X



- Test Sequence: $(A) = \{(0), (x)\}$


ATPG for Sequential Circuits

Implementation of ATPG

- Select a PO for fault detection based on drivability analysis (often based on CC0, CC1 and CO metrics).
- Place a logic value, 1/0 or 0/1, depending on fault type and number of inversions.
- Justify the output value from PIs, considering all necessary paths and adding backward time-frames.
- If justification is impossible, then use drivability to select another PO and repeat justification.
- If the procedure fails for all reachable POs, then the fault is *untestable*.
- If 1/0 or 0/1 cannot be justified at any PO, but 1/X or 0/X can be justified, the the fault is *potentially detectable*.

Complexity of ATPG

- Synchronous circuit -- All flip-flops controlled by clocks; PI and PO synchronized with clock:
 - Cycle-free circuit – No feedback among flip-flops: Test generation for a fault needs no more than $dseq + 1$ time-frames, where $dseq$ is the sequential depth.
 - Cyclic circuit – Contains feedback among flip-flops: May need 9^{Nff} time-frames, where Nff is the number of flip-flops.
- Asynchronous circuit – Higher complexity!

 


max = Number of distinct vectors with 9-valued elements = 9^{Nff}

Cycle-Free Circuits

- Characterized by absence of cycles among flip-flops and a sequential depth, $dseq$.
- $dseq$ is the maximum number of flip-flops on any path between PI and PO.
- Both good and faulty circuits are initializable.
- Test sequence length for a fault is bounded by $dseq+1$.


Cycle-Free Example

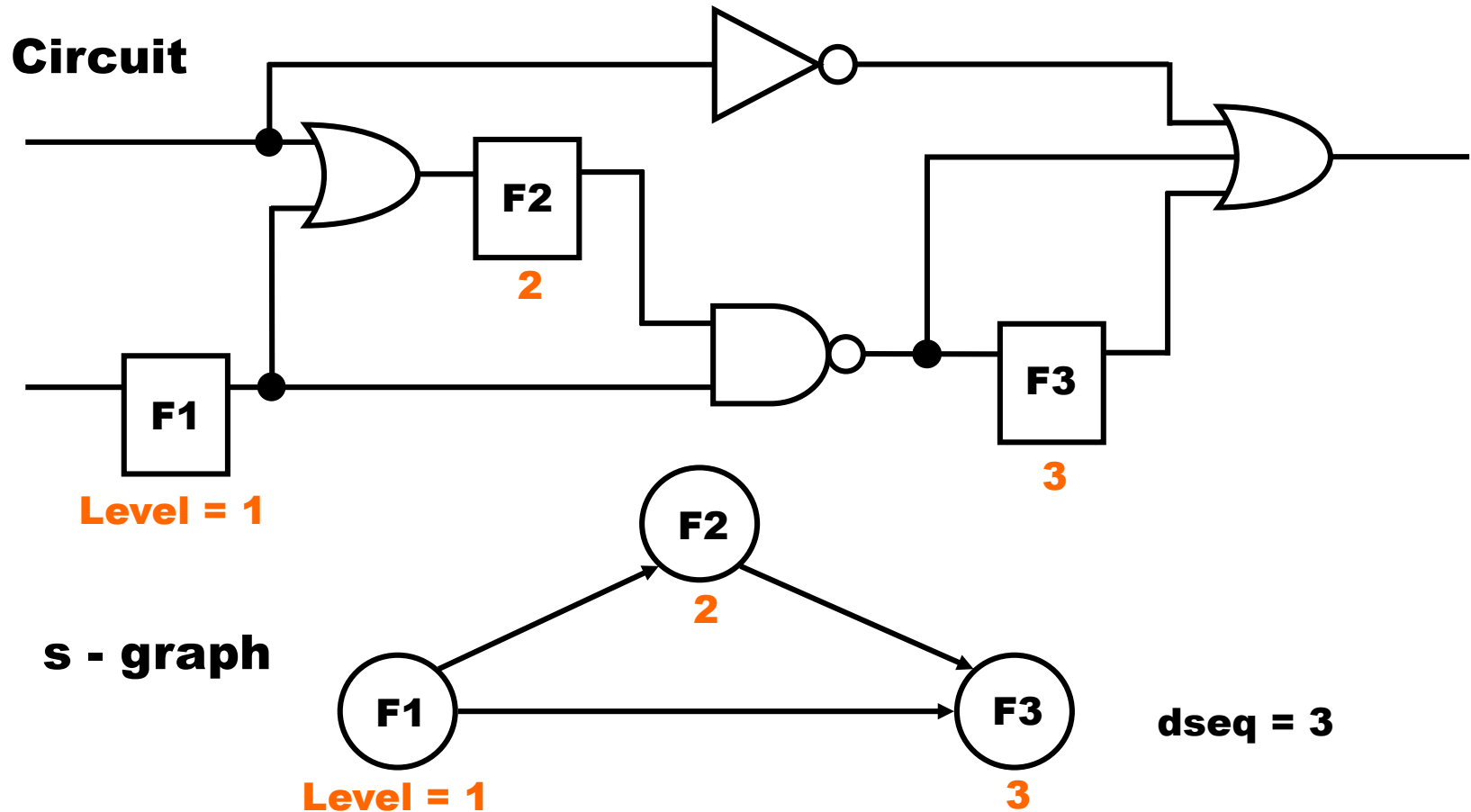


All faults are testable.

Cyclic Circuit Example

Modulo-3 counter

 

s - graph

 


Modulo-3 Counter


- Cyclic structure – Sequential depth is undefined.
- Circuit is not initializable. No tests can be generated for any stuck-at fault.
- After expanding the circuit to $9^{N_{ff}} = 81$, or fewer, time-frames ATPG program calls any given target fault untestable.
- Circuit can only be functionally tested by multiple observations.
- Functional tests, when simulated, give no fault coverage.

Adding Initializing Hardware

Initializable modulo-3 counter

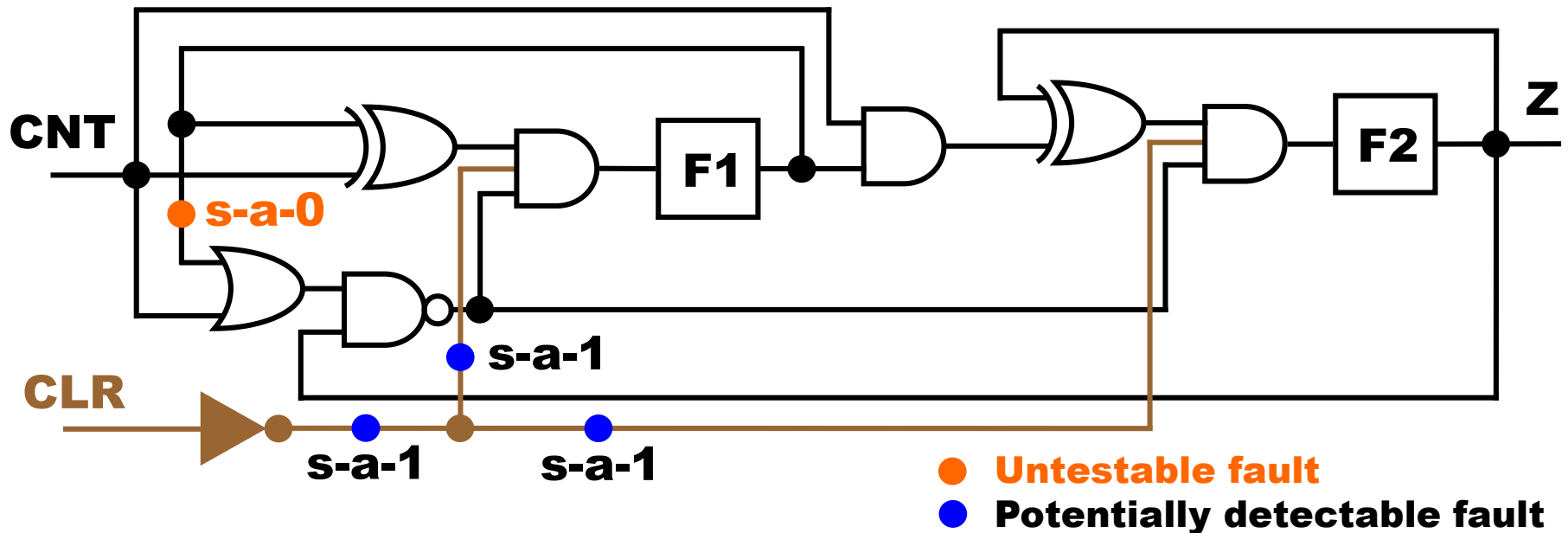

s - graph

 


Benchmark Circuits

| Circuit | s1196 | s1238 | s1488 | s1494 |
|-----------------------------|------------|------------|--------|--------|
| PI | 14 | 14 | 8 | 8 |
| PO | 14 | 14 | 19 | 19 |
| FF | 18 | 18 | 6 | 6 |
| Gates | 529 | 508 | 653 | 647 |
| Structure | Cycle-free | Cycle-free | Cyclic | Cyclic |
| Seq. depth | 4 | 4 | -- | -- |
| Total faults | 1242 | 1355 | 1486 | 1506 |
| Detected faults | 1239 | 1283 | 1384 | 1379 |
| Potentially detected faults | 0 | 0 | 2 | 2 |
| Untestable faults | 3 | 72 | 26 | 30 |
| Abandoned faults | 0 | 0 | 76 | 97 |
| Fault coverage (%) | 99.8 | 94.7 | 93.1 | 91.6 |
| Fault efficiency (%) | 100.0 | 100.0 | 94.8 | 93.4 |
| Max. sequence length | 3 | 3 | 24 | 28 |
| Total test vectors | 313 | 308 | 525 | 559 |
| Gentest CPU s (Sparc 2) | 10 | 15 | 19941 | 19183 |

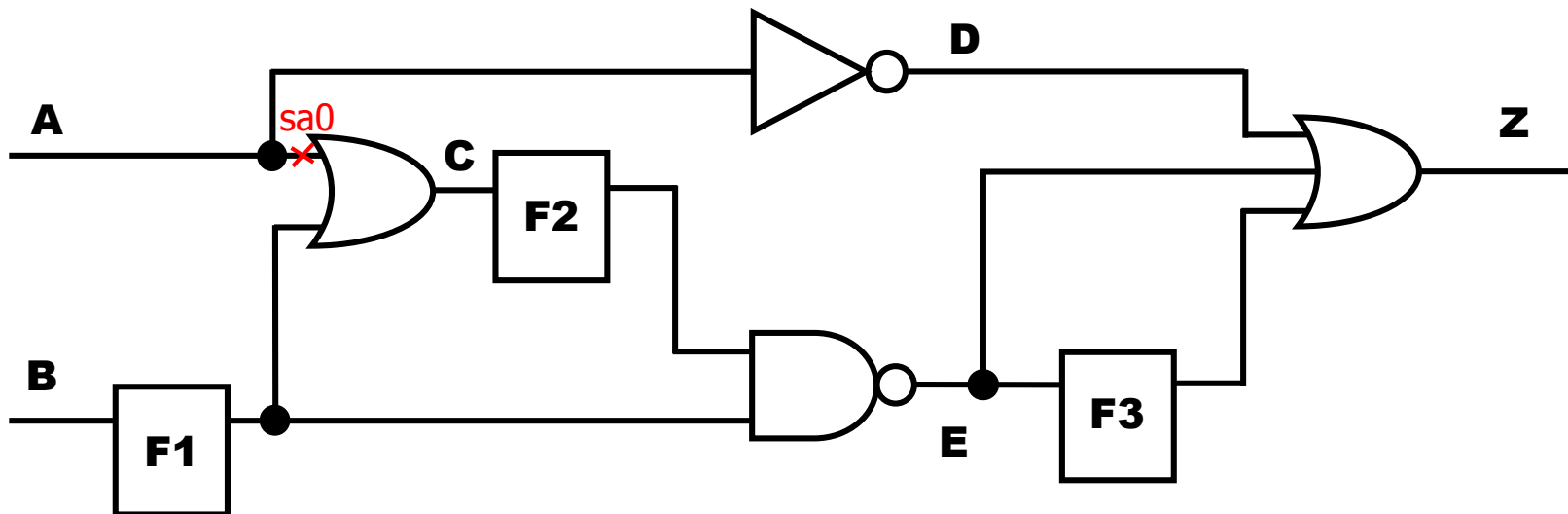
Example III: Cycle-Free Example

- We need at most 4 time-frames because $dseq+1=4$.
- A simple analysis tells us that the fault effect can be propagated to the output Z through two paths only:
 - $C \rightarrow F2 \rightarrow E \rightarrow Z$
 - $C \rightarrow F2 \rightarrow E \rightarrow F3 \rightarrow Z$
- The first path, being shorter (fewer FFs) is chosen as the primary option. Real test generators may use more complex analysis for grading the propagation paths.




Cycle-Free Example – Step 0

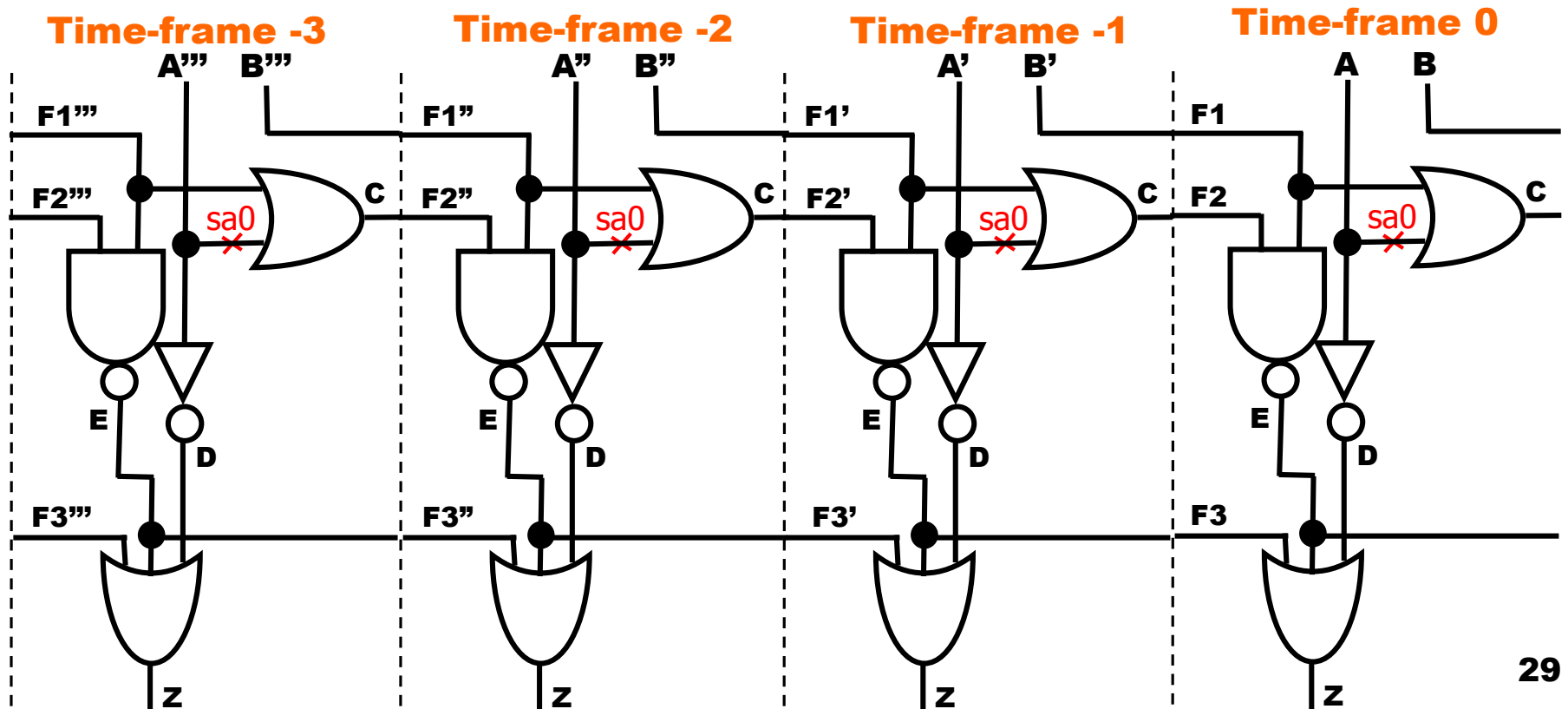- We need at most 4 time-frames because $dseq+1=4$.



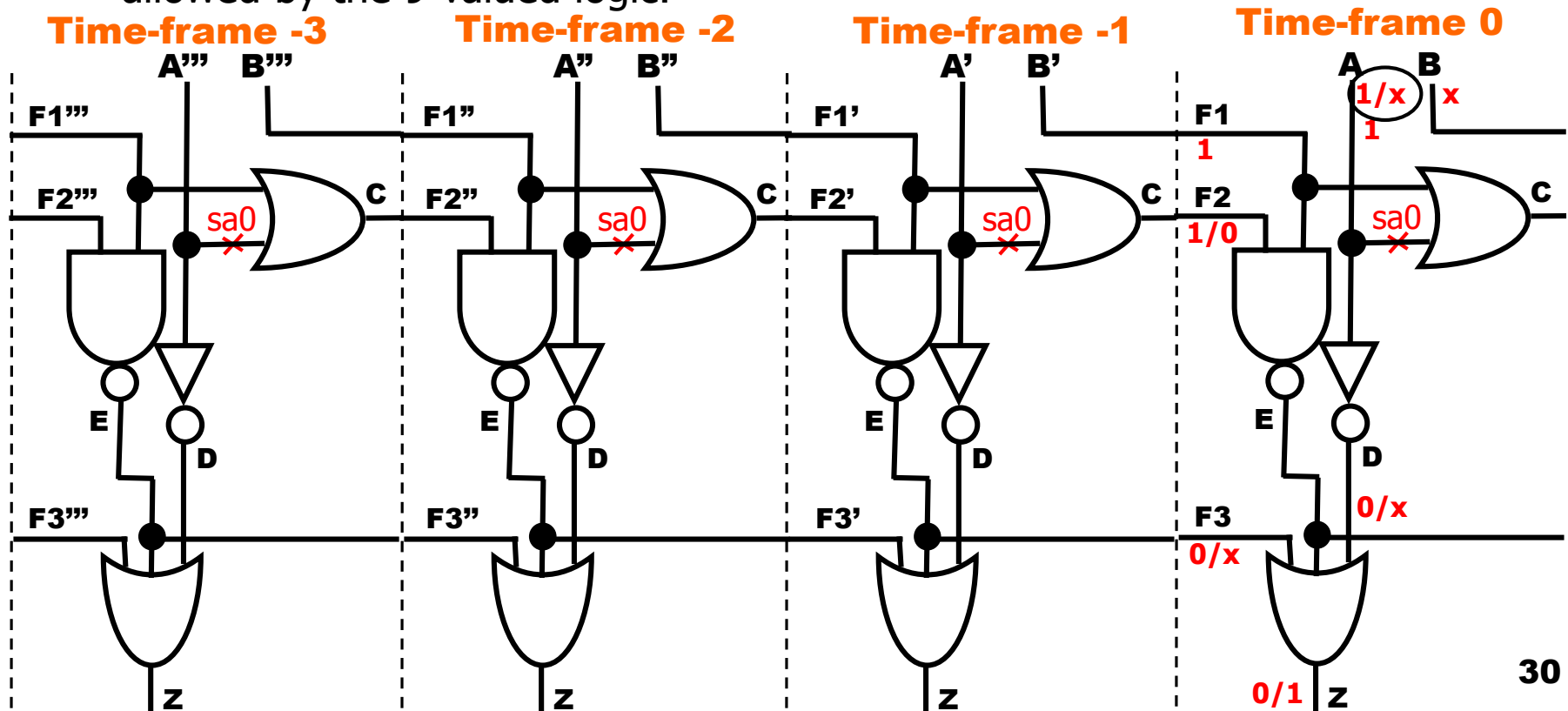
Example – Step 1

- In time-frame 0, we place a 0/1 at Z and justify it by $A=1$, $F1=1$, $F2=1/0$ and $F3=0/x$. Notice:
 - Fault effect propagation is attempted through $C \rightarrow F2 \rightarrow E \rightarrow Z$
 - $F3$ is set to 0/x (and not to 0) because all paths are simultaneously activated.
 - $F3$ is set to 0/x (and not to 0/1) because it is the least restrictive condition allowed by the 9-valued logic.



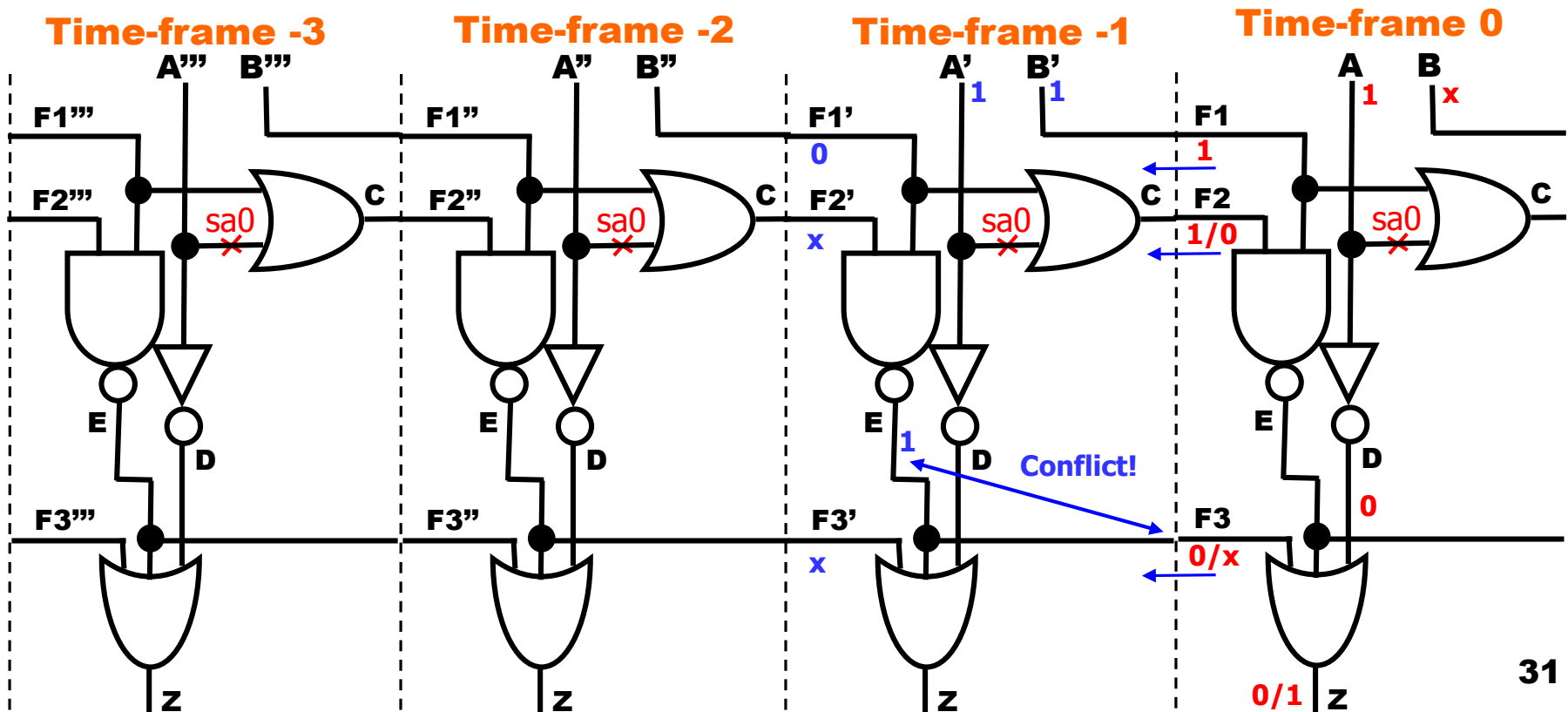
Example – Step 2

- We move to time-frame -1 to justify $F1=1$, $F2=1/0$ and $F3=0/x$. Setting $A'=1$, $B'=1$, $F1'=0$, $F2'=x$ and $F3'=x$ as inputs meets the first two requirements but causes a conflict on $F3$.
— So, backtrack to time-frame 0.



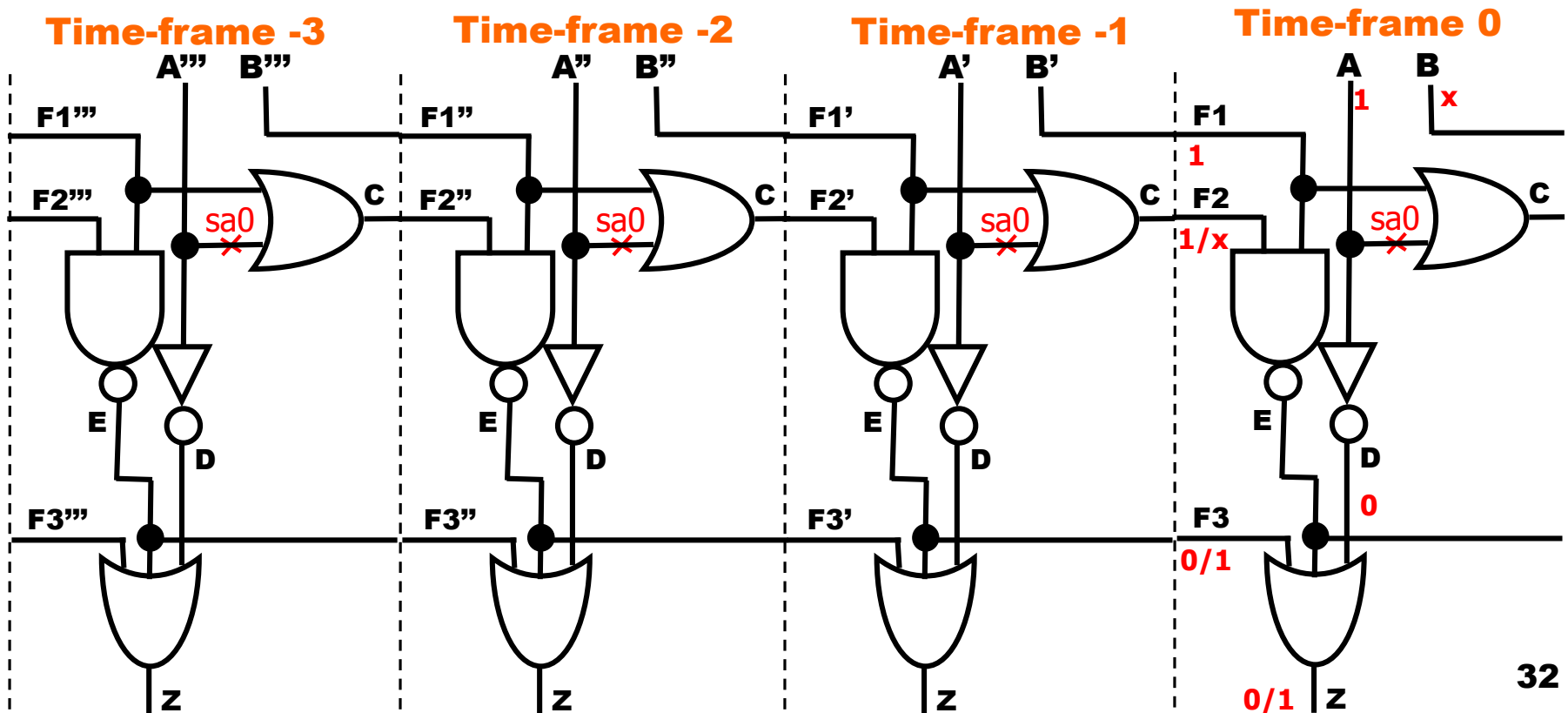
Example – Step 3

- The two path objectives are reversed. $Z=0/1$ is obtained by $F2=1/x$ and $F3=0/1$.
- Fault effect propagation is attempted through $C \rightarrow F2 \rightarrow E \rightarrow F3 \rightarrow Z$



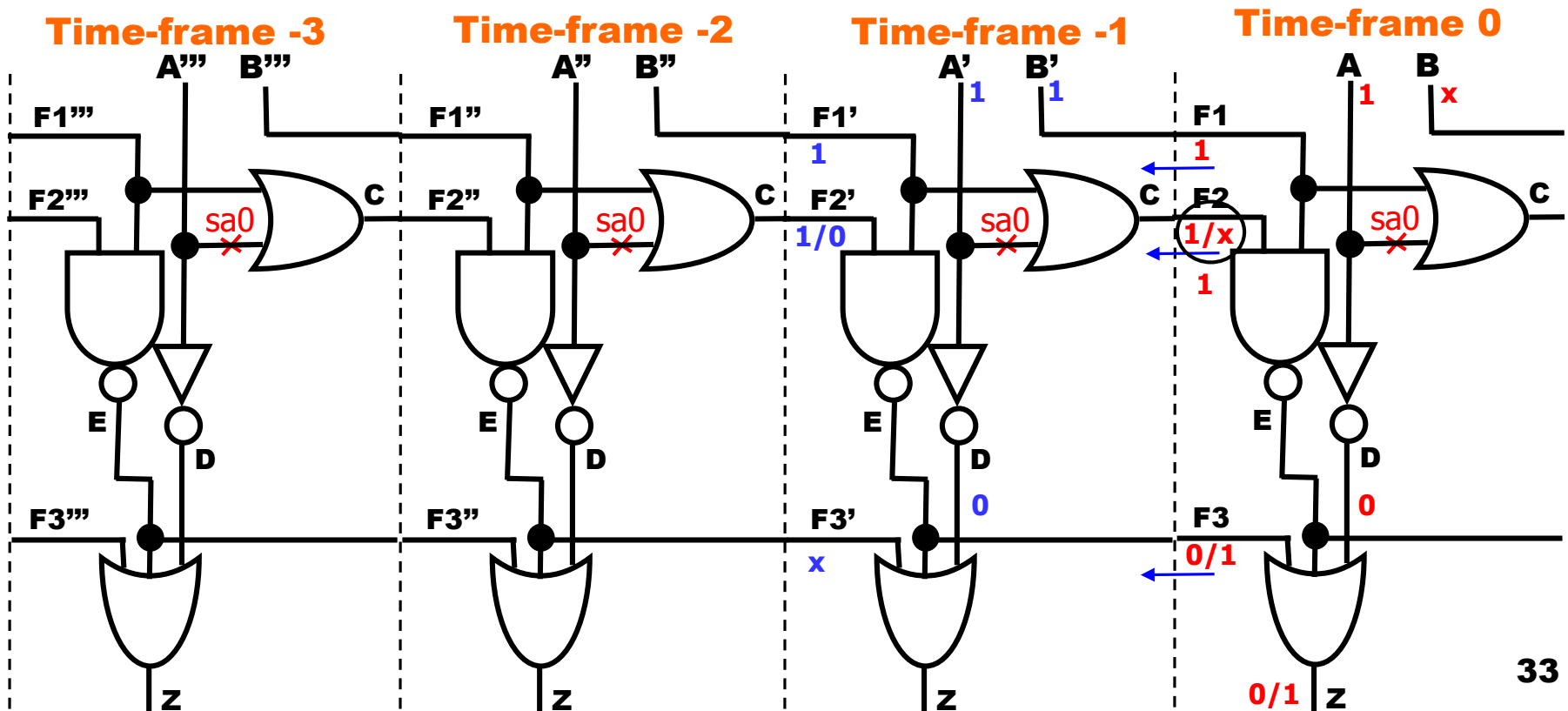
Example – Step 4

- In time-frame -1, we justify $F1=1$, $F2=1/x$ and $F3=0/1$, by $A'=1$, $B'=1$, $F1'=1$, $F2'=1/0$ and $F3'=x$. This changes $F2$ to 1 but that is not a conflict with $1/x$.



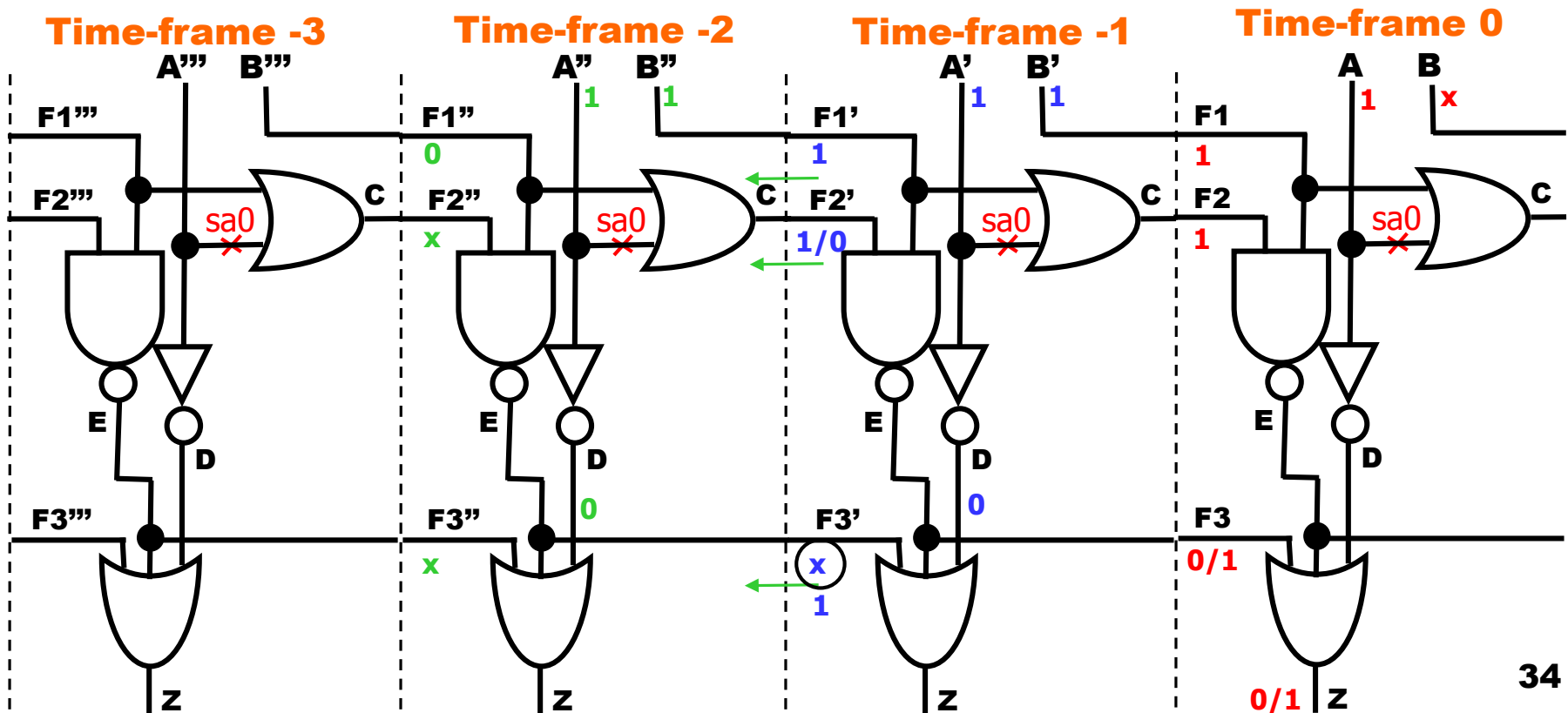Example – Step 5

- In time-frame -2, we justify $F1'=1$, $F2'=1/0$ and $F3'=1$, by $A''=1$, $B''=1$, $F1''=0$, $F2''=x$ and $F3''=x$.



Example – Step 6

- In time-frame -3, we justify $F1''=0$, $F2''=F3''=x$, by $A'''=x$, $B'''=0$.
 — Thus, a 4-vector test is found: $(AB)=\{(x0),(11),(11),(1x)\}$ which produces a 0/1 output on the last vector.
- A full test generation produces 17 vectors for detecting all 21 single s-a-f's in the combinational logic of this circuit.

