

---

# EEDG/CE 6303: Testing and Testable Design

*Mehrdad Nourani*


**Dept. of ECE  
Univ. of Texas at Dallas**

---

## Session 03

# **Test Generation for Combinational Circuits**

# Fault Analysis System (Review)

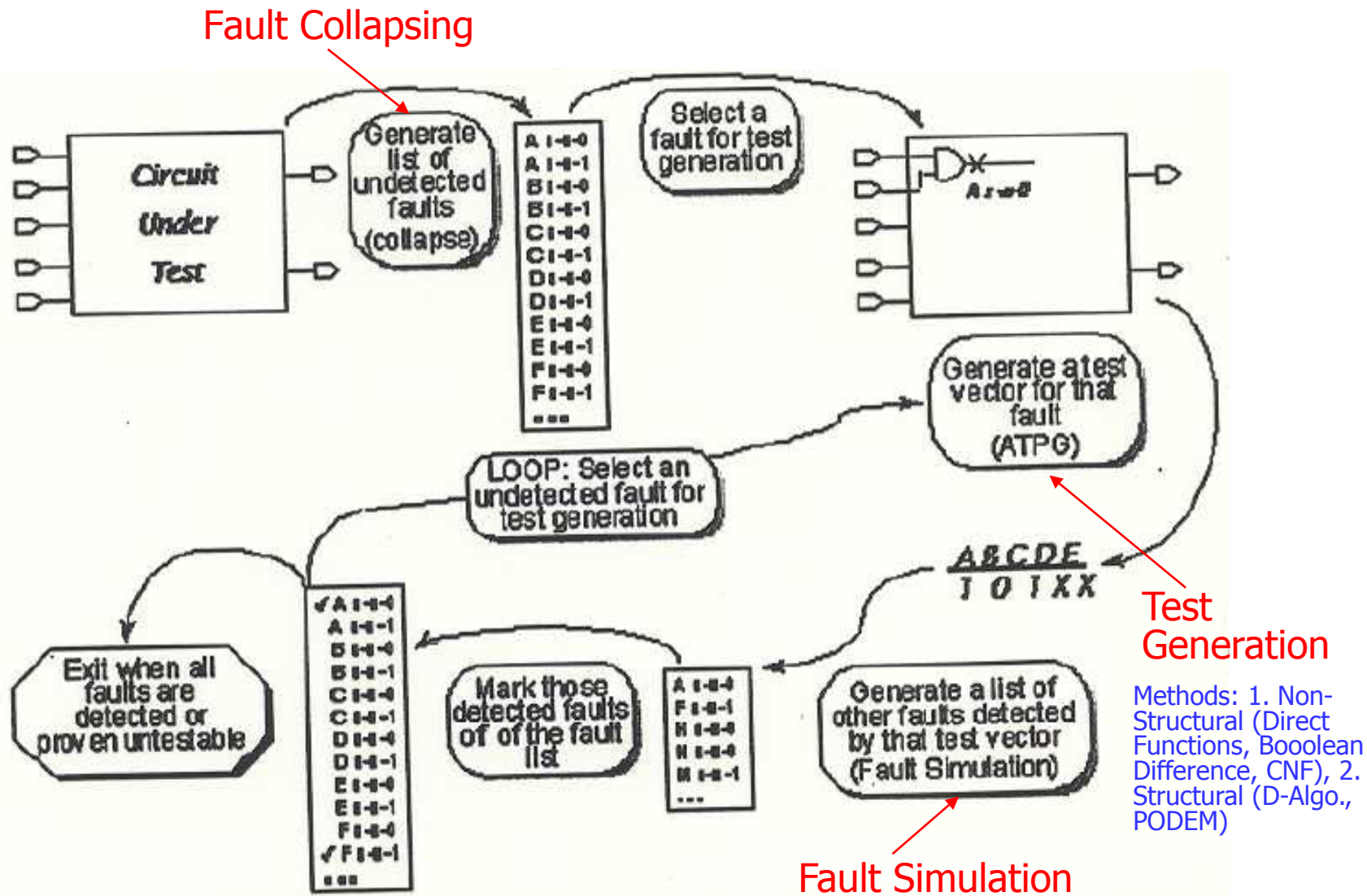

# Test Generation Techniques

---

- There are two main test vector generation techniques
  1. Non-Structural (Analytical)
    - Analyzes the gate-level description of a circuit and implicitly enumerate all possible input combinations to find a test vector for a target fault.
    - Methods: (i) Direct Function, (ii) Boolean Difference, (iii) CNF (product-of-sum form), ...
  2. Structural
    - Analyzes the structure of a given circuit to generate a test vector for a given target fault, or declare it untestable.
    - Methods: (i) D-Algorithm, (ii) PODEM, ...

---

# **Structural Test Generation**


# Structural Test Generation

---

- **Analyzes the structure** of a given circuit to generate a test vector for a given target fault, or declare it untestable.
  - Methods: (i) **D-Algorithm**, (ii) PODEM, ...

# Motivation

- Consider a 64-bit ripple-carry adder

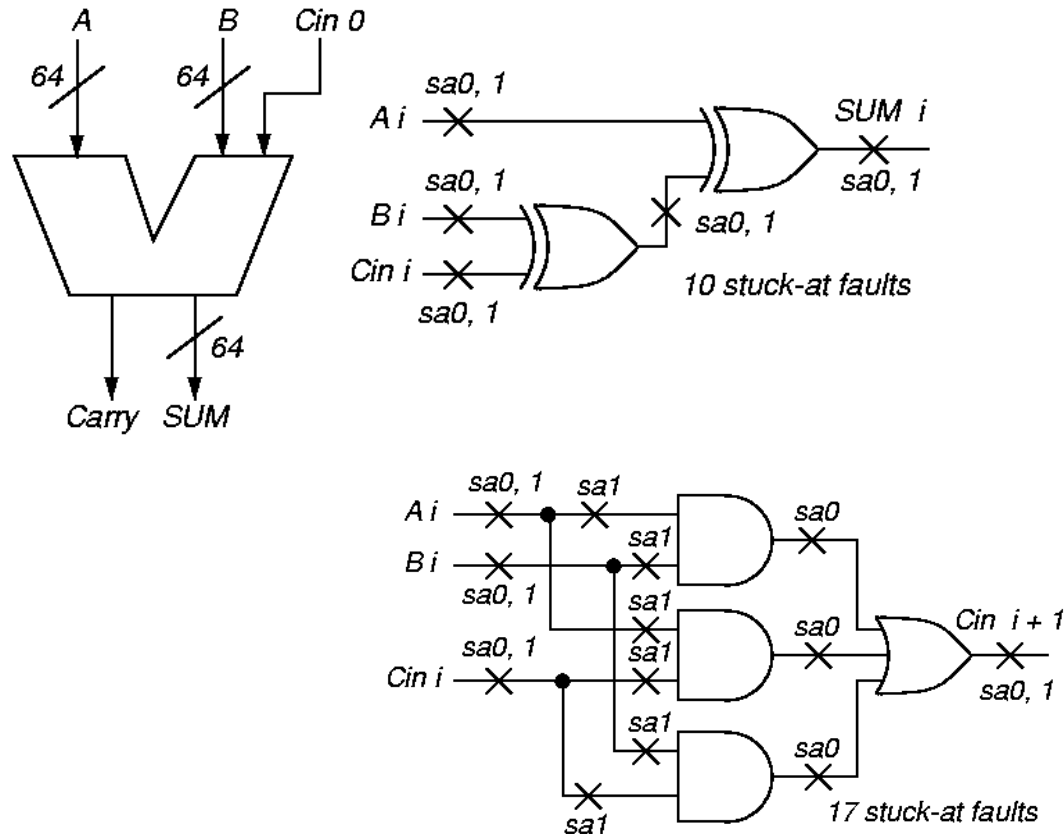

## Motivation (cont.)

---

- Functional (exhaustive) ATPG – generate complete set of tests for circuit input-output combinations
  - 129 inputs, 65 outputs:
  - $2^{129} = 680,564,733,841,876,926,926,749,214,863,536,422,912$  patterns
  - Using 1 GHz ATE, would take  $2.15 \times 10^{22}$  years
- Structural test:
  - No redundant adder hardware, 64 bit slices
  - Each with 27 faults (using fault equivalence)
  - At most  $64 \times 27 = 1728$  faults (tests)
  - Takes  $0.000001728$  s on 1 GHz ATE
- Designer gives small set of functional tests – augment with structural tests to boost coverage to 98+ %




# Algebra for Structural Test

---

- Represent two machines, which are simulated simultaneously by a computer program:
  - Good circuit machine (1<sup>st</sup> value)
  - Bad circuit machine (2<sup>nd</sup> value)
- Better to represent both in the algebra:
  - Need only 1 pass of ATPG to solve both
  - Good machine values that preclude bad machine values become obvious sooner & vice versa
 
# Circuit Representation

- It's more efficient to carry (simulate) fault-free and faulty values at the same time.



# Algebra for Structural Test (cont.)

- Roth's 5-Valued and Muth's 9-Valued Algebra

Symbol	Meaning	Fault-Free (Good)	Faulty (Bad)
0	0/0	0	0
1	1/1	1	1
D	1/0	1	0
$\overline{D}$	0/1	0	1
X	X/X	X	X
G0	0/X	0	X
G1	1/X	1	X
F0	X/0	X	0
F1	X/1	X	1

5-Valued

9-Valued

# Operations in Multi-Valued Logic

- Examples (2-input AND and OR gates)

AND	0	1	$D$	$\bar{D}$	$x$
0	0	0	0	0	0
1	0	1	$D$	$\bar{D}$	$x$
$D$	0	$D$	$D$	0	$x$
$\bar{D}$	0	$\bar{D}$	0	$\bar{D}$	$x$
$x$	0	$x$	$x$	$x$	$x$



OR	0	1	$D$	$\bar{D}$	$x$
0	0	1	$D$	$\bar{D}$	$x$
1	1	1	1	1	1
$D$	$D$	1	$D$	1	$x$
$\bar{D}$	$\bar{D}$	1	1	$\bar{D}$	$x$
$x$	$x$	1	$x$	$x$	$x$

- e.g.  $D+0=1/0+0/0=1/0=D$

# Path Sensitization

- Three key tasks are needed
  1. Fault Sensitization (Stimulation)
  2. Fault (Effect) Propagation
  3. Line Justification
- Forward and Backward Implications


Examples of  
Forward  
Implications

  

Examples of Backward  
Implications

 
# Path Sensitization Example

- Propagate through **top path**.
- Using **5-valued** logic


 
## Path Sensitization Example (cont.)


- Propagate through **top and bottom** paths simultaneously
- Using **5-valued** logic



## Path Sensitization Example (cont.)

- Propagate through the **bottom path**
- Using **5-valued logic**


**Test Pattern Found**

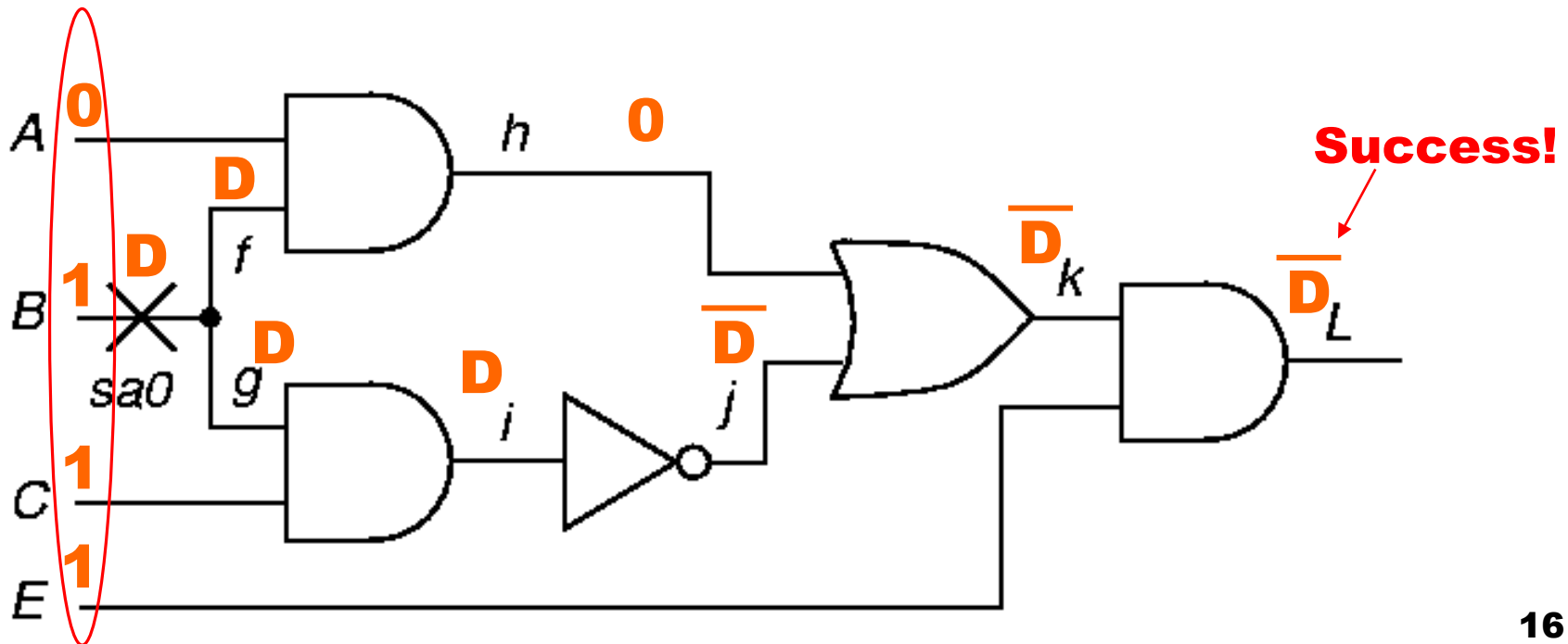




# Path Sensitization Example (9-Valued Logic)

- Trying **top** path:

 


- Trying **bottom** path:

**Test Pattern Found**

 


## Path Sensitization – Example 2

- Top path does not work

 

 - Bottom path does not work either (circuit is symmetrical)
- Both paths together can test the fault



# History of Algorithms

---

Algorithm	Est. speedup over D-ALG (normalized to D-ALG time)	Year
<b>D-ALG</b>	<b>1</b>	<b>1966</b>
<b>PODEM</b>	<b>7</b>	<b>1981</b>
<b>FAN</b>	<b>23</b>	<b>1983</b>
<b>TOPS</b>	<b>292</b>	<b>1987</b>
<b>SOCRATES</b>	<b>1574 † ATPG System</b>	<b>1988</b>
<b>Waicukauski et al.</b>	<b>2189 † ATPG System</b>	<b>1990</b>
<b>EST</b>	<b>8765 † ATPG System</b>	<b>1991</b>
<b>TRAN</b>	<b>3005 † ATPG System</b>	<b>1993</b>
<b>Recursive learning</b>	<b>485</b>	<b>1995</b>
<b>Tafertshofer et al.</b>	<b>25057</b>	<b>1997</b>

# Symbols Used in Value Systems

- In the **five-valued system**

- Unique symbols –  $0_5$ ,  $1_5$ ,  $D_5$ , and  $\overline{D}_5$  – are assigned to each set denoting a completely-specified value
- One single symbol –  $X_5$  – denotes all sets with more than one basic value

16-valued	Symbols in other value systems		
	Five-valued	Six-valued	Nine-valued
$\{\}$	—	—	—
$\{0\}$	$0_5$	$0_6$	$0_9$
$\{1\}$	$1_5$	$1_6$	$1_9$
$\{D\}$	$D_5$	$D_6$	$D_9$
$\{\overline{D}\}$	$\overline{D}_5$	$\overline{D}_6$	$\overline{D}_9$
$\{0, 1\}$	$X_5$	$x_6$	$xx_9$
$\{0, D\}$	$X_5$	$X_6$	$x0_9$
$\{0, \overline{D}\}$	$X_5$	$X_6$	$0x_9$
$\{1, D\}$	$X_5$	$X_6$	$1x_9$
$\{1, \overline{D}\}$	$X_5$	$X_6$	$x1_9$
$\{D, \overline{D}\}$	$X_5$	$X_6$	$xx_9$
$\{0, 1, D\}$	$X_5$	$X_6$	$xx_9$
$\{0, 1, \overline{D}\}$	$X_5$	$X_6$	$xx_9$
$\{0, D, \overline{D}\}$	$X_5$	$X_6$	$xx_9$
$\{1, D, \overline{D}\}$	$X_5$	$X_6$	$xx_9$
$\{0, 1, D, \overline{D}\}$	$X_5$	$X_6$	$xx_9$

# Symbols Used in Value Systems (cont.)

- In the **six-valued system**
  - Unique symbols –  $0_6$ ,  $1_6$ ,  $D_6$ , and  $\overline{D}_6$  – are assigned to each set denoting a completely-specified value
  - One single symbol –  $\chi_6$  – denotes the set  $\{\underline{0}, \underline{1}\}$ , i.e., the only incompletely-specified set that does not contain  $D$  or  $\overline{D}$
  - One single symbol –  $x_6$  – denotes all sets with more than one basic value (including  $\{\underline{0}, \underline{1}\}$ )

16-valued	Symbols in other value systems		
	Five-valued	Six-valued	Nine-valued
$\{\}$	—	—	—
$\{\underline{0}\}$	$0_5$	$0_6$	$0_9$
$\{\underline{1}\}$	$1_5$	$1_6$	$1_9$
$\{D\}$	$D_5$	$D_6$	$D_9$
$\{\overline{D}\}$	$\overline{D}_5$	$\overline{D}_6$	$\overline{D}_9$
$\{\underline{0}, \underline{1}\}$	$X_5$	$\chi_6$	$xx_9$
$\{\underline{0}, D\}$	$X_5$	$X_6$	$x0_9$
$\{\underline{0}, \overline{D}\}$	$X_5$	$X_6$	$0x_9$
$\{\underline{1}, D\}$	$X_5$	$X_6$	$1x_9$
$\{\underline{1}, \overline{D}\}$	$X_5$	$X_6$	$x1_9$
$\{D, \overline{D}\}$	$X_5$	$X_6$	$xx_9$
$\{\underline{0}, \underline{1}, D\}$	$X_5$	$X_6$	$xx_9$
$\{\underline{0}, \underline{1}, \overline{D}\}$	$X_5$	$X_6$	$xx_9$
$\{\underline{0}, D, \overline{D}\}$	$X_5$	$X_6$	$xx_9$
$\{\underline{1}, D, \overline{D}\}$	$X_5$	$X_6$	$xx_9$
$\{\underline{0}, \underline{1}, D, \overline{D}\}$	$X_5$	$X_6$	$xx_9$

# Behavior of Gates Using Multi-Valued System

		$V(c_{i_2})$			
		<u>0</u>	<u>1</u>	$\overline{D}$	$\overline{D}$
$V(c_{i_1})$	<u>0</u>	<u>1</u>	<u>1</u>	<u>1</u>	<u>1</u>
	<u>1</u>	<u>1</u>	<u>0</u>	$\overline{D}$	$\overline{D}$
	$\overline{D}$	<u>1</u>	$\overline{D}$	$\overline{D}$	<u>1</u>
	$\overline{D}$	<u>1</u>	$\overline{D}$	<u>1</u>	$\overline{D}$

2-Input NAND

		$V(c_{i_2})$			
		<u>0</u>	<u>1</u>	$\overline{D}$	$\overline{D}$
$V(c_{i_1})$	<u>0</u>	<u>1</u>	<u>0</u>	$\overline{D}$	$\overline{D}$
	<u>1</u>	<u>0</u>	<u>0</u>	<u>0</u>	<u>0</u>
	$\overline{D}$	$\overline{D}$	<u>0</u>	$\overline{D}$	<u>0</u>
	$\overline{D}$	$\overline{D}$	<u>0</u>	<u>0</u>	$\overline{D}$

2-Input NOR

		$V(c_{i_2})$			
		<u>0</u>	<u>1</u>	$\overline{D}$	$\overline{D}$
$V(c_{i_1})$	<u>0</u>	<u>0</u>	<u>1</u>	$\overline{D}$	$\overline{D}$
	<u>1</u>	<u>1</u>	<u>0</u>	$\overline{D}$	$\overline{D}$
	$\overline{D}$	$\overline{D}$	$\overline{D}$	<u>0</u>	<u>1</u>
	$\overline{D}$	$\overline{D}$	$\overline{D}$	<u>1</u>	<u>0</u>

2-Input XOR

$V(c_i)$	$V(c_{j_1})$	$\dots$	$V(c_{j_l})$	$\dots$
<u>0</u>	<u>0</u>	$\dots$	<u>0</u>	$\dots$
<u>1</u>	<u>1</u>	$\dots$	<u>1</u>	$\dots$
$\overline{D}$	$\overline{D}$	$\dots$	$\overline{D}$	$\dots$
$\overline{D}$	$\overline{D}$	$\dots$	$\overline{D}$	$\dots$

A fanout system

# 6-Valued Cube Cover

- A **cube** represents a combination of inputs.
  - **singular cover:** cubes with  $0_6$  or  $1_6$  at output (i.e., no fault effect)
  - **propagation cubes:** cubes with  $D_6$  or  $\overline{D}_6$  at output
  - **cube cover:** together, all the cubes

$V(c_{i_1})$	$V(c_{i_2})$	$V(c_j)$
$0_6$	$X_6$	$1_6$
$X_6$	$0_6$	$1_6$
$D_6$	$\overline{D}_6$	$1_6$
$\overline{D}_6$	$D_6$	$1_6$
$1_6$	$1_6$	$0_6$
$\overline{D}_6$	$1_6$	$D_6$
$1_6$	$\overline{D}_6$	$D_6$
$\overline{D}_6$	$\overline{D}_6$	$D_6$
$D_6$	$1_6$	$\overline{D}_6$
$1_6$	$D_6$	$\overline{D}_6$
$D_6$	$D_6$	$\overline{D}_6$

2-Input NAND

# Fault Excitation Cubes

---

- For test generation for single stuck-at fault in a combinational circuit
  - Only fault-free values may appear at the inputs of faulty circuit element
  - It is necessary to apply a combination of values at the inputs of the faulty element that can cause a D or  $\overline{D}$  to appear at its outputs
  - **Fault excitation cubes** capture this aspect of a faulty circuit element



# Fault Excitation Cubes (cont.)

$V(c_{i_1})$	$V(c_{i_2})$	$V(c_j)$
$1_6$	$1_6$	$\overline{D}_6$

Two-input NAND with  
output SA1

$V(c_{i_1})$	$V(c_{i_2})$	$V(c_j)$
$0_6$	$x_6$	$D_6$
$x_6$	$0_6$	$D_6$

Two-input NAND with  
output SA0

$V(c_{i_1})$	$V(c_{i_2})$	$V(c_j)$
$0_6$	$1_6$	$D_6$

Two-input NAND with  
input  $c_{i_1}$  SA1

$V(c_i)$	$V(c_{j_1})$	$\dots$	$V(c_{j_l})$	$\dots$
$0_6$	$0_6$	$\dots$	$\overline{D}_6$	$\dots$

A fanout system with  
branch  $c_{j_l}$  SA1

$V(c_i)$	$V(c_{j_1})$	$\dots$	$V(c_{j_l})$	$\dots$
$0_6$	$\overline{D}_6$	$\dots$	$\overline{D}_6$	$\dots$

A fanout system with stem  
SA1

# More Cube Covers

NAND

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
0 <sub>6</sub>	X <sub>6</sub>	1 <sub>6</sub>
X <sub>6</sub>	0 <sub>6</sub>	1 <sub>6</sub>
D <sub>6</sub>	$\overline{D}_6$	1 <sub>6</sub>
$\overline{D}_6$	D <sub>6</sub>	1 <sub>6</sub>
1 <sub>6</sub>	1 <sub>6</sub>	0 <sub>6</sub>
$\overline{D}_6$	1 <sub>6</sub>	D <sub>6</sub>
1 <sub>6</sub>	$\overline{D}_6$	D <sub>6</sub>
$\overline{D}_6$	$\overline{D}_6$	D <sub>6</sub>
D <sub>6</sub>	1 <sub>6</sub>	$\overline{D}_6$
1 <sub>6</sub>	D <sub>6</sub>	$\overline{D}_6$
D <sub>6</sub>	D <sub>6</sub>	$\overline{D}_6$

AND

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
1 <sub>6</sub>	1 <sub>6</sub>	1 <sub>6</sub>
0 <sub>6</sub>	X <sub>6</sub>	0 <sub>6</sub>
X <sub>6</sub>	0 <sub>6</sub>	0 <sub>6</sub>
D <sub>6</sub>	$\overline{D}_6$	0 <sub>6</sub>
$\overline{D}_6$	D <sub>6</sub>	0 <sub>6</sub>
D <sub>6</sub>	1 <sub>6</sub>	D <sub>6</sub>
1 <sub>6</sub>	D <sub>6</sub>	D <sub>6</sub>
D <sub>6</sub>	D <sub>6</sub>	D <sub>6</sub>
$\overline{D}_6$	1 <sub>6</sub>	$\overline{D}_6$
1 <sub>6</sub>	$\overline{D}_6$	$\overline{D}_6$
$\overline{D}_6$	$\overline{D}_6$	$\overline{D}_6$

OR

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
1 <sub>6</sub>	X <sub>6</sub>	1 <sub>6</sub>
X <sub>6</sub>	1 <sub>6</sub>	1 <sub>6</sub>
D <sub>6</sub>	$\overline{D}_6$	1 <sub>6</sub>
$\overline{D}_6$	D <sub>6</sub>	1 <sub>6</sub>
0 <sub>6</sub>	0 <sub>6</sub>	0 <sub>6</sub>
D <sub>6</sub>	0 <sub>6</sub>	D <sub>6</sub>
0 <sub>6</sub>	D <sub>6</sub>	D <sub>6</sub>
D <sub>6</sub>	D <sub>6</sub>	D <sub>6</sub>
$\overline{D}_6$	0 <sub>6</sub>	$\overline{D}_6$
0 <sub>6</sub>	$\overline{D}_6$	$\overline{D}_6$
$\overline{D}_6$	$\overline{D}_6$	$\overline{D}_6$

XOR

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
1 <sub>6</sub>	0 <sub>6</sub>	1 <sub>6</sub>
0 <sub>6</sub>	1 <sub>6</sub>	1 <sub>6</sub>
D <sub>6</sub>	$\overline{D}_6$	1 <sub>6</sub>
$\overline{D}_6$	D <sub>6</sub>	1 <sub>6</sub>
0 <sub>6</sub>	0 <sub>6</sub>	0 <sub>6</sub>
1 <sub>6</sub>	1 <sub>6</sub>	0 <sub>6</sub>
D <sub>6</sub>	D <sub>6</sub>	0 <sub>6</sub>
$\overline{D}_6$	$\overline{D}_6$	0 <sub>6</sub>
0 <sub>6</sub>	D <sub>6</sub>	D <sub>6</sub>
D <sub>6</sub>	0 <sub>6</sub>	D <sub>6</sub>
1 <sub>6</sub>	$\overline{D}_6$	D <sub>6</sub>
$\overline{D}_6$	1 <sub>6</sub>	D <sub>6</sub>
1 <sub>6</sub>	D <sub>6</sub>	$\overline{D}_6$
D <sub>6</sub>	1 <sub>6</sub>	$\overline{D}_6$
0 <sub>6</sub>	$\overline{D}_6$	$\overline{D}_6$
$\overline{D}_6$	0 <sub>6</sub>	$\overline{D}_6$

Fanout System

$V(c_i)$	$V(c_{j1})$	...	$V(c_{j1})$	...
1 <sub>6</sub>	1 <sub>6</sub>	...	1 <sub>6</sub>	...
0 <sub>6</sub>	0 <sub>6</sub>	...	0 <sub>6</sub>	...
D <sub>6</sub>	D <sub>6</sub>	...	D <sub>6</sub>	...
$\overline{D}_6$	$\overline{D}_6$	...	$\overline{D}_6$	...

# More Fault Excitation Cubes

## 2-Input NAND

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
1 <sub>6</sub>	1 <sub>6</sub>	$\overline{D}_6$

output SA1

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
0 <sub>6</sub>	1 <sub>6</sub>	$D_6$
1 <sub>6</sub>	0 <sub>6</sub>	$D_6$

output SA0

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
0 <sub>6</sub>	1 <sub>6</sub>	$D_6$

input  $c_{i1}$  SA1

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
1 <sub>6</sub>	1 <sub>6</sub>	$\overline{D}_6$

input  $c_{i1}$  SA0

## 2-Input XOR

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
0 <sub>6</sub>	0 <sub>6</sub>	$\overline{D}_6$
1 <sub>6</sub>	1 <sub>6</sub>	$\overline{D}_6$

output SA1

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
0 <sub>6</sub>	1 <sub>6</sub>	$D_6$
1 <sub>6</sub>	0 <sub>6</sub>	$D_6$

output SA0

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
0 <sub>6</sub>	1 <sub>6</sub>	$D_6$
0 <sub>6</sub>	0 <sub>6</sub>	$\overline{D}_6$

input  $c_{i1}$  SA1

$V(c_{i1})$	$V(c_{i2})$	$V(c_j)$
1 <sub>6</sub>	0 <sub>6</sub>	$D_6$
1 <sub>6</sub>	1 <sub>6</sub>	$\overline{D}_6$

input  $c_{i1}$  SA0

## Fanout System

$V(c_i)$	$V(c_{j1})$	...	$V(c_{jn})$	...
0 <sub>6</sub>	0 <sub>6</sub>	...	$\overline{D}_6$	...

branch  $c_{ji}$  SA1

$V(c_i)$	$V(c_{j1})$	...	$V(c_{jn})$	...
1 <sub>6</sub>	1 <sub>6</sub>	...	$D_6$	...

branch  $c_{ji}$  SA0

$V(c_i)$	$V(c_{j1})$	...	$V(c_{jn})$	...
0 <sub>6</sub>	$\overline{D}_6$	...	$\overline{D}_6$	...

stem  $c_i$  SA1

$V(c_i)$	$V(c_{j1})$	...	$V(c_{jn})$	...
1 <sub>6</sub>	$D_6$	...	$D_6$	...

stem  $c_i$  SA0


# Test Generation Basics

---

- **Fault effect excitation (FEE)** is the process of creating a fault effect ( $D$  or  $\overline{D}$ ) at one or more outputs of the faulty circuit element
- **Fault effect propagation (FEP)** is the process of assigning values to circuit lines such that a fault-effect propagates from an output of the faulty circuit element to a primary output
  - One or more paths must exist between the fault site and a primary output, such that every line along the path has  $D_6$  or  $\overline{D}_6$
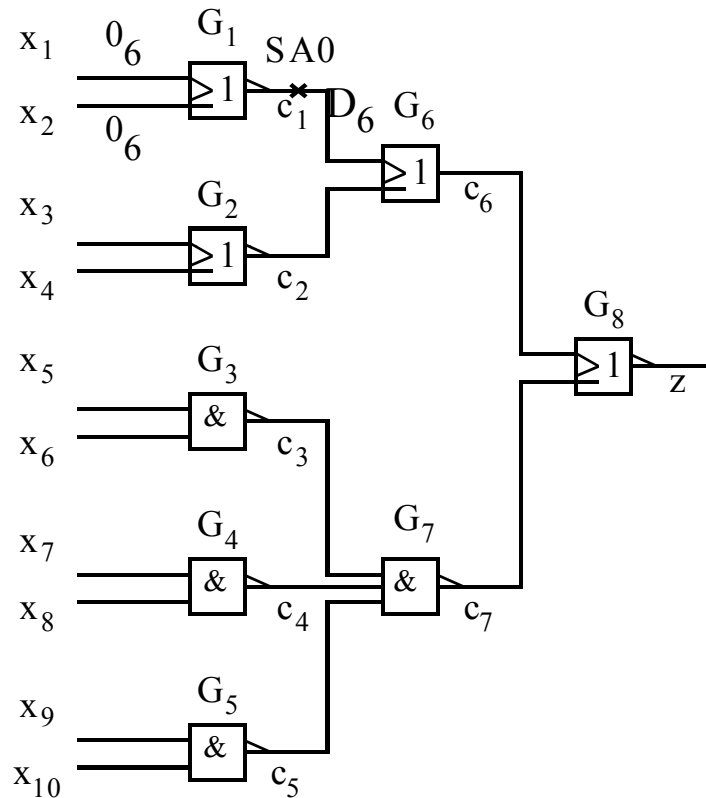
# Test Generation Example

- In our example, only a single path  $c_1c_6z$  exists for such propagation, i.e., FEP via  $G_6$  and  $G_8$  necessary




Fault excitation cube for  $G_1$

$V(x_1)$	$V(x_2)$	$V(c_1)$
$0_6$	$0_6$	$D_6$
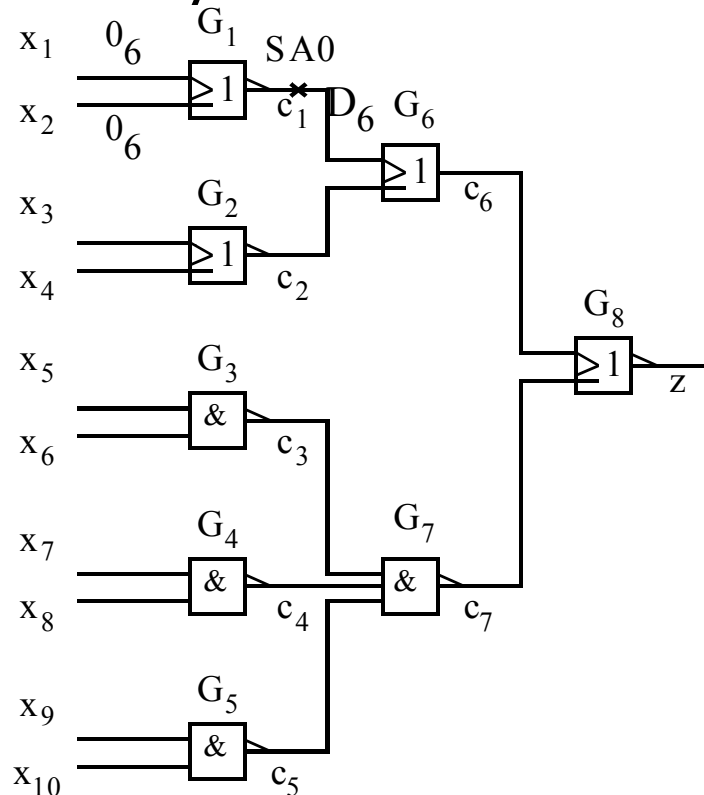
# Test Generation Example (cont.)

- To propagate via  $G_6$ , first use propagation cubes for  $G_6$
  - Next, eliminate rows incompatible with currently assigned values
  - Make one of the remaining assignments
- Only one remained in this case




Propagation cubes for  $G_6$

$V(c_1)$	$V(c_2)$	$V(c_6)$
$D_6$	$0_6$	$D_6$

# Test Generation Example (cont.)

- Similarly, propagate via  $G_8$

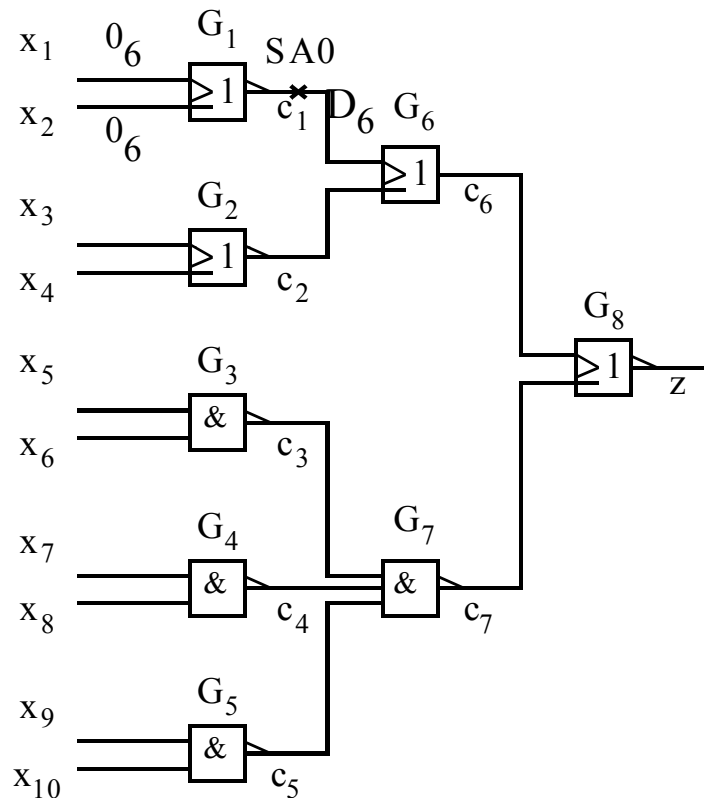


Propagation cubes for  $G_8$

$V(c_6)$	$V(c_7)$	$V(z)$
$D_6$	$0_6$	$\overline{D_6}$
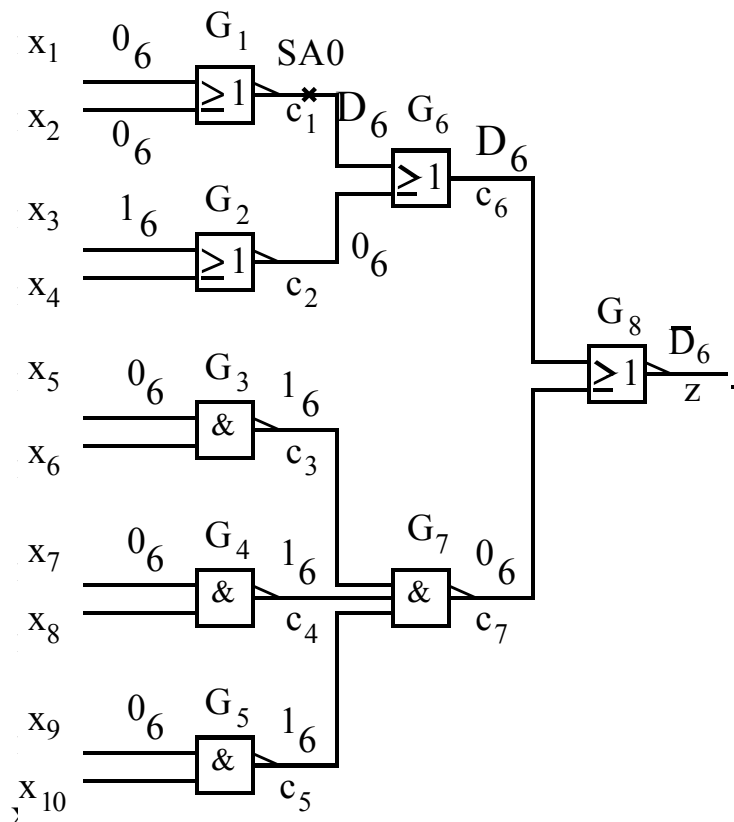
# Test Generation Example (cont.)

- **Justification** is the task of assigning values to primary inputs so as to imply a desired value at an internal line
  - Values at  $c_2$  and  $c_7$  are **not** justified




Singular cover of  $G_2$

$V(x_3)$	$V(x_4)$	$V(c_2)$
$1_6$	$X_6$	$0_6$
$X_6$	$1_6$	$0_6$


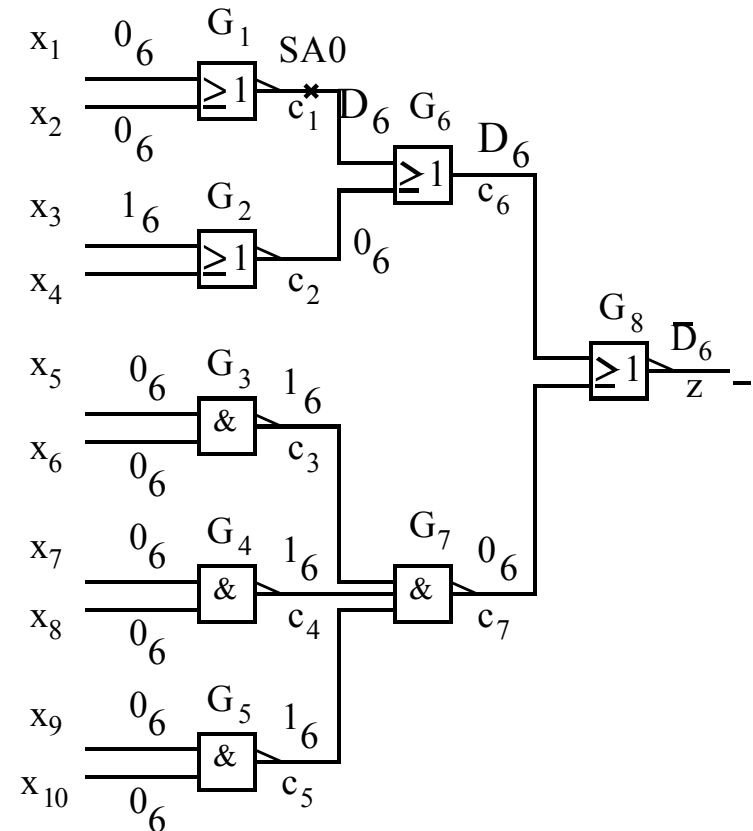
# Test Generation Example (cont.)

- **Justification** is the task of assigning values to primary inputs so as to imply a desired value at an internal line
  - Values at  $c_2$  and  $c_7$  are **not** justified
  - Justify value at  $c_2$ 
    - Identify all cubes in singular cover of  $G_2$
    - Eliminate cubes not consistent with currently applied values
      - + Two choices remain
        - Either  $1_6$  at  $x_3$
        - Or  $1_6$  at  $x_4$
      - + In this **fanout-free circuit** use either one
    - Similarly, justify value at  $c_7$




Singular cover of  $G_2$

$V(x_3)$	$V(x_4)$	$V(c_2)$
$1_6$	$X_6$	$0_6$
$X_6$	$1_6$	$0_6$
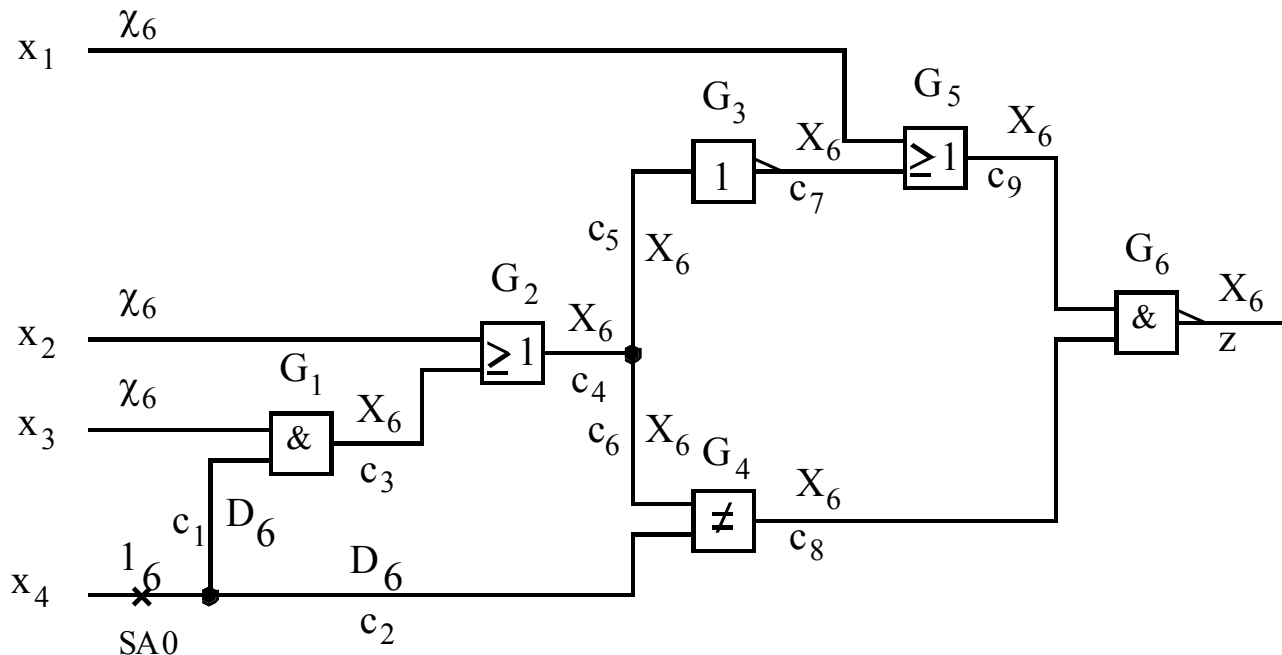
# Test Generation Example (cont.)

- Consider a circuit with fanouts for a more general case
  - Initialization: All lines in fanout of fault site  $x_6$ , other lines  $\chi_6$
  - Fault-effect excitation
  - $G_1$  and  $G_4$  as possible sites for FEP
    - D-frontier** is a set of gates where each gate has
      - $D_6$  or  $\overline{D}_6$  at one or more inputs, and
      - $x_6$  at output
    - Each gate in D-frontier is a candidate for FEP
    - Here,  $D = \{G_1, G_4\}$




Fault excitation cubes for fanout system with stem  $x_4$  with SA0 at  $x_4$

$V(x_4)$	$V(c_1)$	$V(c_2)$
1 <sub>6</sub>	$D_6$	$D_6$
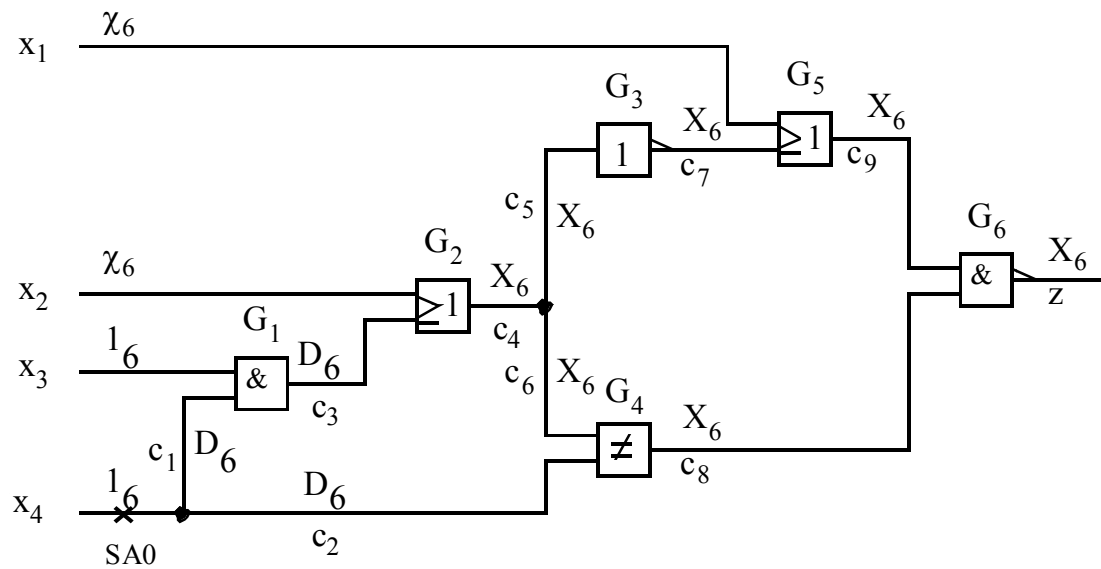
# Test Generation Example (cont.)

- Since  $D = \{G_1, G_4\}$  has more than one gate
  - Select, only say,  $G_1$  for FEP
  - Perform FEP via  $G_1$ 
    - Assign  $1_6$  at  $x_3$
  - Now the D-frontier  $D = \{G_2, G_4\}$




Propagation cubes for  $G_1$

$V(x_3)$	$V(c_1)$	$V(c_3)$
$1_6$	$D_6$	$D_6$
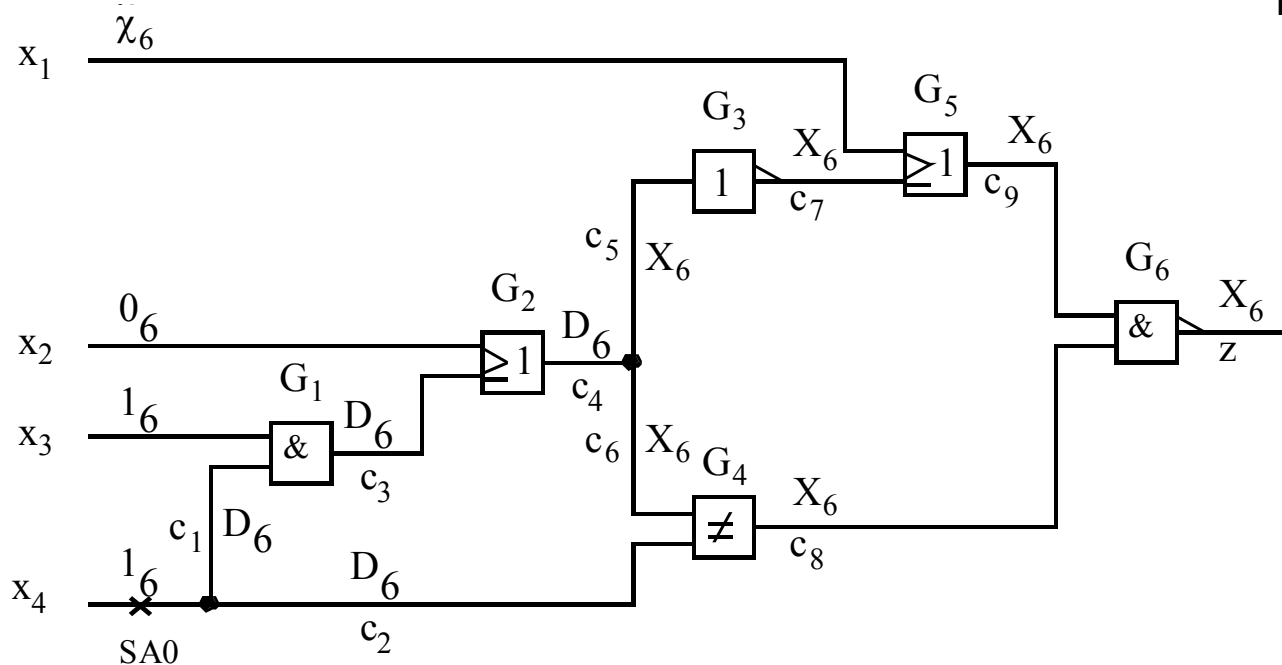
# Test Generation Example (cont.)

- Since  $D = \{G_2, G_4\}$ 
  - Select one, say  $G_2$
  - FEP via  $G_2$ 
    - Assign  $0_6$  to  $x_2$



Propagation cubes for  $G_2$

$x_2$	$c_3$	$c_4$
$0_6$	$D_6$	$D_6$

# Test Generation Example (cont.)

- Implications of currently assigned values
  - Only when a unique value can be identified

Relevant parts of cube covers of:

Fanout system with stem  $c_4$

$V(c_4)$	$V(c_5)$	$V(c_6)$
$D_6$	$D_6$	$D_6$

NOT gate  $G_3$

$V(c_5)$	$V(c_7)$
$D_6$	$\bar{D}_6$

XOR gate  $G_4$


$V(c_2)$	$V(c_6)$	$V(c_8)$
$D_6$	$D_6$	$0_6$

OR gate  $G_5$

$V(x_1)$	$V(c_7)$	$V(c_9)$
$1_6$	$X_6$	$1_6$
$0_6$	$D_6$	$D_6$

NAND gate  $G_6$

$V(c_8)$	$V(c_9)$	$V(z)$
$0_6$	$X_6$	$1_6$

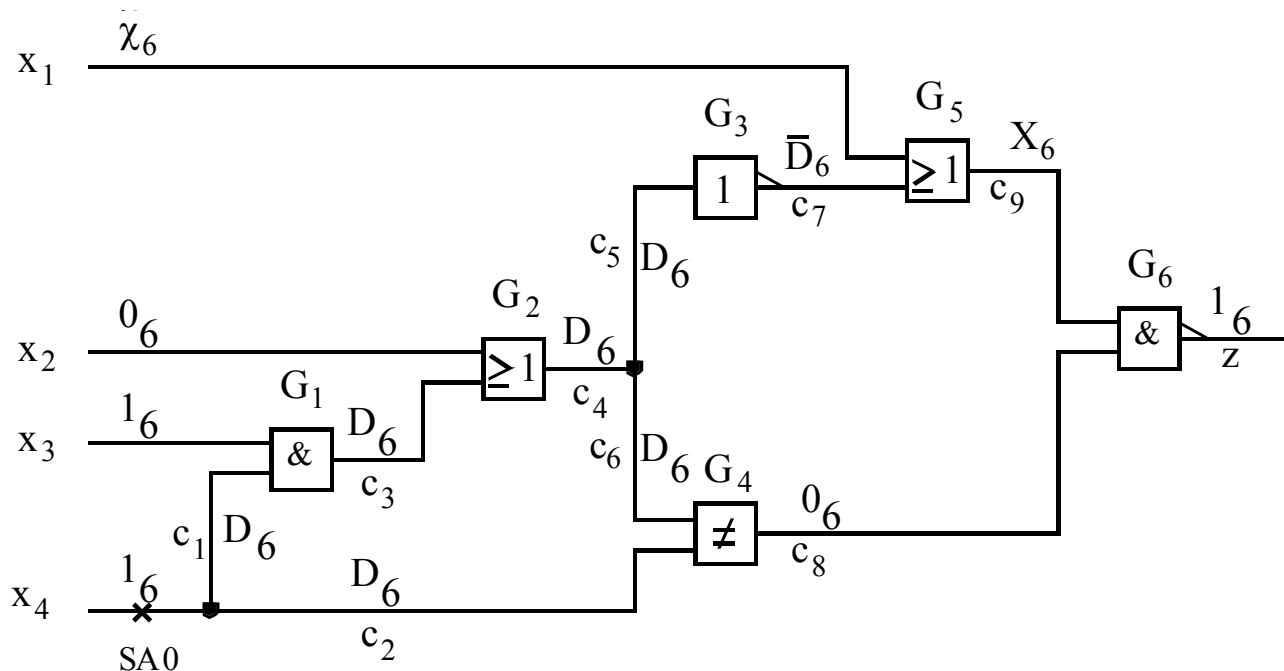


# Test Generation Example (cont.)

---

- Current status
  - $D = \{G_5\}$
  - But  $V(z) = 1_6$ , i.e., no possibility of obtaining  $D_6$  or  $\overline{D}_6$  at output
  - In other words, proceeding further will **not** lead to a test vector
  - Hence we must **backtrack**, i.e.,
    - Identify the most recent primary input value assignment for which an untried alternative exists
      - + Restore the state to prior to that assignment was made
      - + Make the alternative value assignment

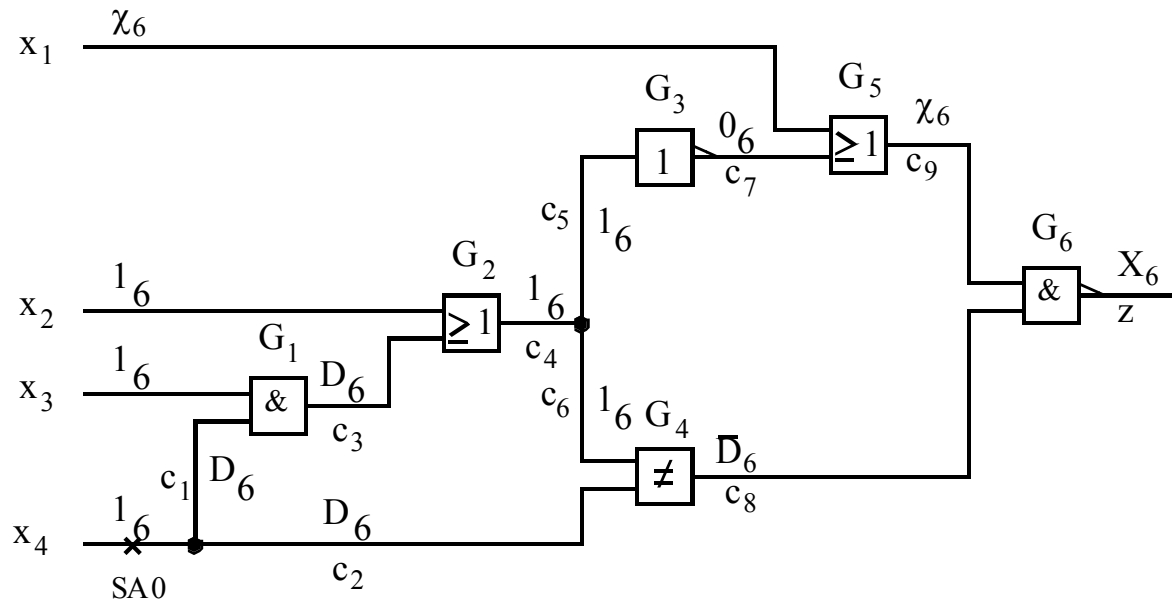
# Test generation basics

- Identifying the most recent primary input value assignment for which an untried alternative exists
  - During assignment of  $0_6$  to  $x_2$ , alternative  $1_6$  at  $x_2$  untried
- Executing backtrack
  - Restore circuit values to before  $0_6$  was assigned to  $x_2$
  - Assign  $1_6$  at  $x_2$  (no more alternatives exist)
  - Perform implication


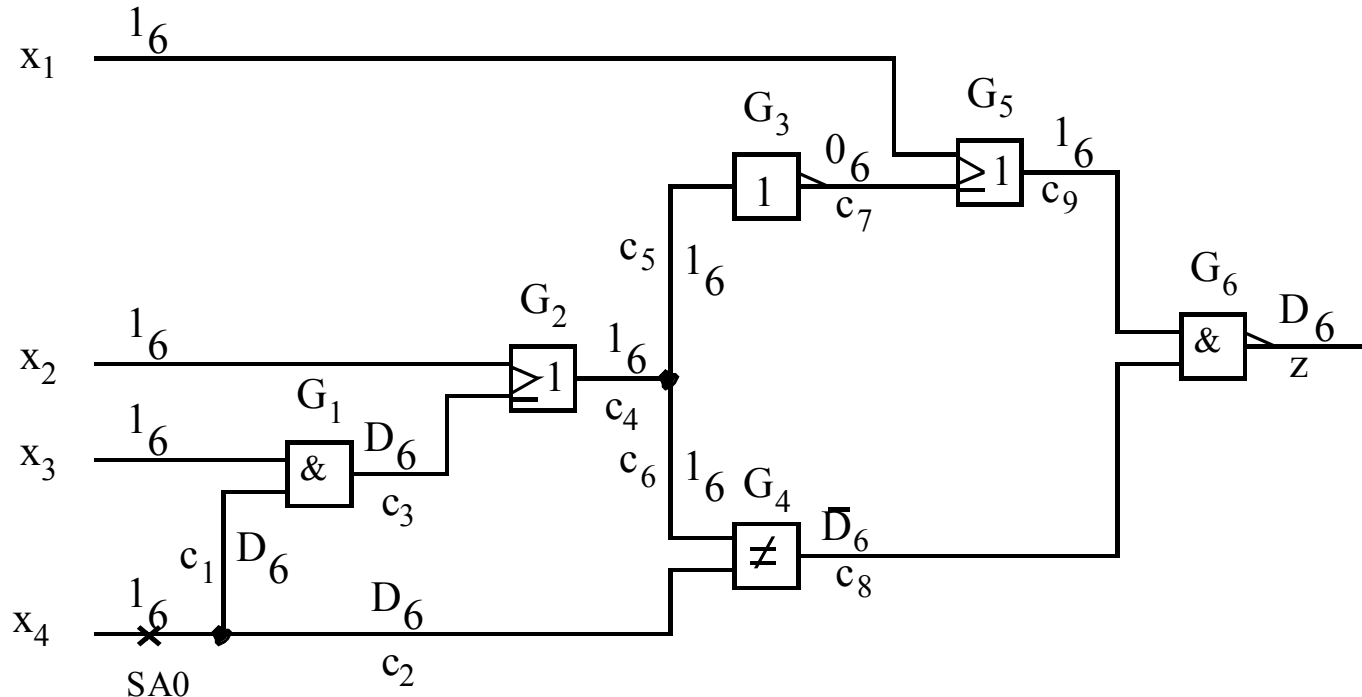
# Test Generation Example (cont.)

- Now  $D = \{G_6\}$ 
  - Select  $G_6$  for FEP
    - Objective  $1_6$  at  $c_9$ , which can be attained by  $1_6$  at  $x_1$ 
      - + Assign  $1_6$  at  $x_1$
    - Perform implication





## Test Generation Example (cont.)

---

- Now  $D_6$  at output and no unjustified lines
  - Hence test generation complete with vector  $(1_6, 1_6, 1_6, 1_6)$
  - In reality, need to apply only the value corresponding to fault-free circuit in each of above composite values
    - That is, apply test  $(1, 1, 1, 1)$

# Importance of Implication

---

- **Implication** is the process of determining logic values that appear at circuit lines as a consequence of the values assigned to some of its lines
- It also
  - Identifies any inconsistency between the values assigned
  - Updates D-frontier and list of unjustified lines
- An **implication procedure** iteratively uses **implication operation**
  - A **direct implication** operation determines values at inputs or outputs of a circuit element, given values assigned at the element's inputs and/or outputs
    - **Forward** implication operation proceeds from lines to those in its fanout
    - **Backward** implication proceeds from lines to those in fanin

# Generic Test Generation Algorithm

---

1. Read the circuit under test (CUT)
2. Preprocessing
  - a. Identify static indirect implications
  - b. Compute testability metrics
3. For each target fault in the fault list
  - a. Insert the target fault by using the appropriate description of the behavior of the faulty element
  - b. Initialize circuit lines
    - In five-valued system, assign  $x_5$  to all lines
    - In six-valued system, assign  $x_6$  to all lines in transitive fanout of fault site and  $\chi_6$  to all other lines
    - In sixteen-valued system
      - + Assign  $\{\underline{0}, \underline{1}, D, \overline{D}\}$  to all lines in transitive fanout of the fault site
      - + Assign  $\{\underline{0}, \underline{1}\}$  to all the other lines
      - + Perform forward implication starting at each output of the faulty circuit element

## Generic Test Generation Algorithm (cont.)

---

- c. Identify test generation sub-tasks (TGSTs)
  - Analyze values at primary outputs of CUT and outputs of the faulty circuit element
  - Analyze gates in the D-frontier D
  - Analyze the set of unjustified lines U
  - Determine, whether
    - + Test generation is complete – print vector, manage fault list, go to Step 3 and process next fault
    - + Conflict, i.e., not possible to generate a vector for target by further specifying currently assigned vector (values) – initiate **backtrack**
    - + Continue search by carrying out a TGST
      1. FEE – fault-effect excitation,
      2. FEP – fault-effect propagation, or
      3. Justification
- d. Identify a value assignment to accomplish the selected TGST
- e. Assign selected value
  - Save the state of the test generation: e.g., values at circuit lines, untried alternatives TGSTs and/or value assignments
  - Assign selected value
  - Perform implications
    - + If successful, continue
    - + Else, backtrack

# Identification of TGSTs

---

- Backtrack
  - Find the most recent value assignment at which an untried alternative existed
  - Restore the state of the test generation algorithm to prior to that value assignment
  - Make an alternative TGST/value assignment and try it, starting at Step 3d or 3e
- Assignment of each logic value by test generator followed by implication that
  - Either returns CONFLICT and initiates backtrack
  - Else, returns SUCCESS after updating
    - Values at circuit lines
    - D-frontier D
    - List of unjustified lines U
- Subsequently, values at circuit lines, D, and U are analyzed to identify TGSTs with following possible outcomes
  - Fault-effect excitation (FEE)
  - Fault-effect propagation (FEP)
  - Justification
  - Backtrack
    - FEE impossible
    - FEP impossible
  - Test generation complete

# Identification of TGSTs

