
EEDG/CE 6303: Testing and Testable Design

Mehrdad Nourani

**Dept. of ECE
Univ. of Texas at Dallas**


Session 09

Scan Design for Testability

Basic Concept


Architectural View

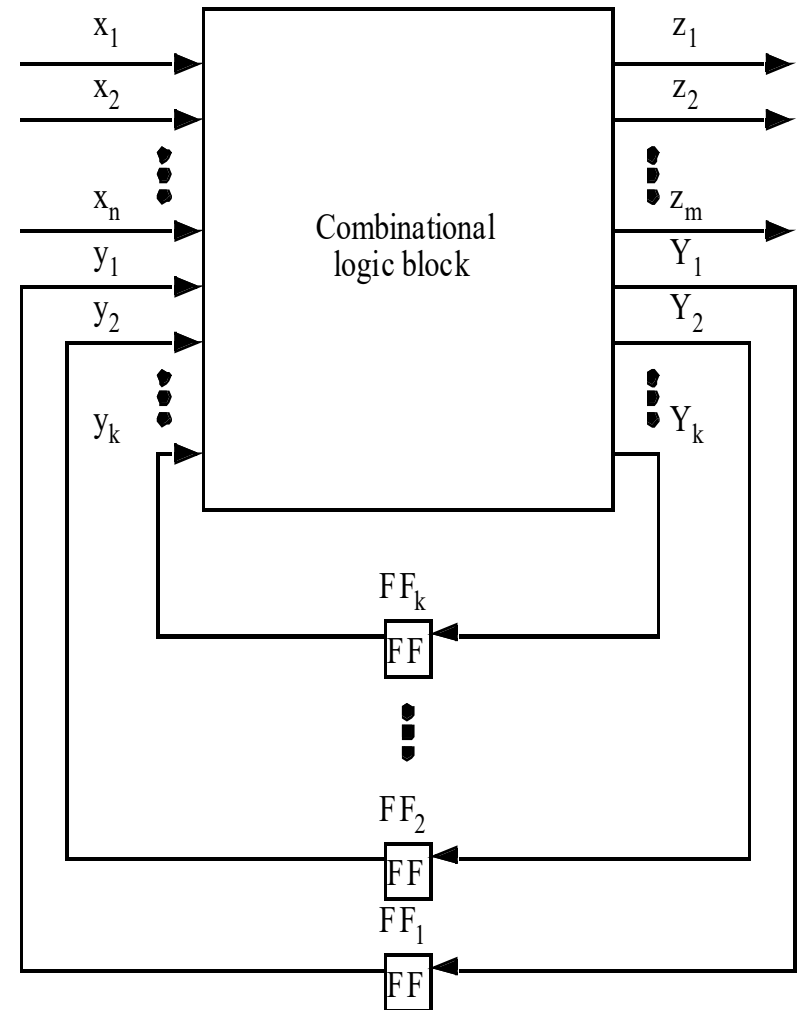- A sequential circuit is viewed as
 - A combinational logic block, with
 - Primary inputs x_1, x_2, \dots, x_n
 - Primary outputs z_1, z_2, \dots, z_m
 - State inputs (present state)
 y_1, y_2, \dots, y_k
 - State outputs (next state)
 Y_1, Y_2, \dots, Y_k
 - Y_i and y_i are respectively the input and output of FF_i




Test Generation in Scan

 - Hence, for purposes of test development
 - State inputs treated as primary inputs
 - State outputs treated as primary outputs
- By reducing test generation for sequential circuits to test generation for combinational circuits, scan
 - Reduces test development cost
 - In many cases, enables attainment of acceptable fault coverage




Scan as a DFT Method

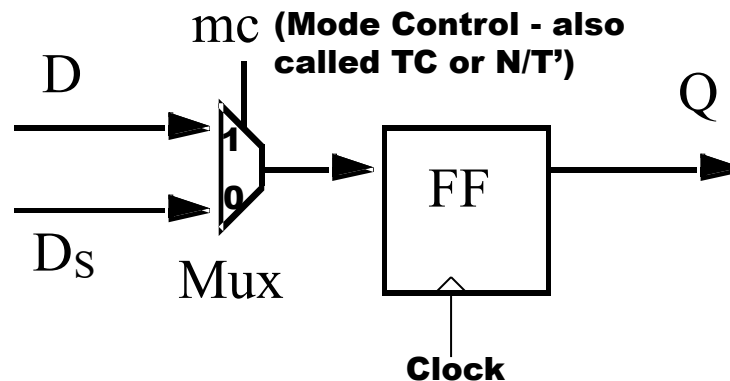- In scan DFT (design for testability) methodology, flip-flops (or latches) designed to support two modes
 - **Normal mode**: Flip-flops configured as in the original circuit
 - **Test mode**: Flip-flops configured as one or more shift-registers, called **scan registers** or **scan chains**
- Most Common Scan Flip-Flop (SFF) cell




Scan Structure

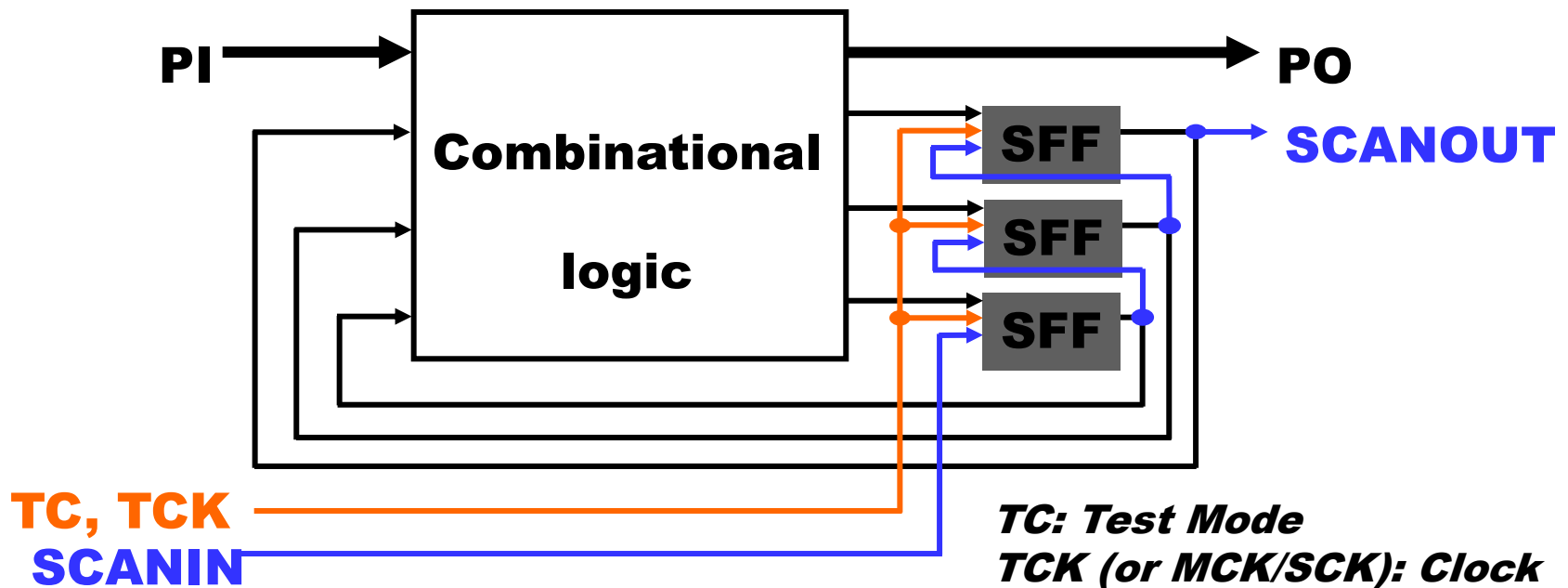- Testing using scan
 - In normal mode, responses at state outputs captured in flip-flops
 - Circuit then configured in the test mode
 - Scan registers clocked
 - The output of the last flip-flop in scan chain observed
 - At the same time, values to be applied at state inputs in the subsequent test shifted into flip-flops



Applying Test in Scan

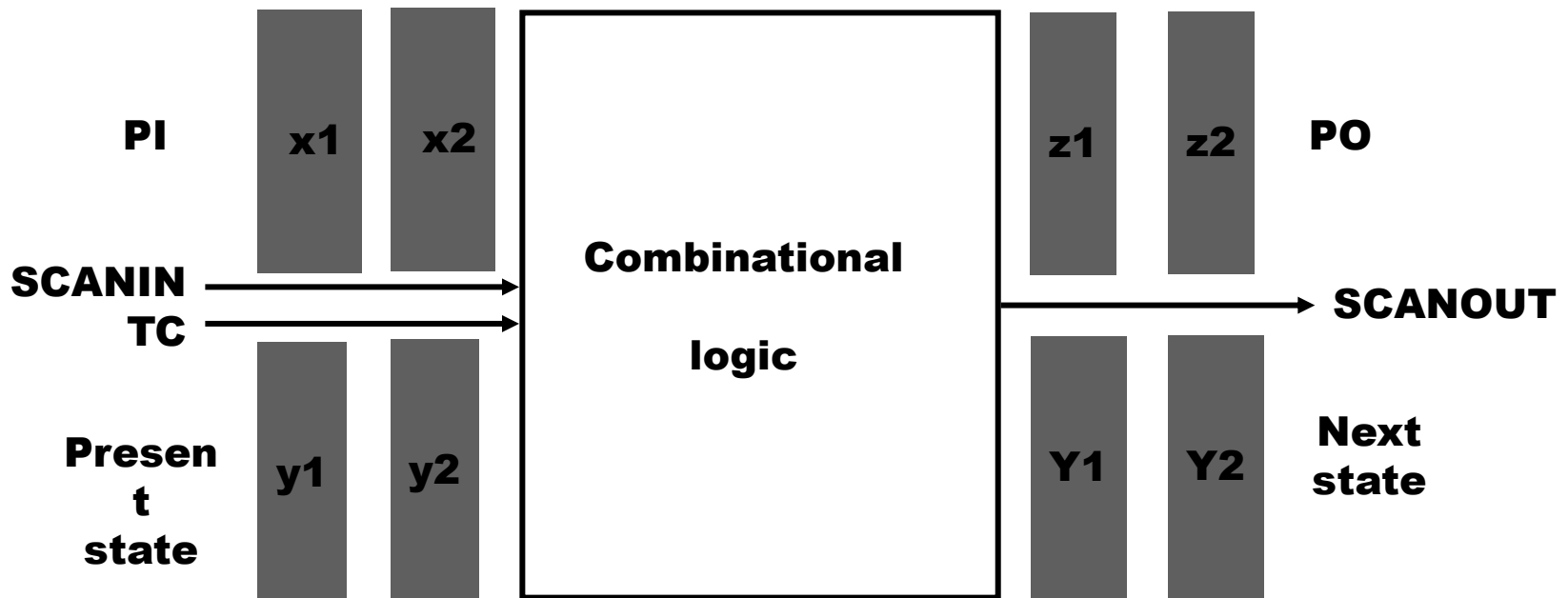- **Shift Register Test:** TC=0 (scan mode) and apply the 001100...
 - Test length: $n_{\text{sff}}+4$
- **Scan Test:**
 - TC=0 (scan mode)
 - Shift y_i values in FFs.
 - Put x_i values in PIs.
 - TC=1 (normal mode) and check z_i 's.
 - Apply clock to TCK (still normal mode).
 - TC=0 (scan mode) and shift Y_i 's out for check.



Applying Test in Scan (cont.)


- **Total scan test length (number of clocks)**

$$(n_{sff}+4) + (n_{sff}+1) n_{comb} + (n_{sff}-1) = (n_{comb}+2) n_{sff} + n_{comb} + 3$$

— n_{comb} = number of combinational vectors

— n_{sff} = number of scan flip-flops

 - Without considering shift register test: $(n_{sff}+1) n_{comb} + (n_{sff}-1)$




Applying Test in Scan (cont.)

- Scan register must be tested prior to application of scan test sequences.
- A shift sequence 00110011 . . . of length $n_{\text{sff}}+4$ in scan mode (TC=0) produces 00, 01, 11 and 10 transitions in all flip-flops and observes the result at SCANOUT output.
- Total scan test length:
 $(n_{\text{comb}} + 2) n_{\text{sff}} + n_{\text{comb}} + 3$ *clock periods*.
- Example: 2,000 scan flip-flops, 500 comb. vectors, total scan test length $\sim 10^6$ clocks.
- Multiple scan registers reduce test length.


Multiple Scan Registers

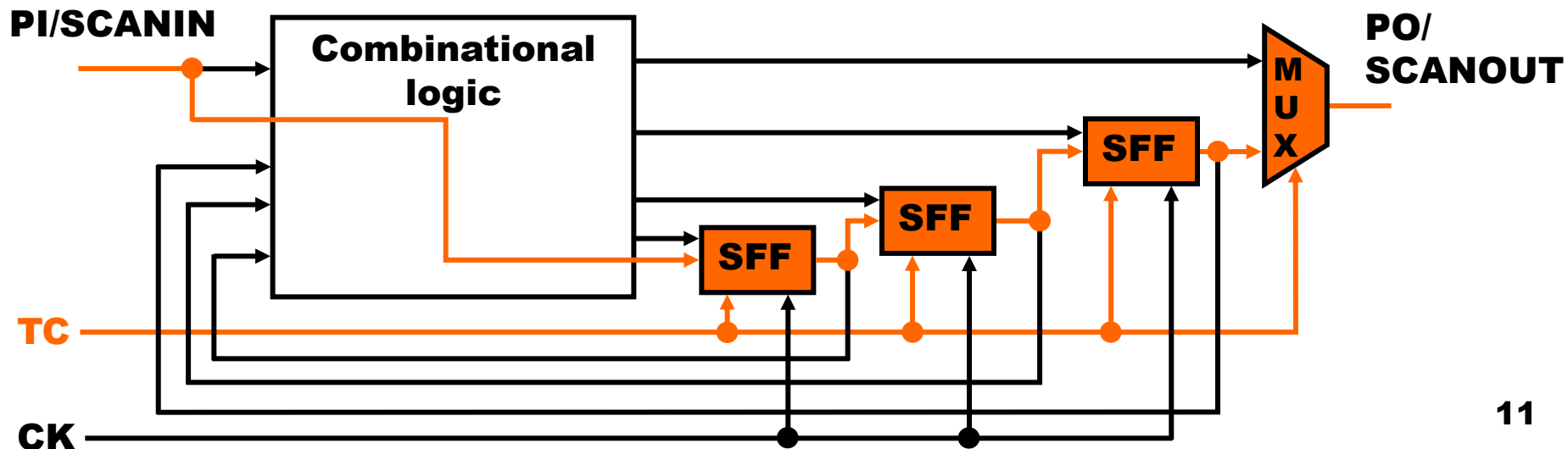- Scan flip-flops can be distributed among any number of shift registers, each having a separate *scanin* and *scanout* pin.
- Test sequence length is determined by the longest scan shift register.
- Just one *test control* (TC) pin is essential.



Scan Test Overhead

- IO pins: One pin necessary.
- Area overhead:
 - $\text{Gate overhead} = [4 n_{\text{sff}} / (n_g + 10 n_{\text{ff}})] \times 100\%$
 - $n_g = \text{comb. Gates}$
 - $n_{\text{ff}} = \text{flip-flops}$
 - Example – $n_g = 100\text{k gates}$, $n_{\text{ff}} = 2\text{k flip-flops}$, overhead = 6.7%.
 - More accurate estimate must consider scan wiring and layout area.
- Performance overhead:
 - Multiplexer delay added in combinational path; approx. two gate-delays.
 - Flip-flop output loading due to one additional fanout; approx. 5-6%.

 

Timing and Power During Scan

- Small delays in scan path and clock skew can cause race condition.
- Large delays in scan path require slower scan clock.
- Dynamic multiplexers: Skew between TC and TC signals can cause momentary shorting of D and SD inputs.
- Random signal activity in combinational circuit during scan can cause excessive power dissipation.

Full-Scan vs. Partial Scan

- In a **full-scan** circuit, scan mode and scan chains enable
 - Desired values to be **scanned in** into every flip-flop from *ScanIn*
 - Response captured in every flip-flop to be **scanned out** and observed at *ScanOut*
- In a **partial-scan**, a subset of flip-flops is scanned.
 - Minimize area overhead and scan sequence length, yet achieve required fault coverage
 - Exclude selected flip-flops from scan:
 - Improve performance
 - Allow limited scan design rule violations
 - Shorter scan sequences
- Hence, combinational part of the circuit used to generate tests

Effect on Cost and Performance

- Cost and benefits of scan
 - Area overhead: Increase in circuit area to add extra circuitry, route additional control signals and/or clocks
 - Increases chip area and hence cost, since
 - + Fewer chips manufactured per wafer
 - + Increase in area decreases yield
 - Performance penalty: Additional logic typically increases delay in normal mode
 - Performance penalty may be reduced at the cost of higher area


Effect on Cost and Performance (cont.)

- Cost and benefits of scan
 - Need extra pins for ScanIn, ScanOut, control inputs, and so on
 - Typically increase in test application time
 - For many sequential circuits, the only way to achieve acceptable fault coverage
 - Useful for debugging first silicon, i.e., the first batch of chips fabricated for a given design
 - Used to locate failing components when an operational system fails

Partial Scan

- Overheads of scan can be reduced by replacing only a subset of flip-flops in a circuit by scan flip-flops, i.e., via partial scan
- How to select flip-flops to scan?
 - To reduce area overhead, select a minimum number of flip-flops
 - To reduce performance penalty, avoid selecting flip-flops along critical paths, i.e., paths whose delays are equal to or close to the clock period
 - However, flip-flops should be selected to ensure improvements in controllability and observability values so as to provide acceptably high fault coverage



Partial Scan Architecture

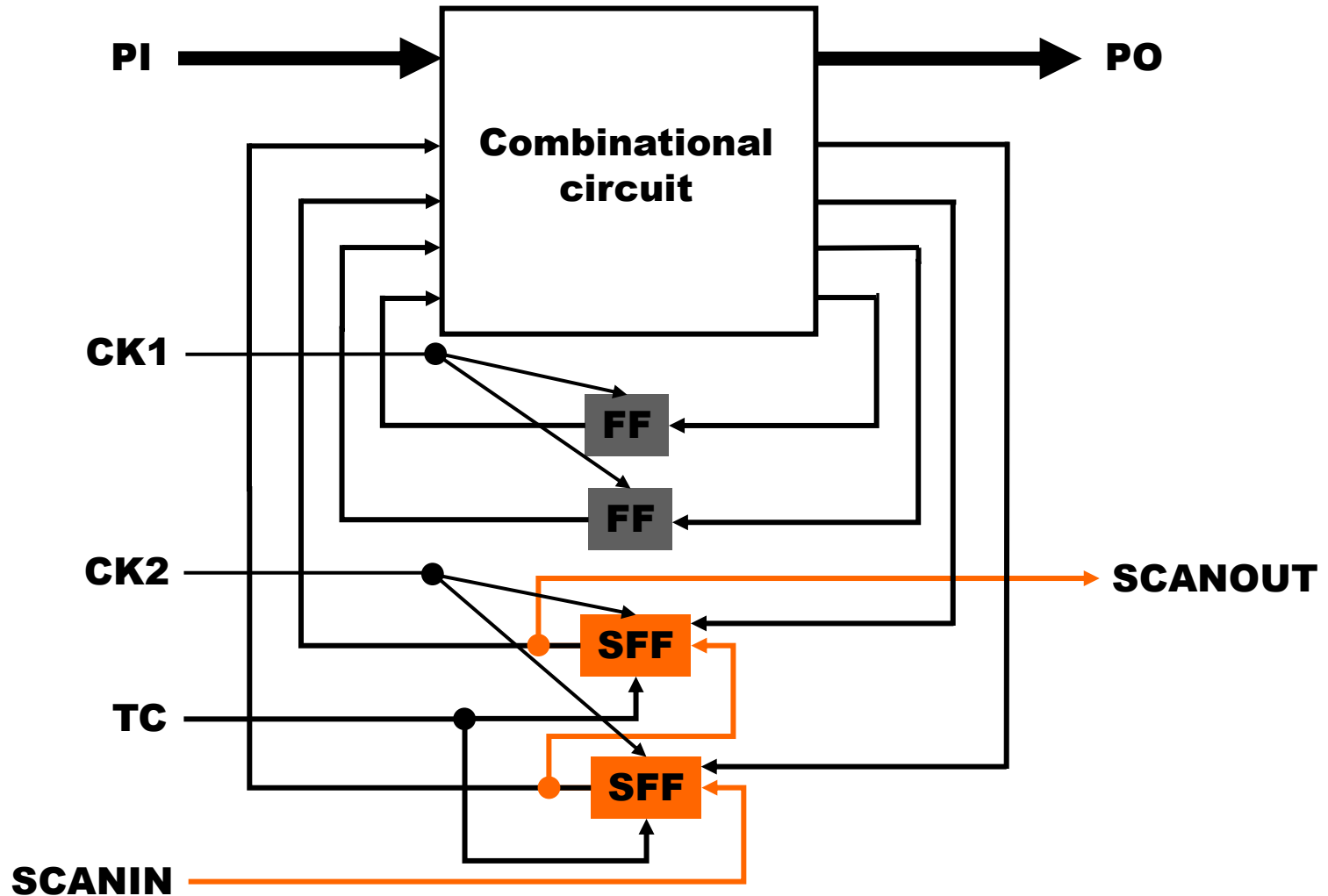

Scan Cells

Scan Design Rules

  
- Use only clocked D-type of flip-flops for all state variables.
- At least one PI pin must be available for test; more pins, if available, can be used.
- All clocks must be controlled from PIs.
- Clocks must not feed data inputs of flip-flops.



Basic Scan Cell

- **Multiplexed-input scan**

- Flip-flop design must be modified such that
 - In normal mode, the input to FF_i is the value at next state output Y_i
 - In the test mode, the input to FF_i is the value at the output of the previous flip-flop in the scan chain
- This can be achieved by adding a multiplexer
 - Two data inputs, D and D_S
 - Mode control input mc
 - + When $mc = normal$ (e.g. 0), input D is selected
 - + When $mc = test$ (e.g. 1), input D_S is selected

 


Basic Scan Cell (cont.)


- Scan flip-flops are connected to support test and scan modes
 - The D input of FF_i is connected to the state output Y_i
 - The D_S input of FF_i is connected to the output of the previous flip-flop in the scan chain
 - The D_S input of the first flip-flop in the scan chain is connected to $ScanIn$, the input to the scan chain
 - The output of FF_i is connected to the state input y_i
 - The output of the last flip-flop in the chain is connected to $ScanOut$, the output of the scan chain

Normal vs. Scan Mode


Normal Mode

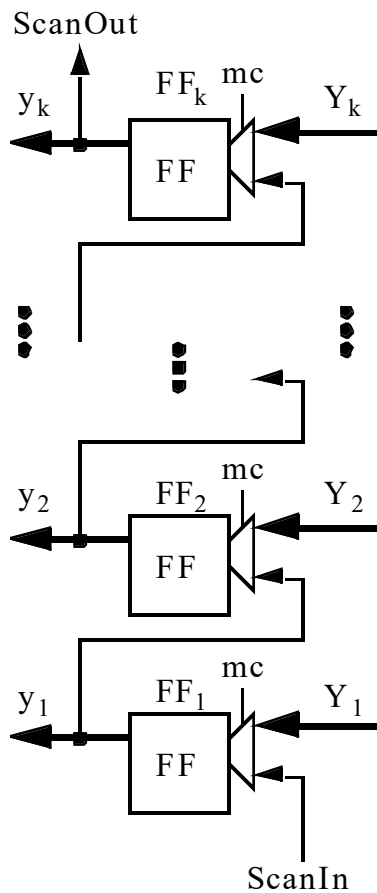


Scan Mode

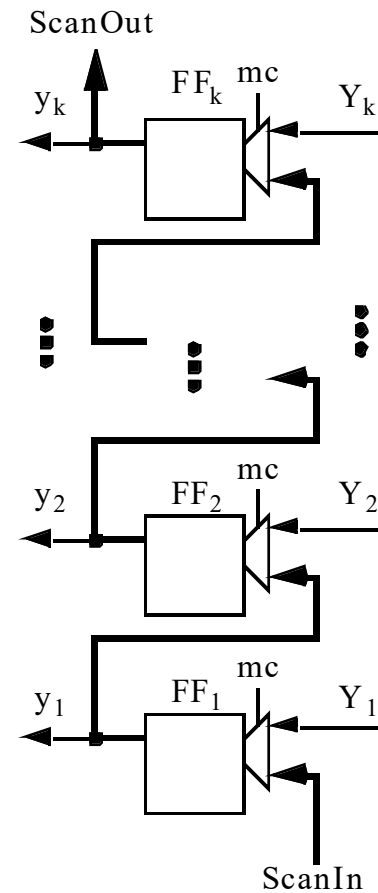

Implementation of Scan FF Cell

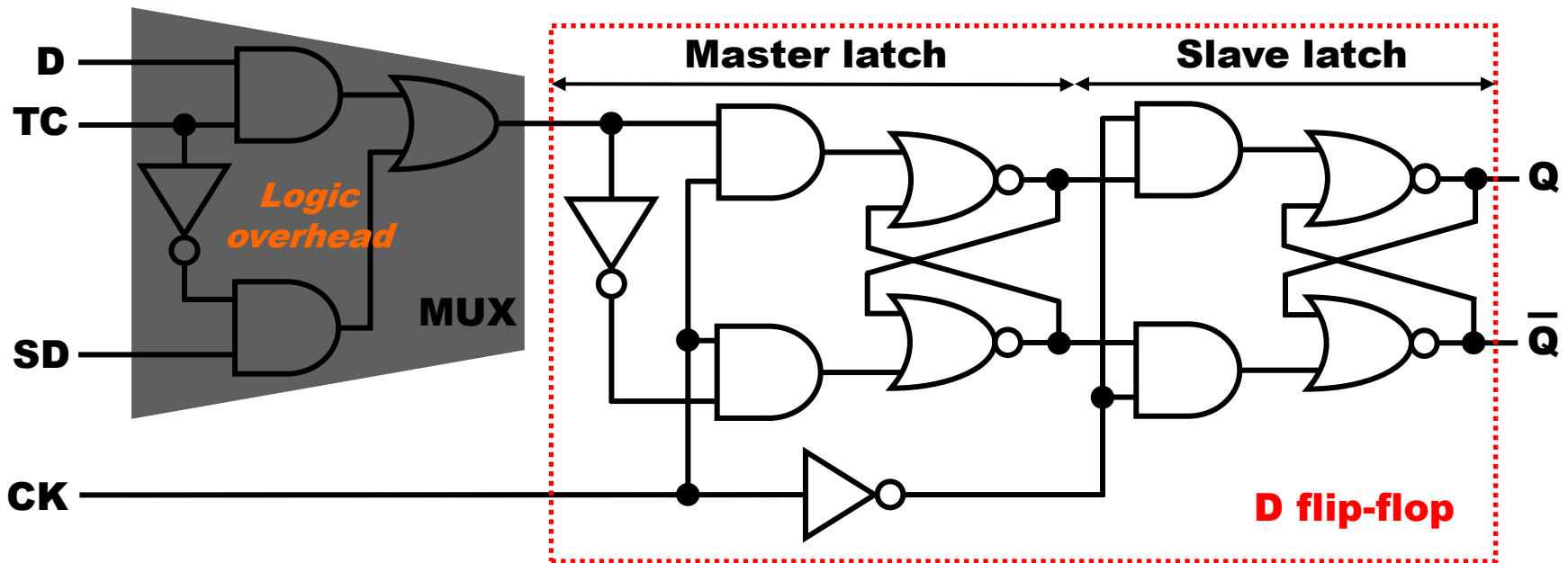


Level-Sensitive Scan D Latch (LSSD)

 


Scan-Hold Flip Flop (SHFF)

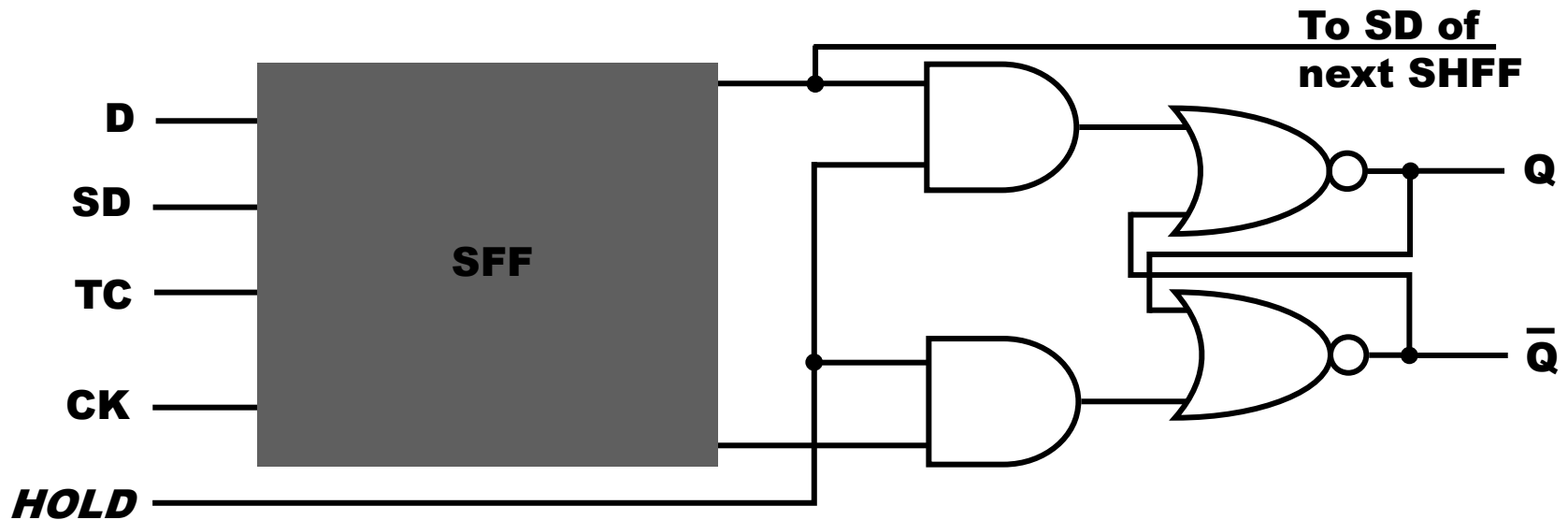
- The control input *HOLD* keeps the output steady at previous state of flip-flop.
- Applications:
 - Reduce power dissipation during scan
 - Isolate asynchronous parts during scan test
 - Delay testing (applying V1→V2 pair)



Random-Access Scan (RAS)


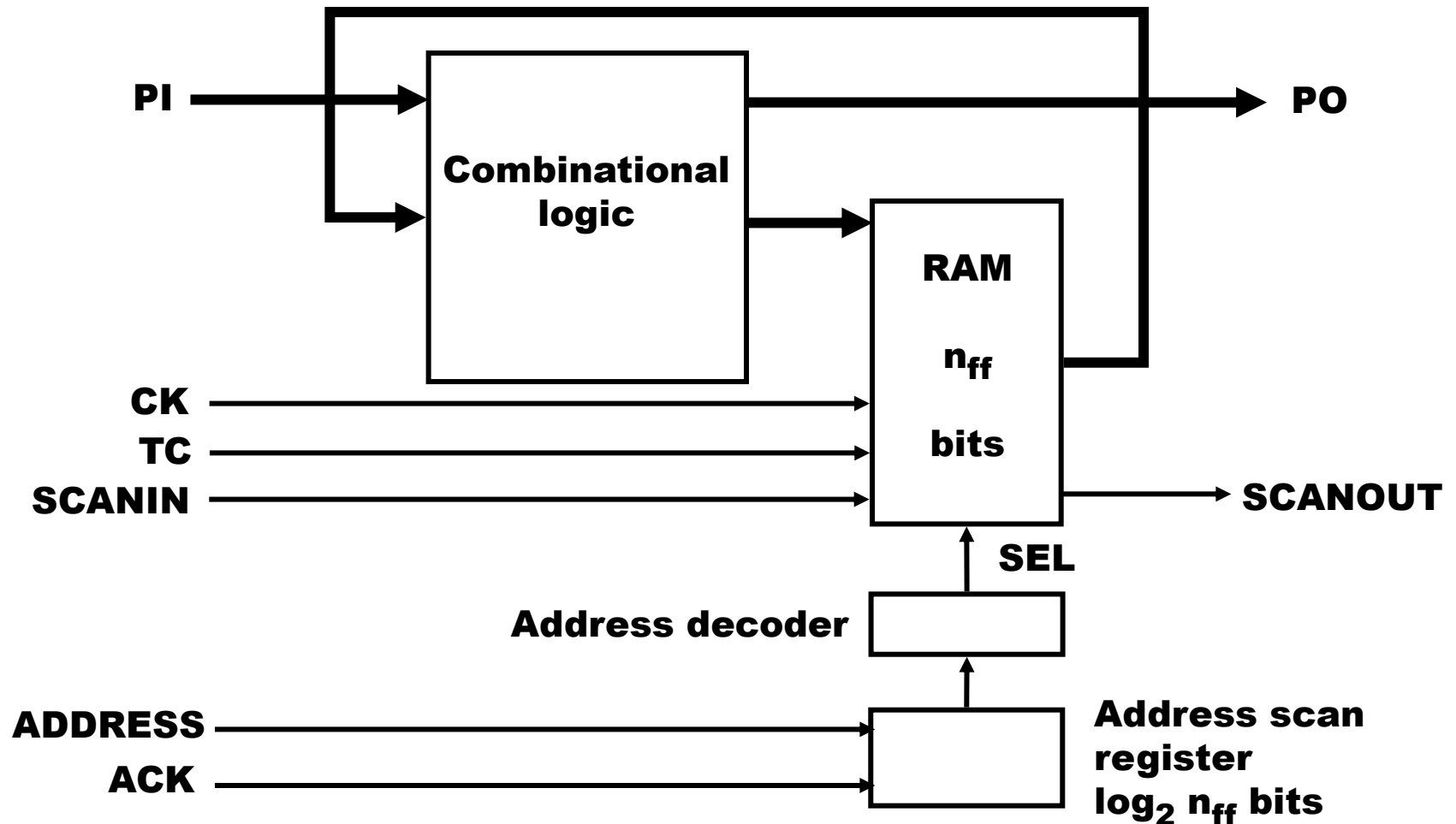


RAM Cell in RAS

 


Single Latch Design - Cells

  - Holds output and state constant when clock is low
- When clock is high, changes in D are reflected at its state as well as outputs with some delay
- Symbol and one possible implementation
- Used in certain types of circuits, e.g., high speed data paths





Single Latch Design - Configuration

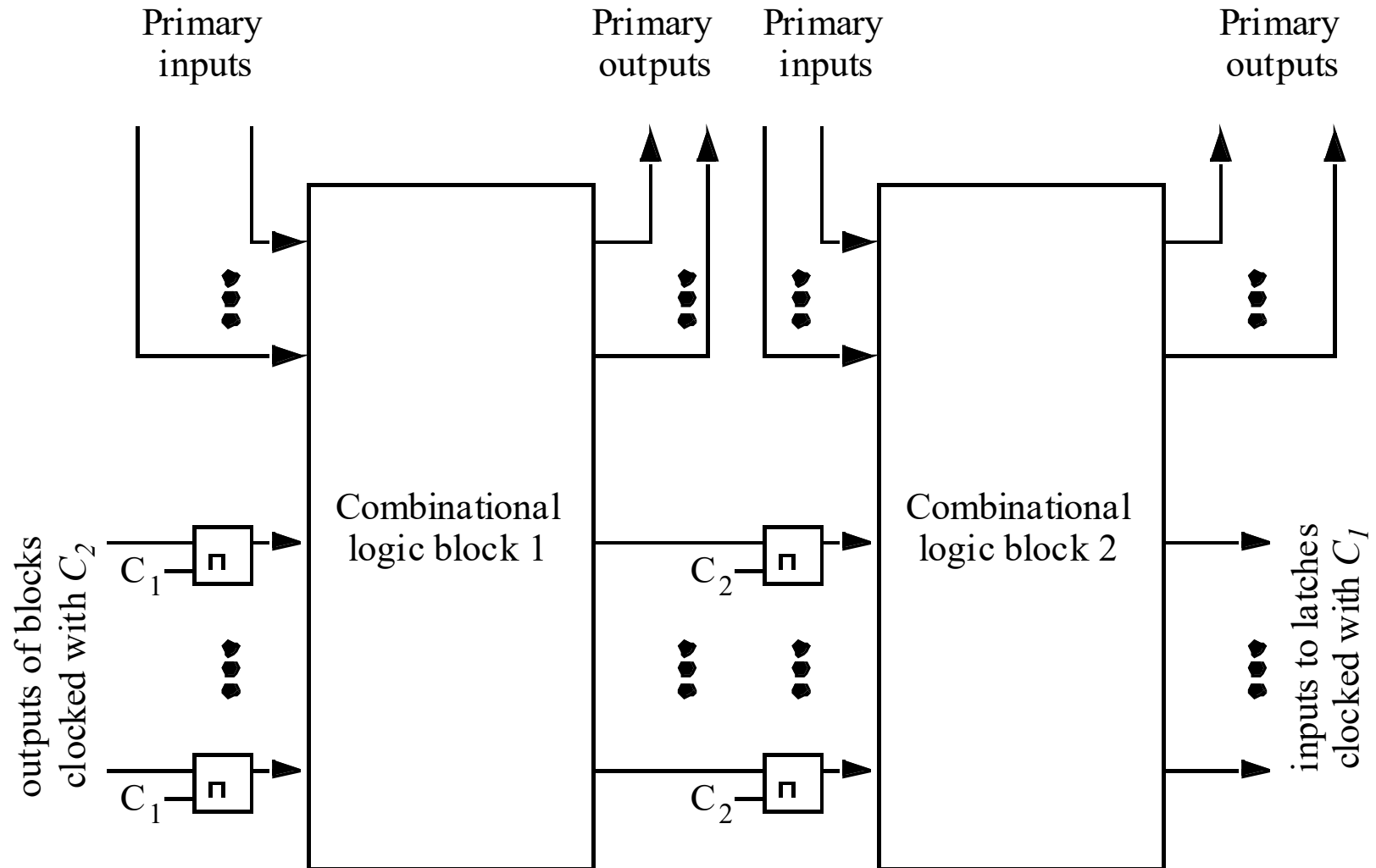


Double Latch Design - Cells

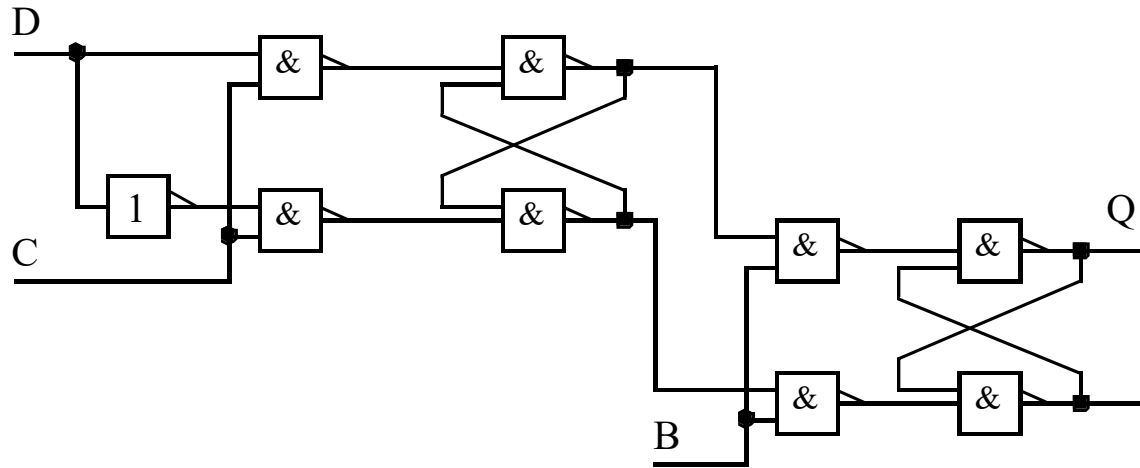 - Two clocks B and C must be non-overlapping, i.e., they must not assume the value 1 at the same time.
 - In particular, B can be complement of C




Double Latch Design - Configuration

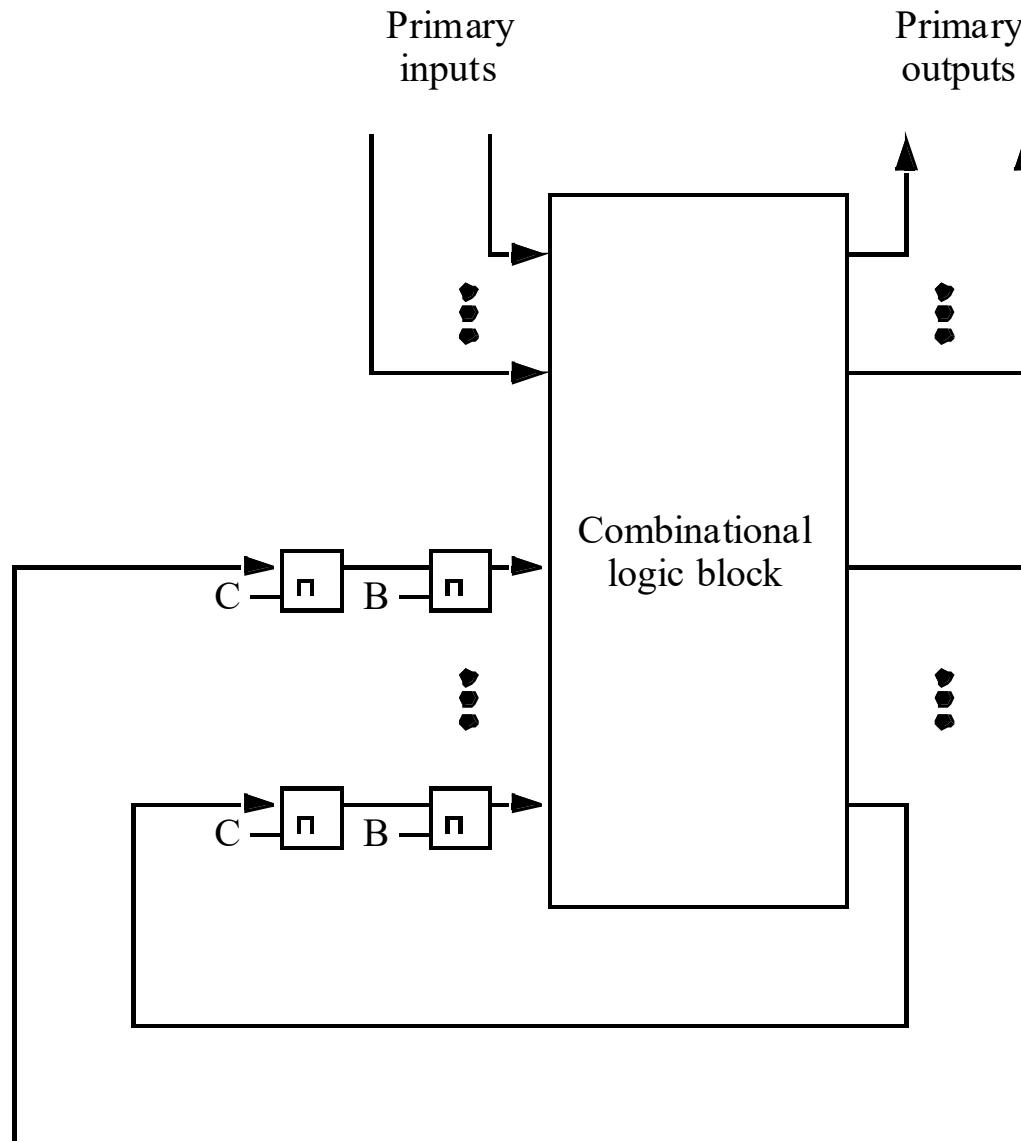


Level Sensitive (LS) Scan Element

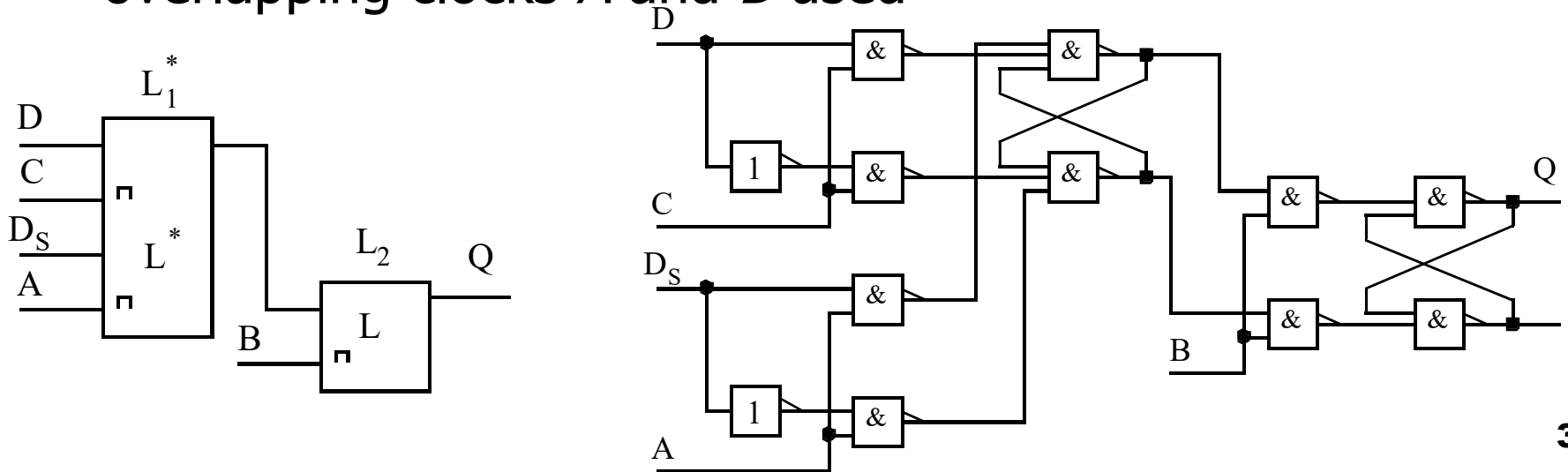
- Latch L_1 in a standard master-slave configuration replaced by a two-port latch L^* , called L_1^*
- L_1^* has
 - Two data inputs D and D_S
 - Two clocks C and A
- L_2 remains unchanged
- In normal mode, clock A held low ($A=0$) and non-overlapping clocks C and B used
- In test (scan) mode, clock C held low ($C=0$) and non-overlapping clocks A and B used



LS Element in Single Latch Configuration

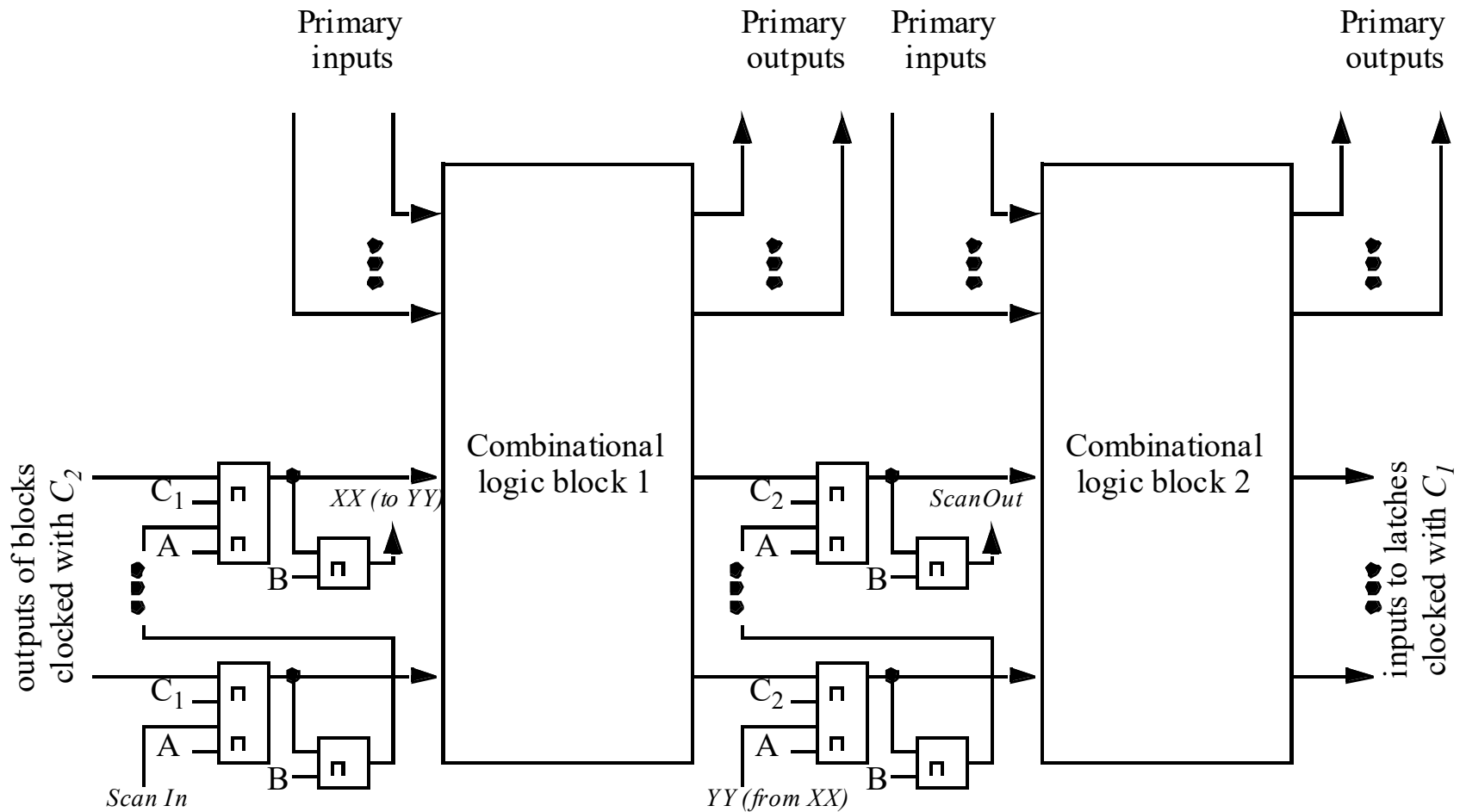

LS Element in Double Latch Configuration

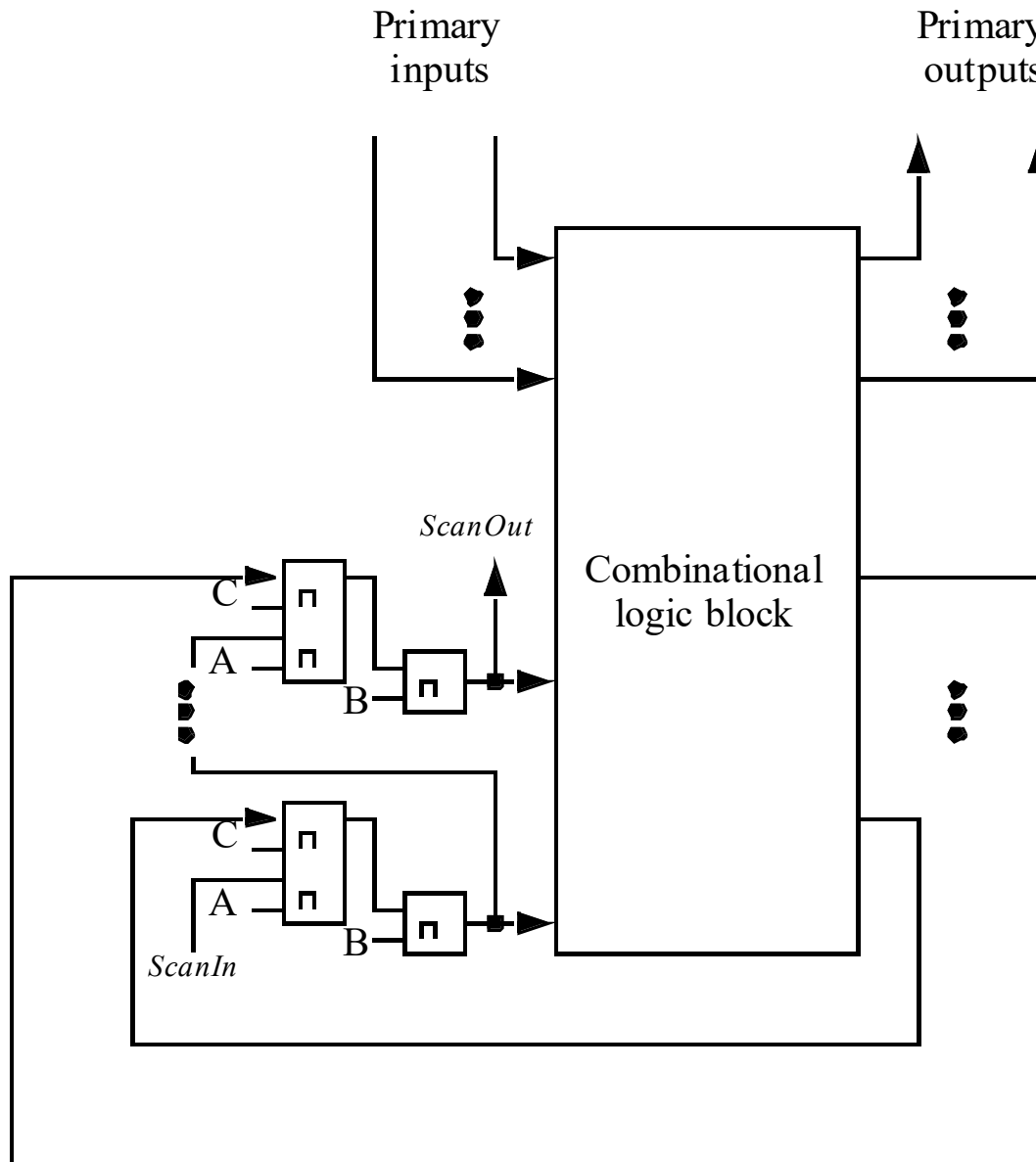

Scan Chain Organization

Organization of Scan Chains

- To organize scan flip-flops into chains by
 - Partitioning them into multiple chains (if applicable)
 - Ordering flip-flops within each chain
 - Using reconfiguration circuitry (if applicable)
- To reduce test application time
- Model of circuit – assuming full-scan
 - Gates and fanout systems combined into one or more maximal combinational blocks
 - Obtained by iteratively combining into one block any two circuit elements between which a combinational path exists
 - Called $CLB_1, CLB_2, \dots, CLB_{Nb}$

Organization of Scan Chains (cont.)

- Model of circuit – assuming full-scan
 - All flip-flops whose normal data inputs are driven by outputs of CLB_j and whose outputs drive inputs of CLB_j (j may be equal to i) are combined into a register
 - Such a register is said to be a
 - + Receiver for CLB_j
 - + Driver for CLB_j
 - $Lreg_j$ is the length of register R_j , i.e., the number of flip-flops in R_j

Definitions & Metrics


- A kernel is a sub-circuit that can be tested independently of the rest of the circuit
- In a full-scan circuit
 - A kernel (K_i) is synonymous with a maximal combinational block (CLB_i)
 - Number of kernels, $N_k = N_b$
- In a partial-scan circuit, a kernel may contain
 - One or more maximal combinational blocks
 - Non-scan registers

Definitions & Metrics (cont.)

- Register R_i is receiver for kernel $K_{j'}$ if outputs of K_j drive normal data inputs of R_i
- R_i is driver for $K_{j'}$ if outputs of R_i drive inputs of K_j
- R_i is a pure-driver if it is not a receiver for any kernel
- R_i is a pure-receiver if it is not a driver for any kernel


The Running Example

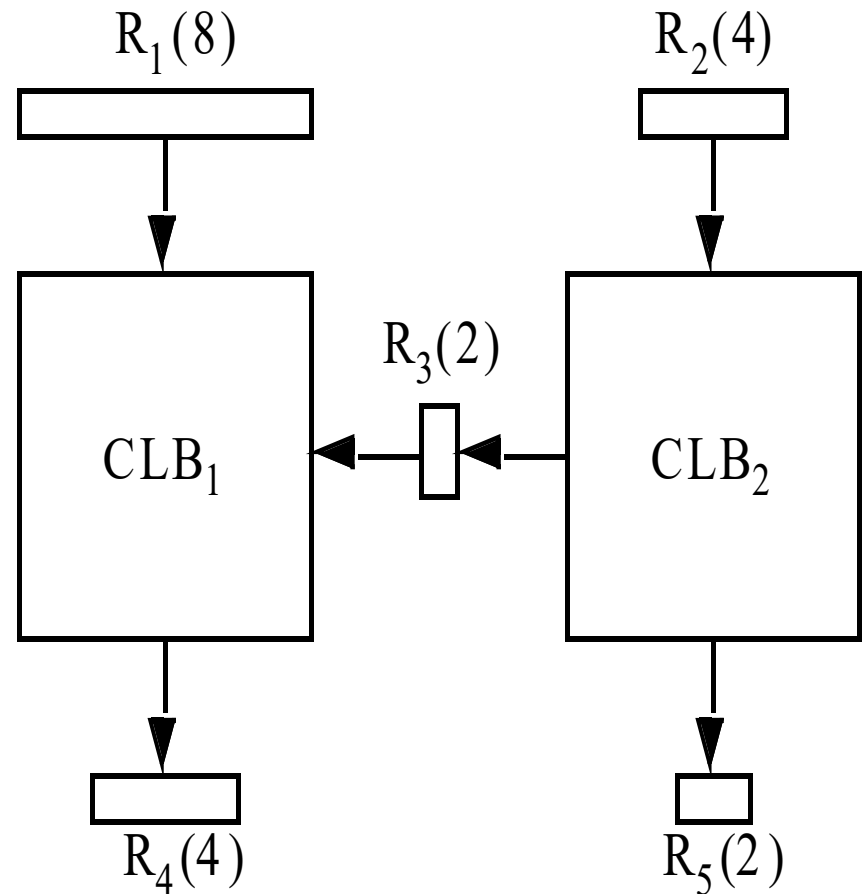- R_1, R_2, R_3, R_4, R_5 registers of lengths 8, 4, 2, 4, and 2, respectively
- R_1 and R_2 pure drivers for CLB_1 and CLB_2 , respectively
- R_4 and R_5 pure receivers for CLB_1 and CLB_2 , respectively
- R_3 is a driver for CLB_1 and receiver for CLB_2



Organization Example – One Test Session

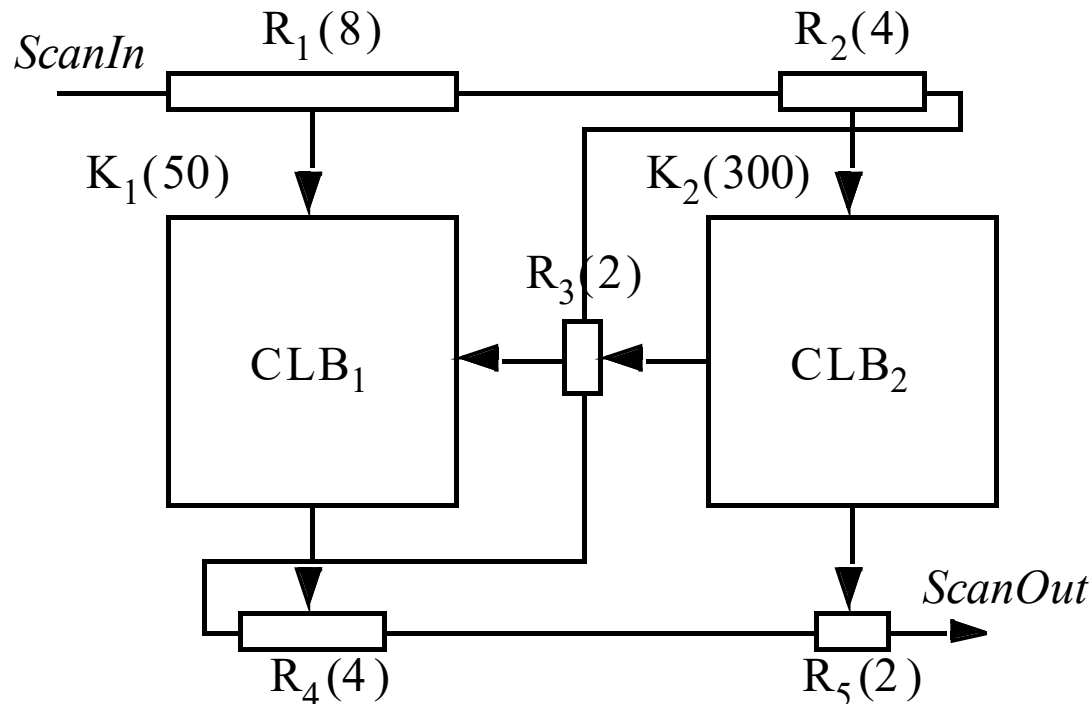- Full-scan version of above example circuit
- K_1 and K_2 are identical to CLB_1 and CLB_2 , respectively



Optimization Metrics

- Let NT_i be the number of test vectors for K_i
- Assume $NT_1 \cdot NT_2 \cdot \dots \cdot NT_{N_k}$
- In a circuit with multiple (N_{sc}) scan chains
 - Chains are called $ScanChain_i$, $1 \cdot i \cdot N_{sc}$
 - $ScanChain_i$ has
 - Scan input output $ScanIn_i$ and $ScanOut_i$
 - SCL_i flip-flops
 - We assume synchronous scan, i.e., all chains share a single mode control (mc) signal


Optimization Metrics (cont.)

- Driving weight of a register R_i DRW_i is the number of vectors for which R_i is used as a driver
- If R_i is a driver for kernel K_j , then $DRW_i = NT_j$
- Receiving weight of a register R_i RCW_i is defined in a similar manner

Organization Example – Two Test Session

- $NT1 = 50$ and $NT2 = 300$
- $R1$ is pure driver with $DRW1 = 50$ and, by definition, $RCW1 = 0$
- $R5$ is pure receiver with $RCW5 = 300$ and, by definition, $DRW5 = 0$
- $R3$ is a driver/receiver with $DRW3 = 50$ and $RCW3 = 300$

Register	Bitwidth	Type	DRW	RCW
R1	8	Pure Driver	50	0
R2	4	Pure Driver	300	0
R3	2	Driver/Receiver	50	300
R4	4	Pure Receiver	0	50
R5	2	Pure Receiver	0	300

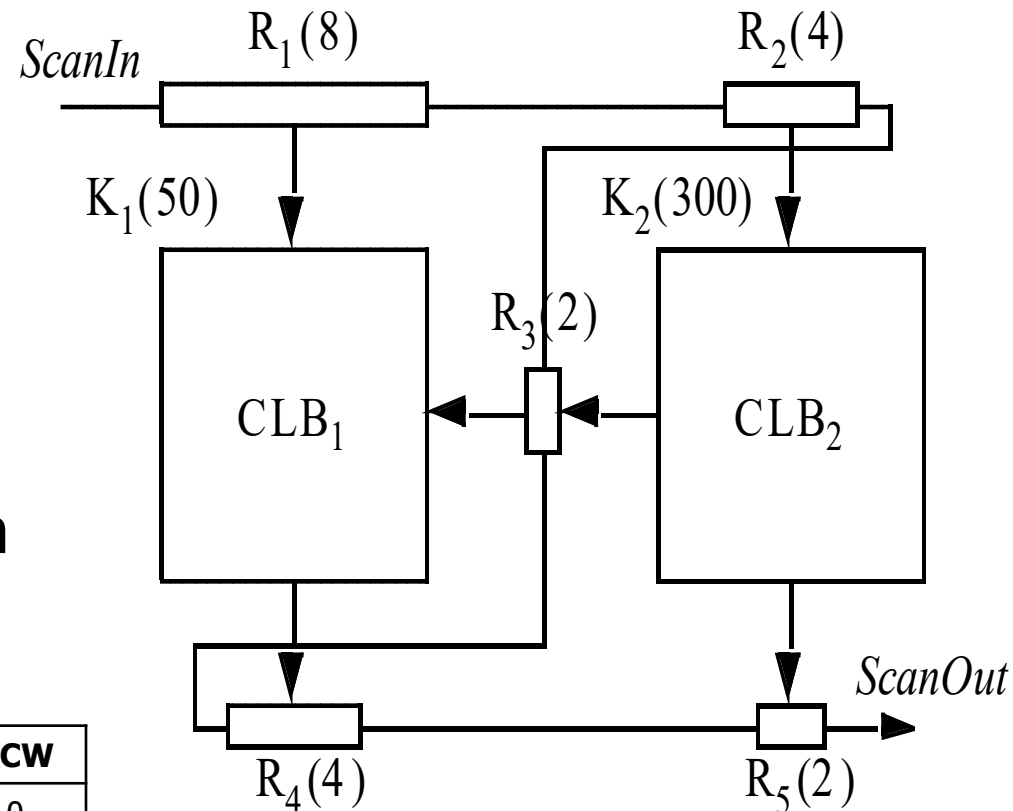

Test Vectors vs. Test Sessions

- Characteristics of scan vectors
 - Vectors may have many don't cares
 - Different kernels require different numbers of vectors
- Desired values must be scanned into some registers for many more vectors than into others
- Responses captured in some registers need to be scanned out for many more vectors than those captured in others
- Test sessions
 - A circuit may be tested in multiple test sessions
 - In each test session, a different combination of kernels tested


Test Application Schemes

- 1. Combined test application scheme
 - Circuit tested in one session
 - All kernels tested simultaneously
 - The number of vectors applied is the maximum of the number of vectors required for any kernel
- 2. Overlapped test application scheme
 - Assume $NT_1 < NT_2 < \dots < NT_{N_k}$
 - Circuit tested in N_k sessions
 - In the first session, $NTS^{Ovr}(TSes_1) = NT_1$ vectors applied to all kernels
 - In the second session, $NTS^{Ovr}(TSes_2) = NT_2 - NT_1$ vectors applied to all kernels except K_1
 - In the third session, $NTS^{Ovr}(TSes_3) = NT_3 - NT_2$ vectors applied to all kernels except K_1 and K_2
 - ...
 - In the last session, $NTS^{Ovr}(TSes_{N_k}) = NT_{N_k} - NT_{N_k - 1}$ vectors applied to the last kernel

Test Application Schemes (cont.)

- 3. Isolated test application scheme
 - In each session, one kernel is tested by itself
 - In the first session, NT_1 vectors applied to K_1
 - In the second session, NT_2 vectors applied to K_2
 - ...
 - This mechanism is not of interest as it has no advantage over the other two.

Comparing Test Application Schemes

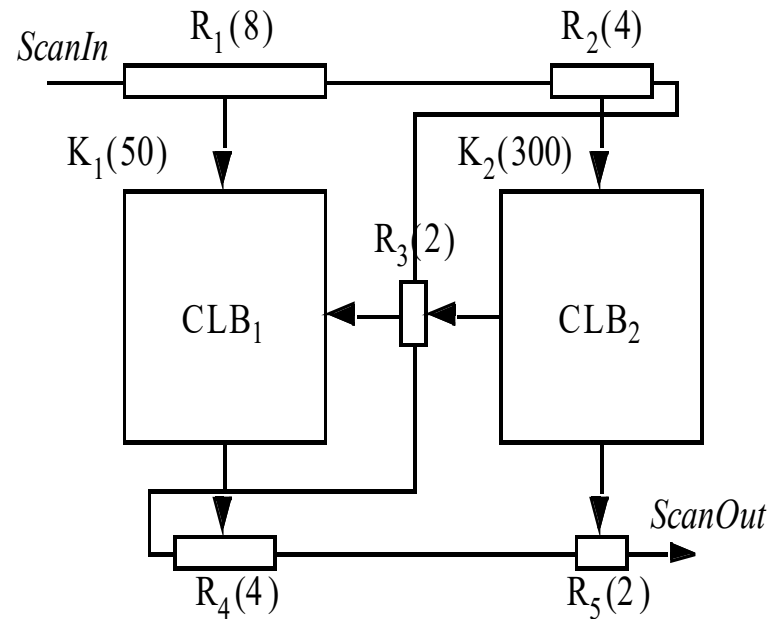


	$TSes_1$	$TSes_2$
Combined	300 vectors to K_1 & K_2	--
Overlapped	50 vectors to K_1 & K_2	250 vectors to K_2
Isolated	50 vectors to K_1	300 vectors to K_2

- Overlapped test application scheme most efficient

Role of Active Drivers/Receivers

- Active drivers in session $TSes_i$, $AD(TSes_i)$, is the set of drivers into which desired values need to be scanned in $TSes_i$
- Active receivers in session $TSes_i$, $AR(TSes_i)$, is the set of receivers from which responses need to be scanned out in $TSes_i$
- For the example circuit
 - $AD(TSes_1) = \{R_1, R_2, R_3\}$;
 $AR(TSes_1) = \{R_3, R_4, R_5\}$
 - $AD(TSes_2) = \{R_2\}$; $AR(TSes_2) = \{R_3, R_5\}$
- A chain is active in $TSes_i$ if any of the registers in the chain is active as a driver or receiver in $TSes_i$

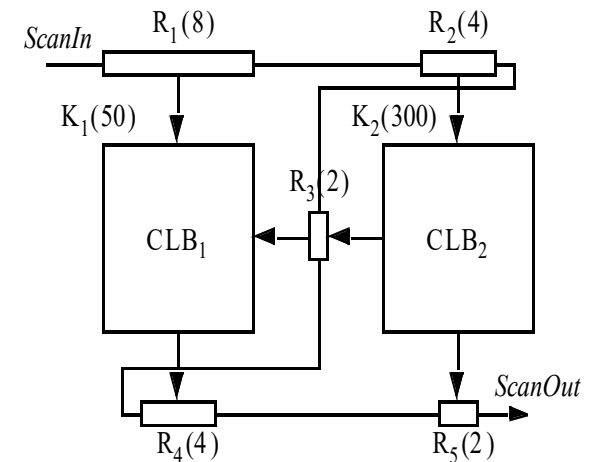

Scan Shift/Flush Policy

- Scan-shift policies
 - Scan has two purposes
 - To scan out response captured for the previous vector
 - To scan in the next vector
- I. Flush policy
 - For every chain
 - Content of every flip-flop scanned out
 - Test data scanned into every flip-flop
 - If N_{sc} chains of lengths $SCL_1, SCL_2, \dots, SCL_{N_{sc}}$
 - For application of each vector, chains configured in test mode, and
 - $SC^{Flush} = \max(SCL_1, SCL_2, \dots, SCL_{N_{sc}})$ clocks applied
 - SC^{Flush} is called the shift cycle for the flush policy

Minimum Shift Policy

- II. Minimum shift policy – in a particular test session
 - Shift test data into every active driver
 - Shift response out of every active receiver
 - If for $ScanChain_i$ the above two respectively require $SCin_i$ and $SCout_i$ cycles, then
 - $SC_i = \max(SCin_i, SCout_i)$
 - Hence, for that session, $SC^{MS} = \max_i SC_i$


Example of Shift/Flush Policy

- For flush policy

- $SC^{Flush}(TSes_1) = 20$ cycles (8+4+2+4+2)
- $SC^{Flush}(TSes_2) = 20$ cycles
- Time (Combined) = $n_{comb}(n_{sff}+1) + (n_{sff}-1) = 300(20+1) + (20-1) = 6319$

- Lower shift-cycle can be used (i.e. Minimum Shift)

- In $TSes_1$
 - Test data needs to be scanned into R_1 , R_2 , and R_3
 - + Hence, $SCin = 8+4+2 = 14$
 - Response needs to be scanned out of R_3 , R_4 , and R_5
 - + Hence, $SCout = 2+4+2 = 8$
 - Hence, $max(SCin, SCout) = 14$ cycles sufficient for $TSes_1$
- In $TSes_2$, only R_2 active as a driver and R_3 and R_5 as receivers
 - Hence, $SCin = 8+4 = 12$, $SCout = 2+4+2 = 8$
 - Hence, $max(SCin, SCout) = 12$ cycles sufficient for $TSes_2$
- Time (Overlapped) = $[50(14+1) + 250(12+1)] + (14-1) = 4013$

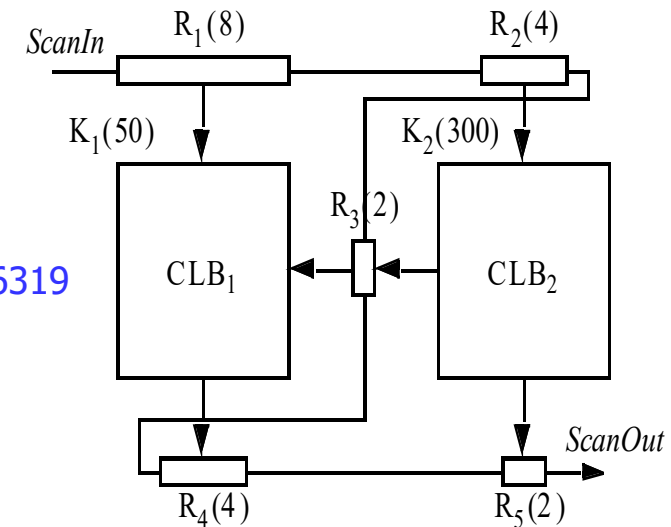

Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

Active Shift/Flush Policy


- III. Active flush policy
 - Flush policy applied only to active scan chains
 - For **single chain** designs, identical to flush policy
- IV. Active minimum-shift policy
 - Minimum shift policy applied only to active scan chains
 - For **single chain** designs, identical to minimum-shift policy

Summary of Scan Application/Shift

Number of Chains	Scan-Shift Policy	Test Application Schemes		
		Combined (Test all kernels in one session; $N_{\text{vectors}} = \text{Max}\{N_k\}$)	Overlapped (Test K kernels in K sessions; $N_{\text{vectors}} = N_1, N_2, \dots, N_k$)	Isolated (Test one kernel per session)
One	Flush (scan in/out into/from all FFs)			Has no advantage over other schemes/policies. It's not of interest.
	Minimum-Shift (scan in/out into/from active driver/receiver FFs)		Minimum Overall Time	
Multiple	Active Flush (apply flush to active scan chains)			
	Active Minimum-Shift (apply minimum-shift to active scan chains)		Minimum Overall Time	

Comparison - Single Scan Chain Example

Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

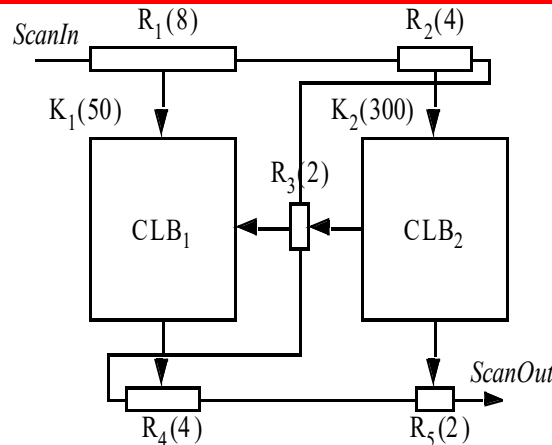


	Combined	Overlapped
Flush	6319	6319
Minimum-Shift	4513	4013

- Shift Policy: Flush; Application Scheme: Combined
 - Time = $[n_{\text{comb}}(n_{\text{sff}}+1)]+(n_{\text{sff}}-1) = [300(20+1)]+(20-1) = 6319$
- Shift Policy: Flush; Application Scheme: Overlapped
 - Time = $[50(20+1)+250(20+1)]+(20-1) = 6319$
- Shift Policy: Minimum-Shift; Application Scheme: Combined
 - Time = $[300(14+1)]+(14-1) = 4513$
 session 1: max input/output scan shifts = $\max\{14,8\} = 14$
- Shift Policy: Minimum Shift; Application Scheme: Overlapped
 - Time = $[50(14+1)+250(12+1)]+(14-1) = 4013$
 session 1: max input/output scan shifts (CLB₁ and CLB₂) = $\max\{14,8\} = 14$
 session 2: max input/output scan shifts (CLB₂) = $\max\{12,8\} = 12$

Multiple Scan Chains

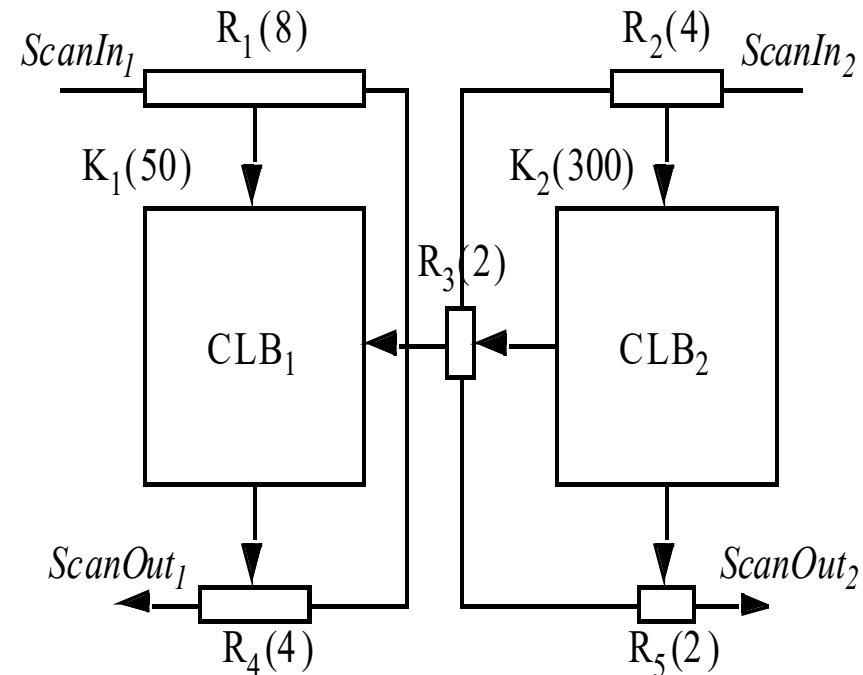
- This design has two chains
 - $ScanChain_1$ with $SCL_1 = 12$
 - $ScanChain_2$ with $SCL_2 = 8$
- Under overlapped test application
 - For active flush policy
 - $SC^{AFlush}(TSes_1) = \max\{12, 8\} = 12$
 - $SC^{AFlush}(TSes_2) = 8$
 - For active minimum-shift policy
 - $SC^{AMS}(TSes_1) = 8$ and $SC^{AMS}(TSes_2) = 4$



Register	Bitwidth	Type	DRW	RCW
R1	8	Pure Driver	50	0
R2	4	Pure Driver	300	0
R3	2	Driver/Receiver	50	300
R4	4	Pure Receiver	0	50
R5	2	Pure Receiver	0	300

Comparison - Multiple Scan Chain Example

Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

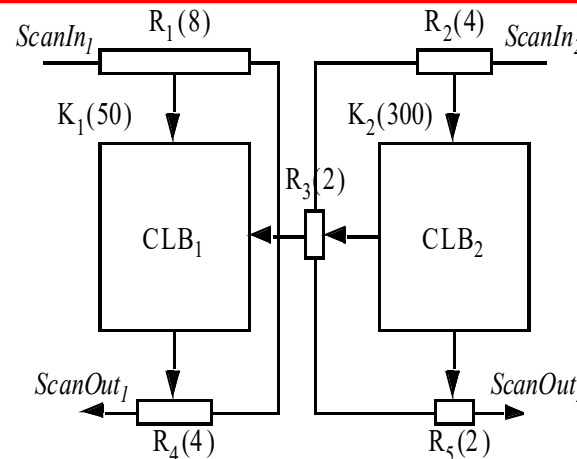


	Combined	Overlapped
Flush	3911	2911
Minimum-Shift	2707	1707

- Shift Policy: Active Flush; Application Scheme: Combined
 - Time = $[300(12+1)] + (12-1) = 3911$ ($\max\{12, 8\} = 12$ is max length of active chains)
- Shift Policy: Active Flush; Application Scheme: Overlapped
 - Time = $[50(12+1) + 250(8+1)] + (12-1) = 2911$
- Shift Policy: Active Minimum-Shift; Application Scheme: Combined
 - Time = $[300(8+1)] + (8-1) = 2707$
 session 1: max active scan shifts (ScanIn1 and ScanIn2) = $\max\{\max\{8, 4\}, \max\{6, 4\}\} = 8$
- Shift Policy: Active Minimum Shift; Application Scheme: Overlapped
 - Time = $[50(8+1) + 250(4+1)] + (8-1) = 1707$
 session 1: max active scan shifts (ScanIn1 and ScanIn2) = $\max\{\max\{8, 4\}, \max\{6, 4\}\} = 8$
 session 2: max active scan shifts (ScanIn2) = $\max\{4, 4\} = 4$

Register Organization

- Organization of registers in a single chain depends upon
 - The test application scheme
 - Shift policy
 - The characteristics of design, including
 - The numbers of tests required for each kernel
 - Sizes and driving/receiving weights of registers
 - The key operation is ordering of registers in the chain
- Ordering of registers
 - No impact for flush policy
 - But has impact for minimum-shift policy


Register Organization – Single Chain #1

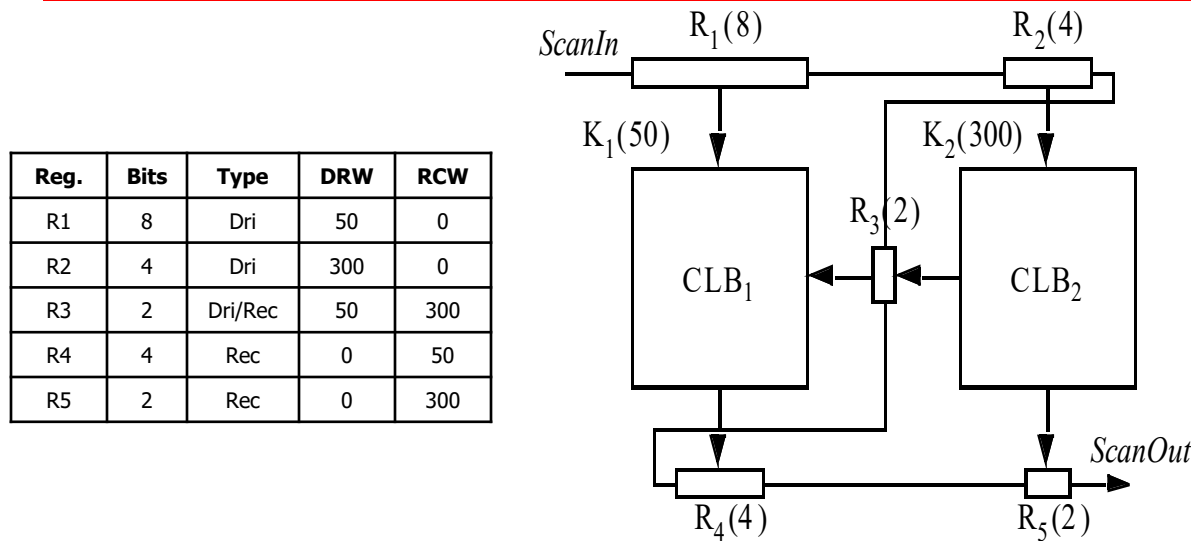

- Organization: overlapped test application and minimum-shift policy
 - In TSes1, 50 vectors applied to CLB1 and CLB2 (Kernels K1 and K2)
 - In TSes2, 250 vectors applied to CLB2 (Kernel K2)
 - $AD(TSes1) = \{R1, R2, R3\}$
 - $AR(TSes1) = \{R3, R4, R5\}$
 - $AD(TSes2) = \{R2\}$
 - $AR(TSes2) = \{R3, R5\}$
 - $SC(TSes1) = \max\{14, 8\} = 14$ and $SC(TSes2) = \max\{12, 8\} = 12$
 - Hence, test application time for this order of registers
 - $Time = [50(14 + 1) + 250(12 + 1)] + (14 - 1) = 4013$ clock cycles

Register Organization – Single Chain #2


Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

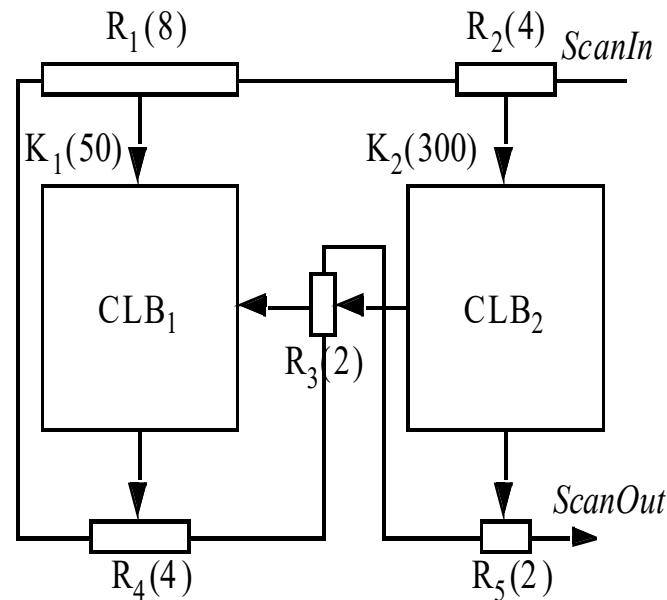

- Organization: overlapped test application and minimum-shift policy
 - In TSes1, 50 vectors applied to CLB1 and CLB2
 - In TSes2, 250 vectors applied to CLB2
 - $SC(TSes1) = \max\{18, 8\} = 18$ and $SC(TSes2) = \max\{4, 4\} = 4$
 - Hence, test application time for this order of registers
 - Time = $[50(18 + 1) + 250(4 + 1)] + (18 - 1) = 2217$ clock cycles

Register Organization – Multiple Chains #1


Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

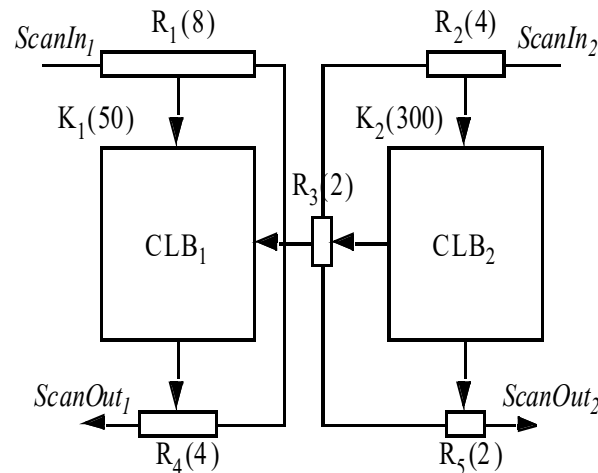

- Organization: overlapped test application and minimum-shift policy
 - TSes1: 50 vectors applied to CLB1 and CLB2
 - TSes2: 250 vectors applied to CLB2
 - $SC1(TSes1) = \max\{8, 4\} = 8$ and $SC2(TSes1) = \max\{6, 4\} = 6 \rightarrow SC(TSes1) = \max\{8, 6\} = 8$
 - $SC1(TSes2) = 0$ (NOT ACTIVE), and $SC2(TSes2) = \max\{4, 4\} = 4 \rightarrow SC(TSes2) = \max\{0, 4\} = 4$
 - Hence, test application time for this order of registers
 - Time = $[50(8+1) + 250(4+1)] + (8-1) = 1707$ clock cycles

Register Organization – Multiple Chains #2


Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

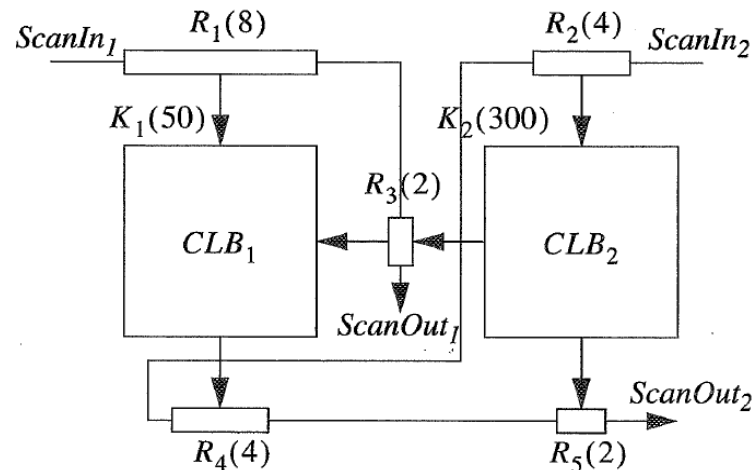

- Organization: overlapped test application and minimum-shift policy
 - TSes1: 50 vectors applied to CLB1 and CLB2
 - TSes2: 250 vectors applied to CLB2
 - $SC1(TSes1) = \max\{10, 2\} = 10$ and $SC2(TSes1) = \max\{4, 6\} = 6 \rightarrow SC(TSes1) = \max\{10, 6\} = 10$
 - $SC1(TSes2) = \max\{0, 2\} = 2$ and $SC2(TSes2) = \max\{4, 2\} = 4 \rightarrow SC(TSes2) = 4$
 - Hence, test application time for this order of registers
 - Time = $[50(10+1) + 250(4+1)] + (10-1) = 1809$ clock cycles

Register Organization – Multiple Chains #3

Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

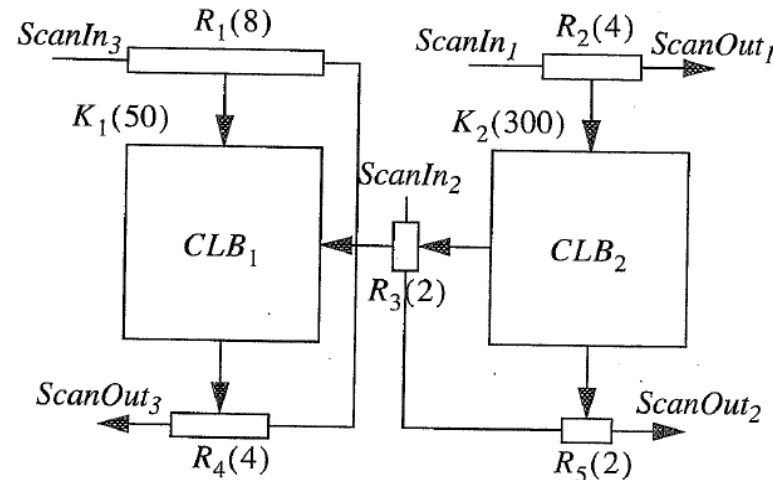

- Organization: overlapped test application and minimum-shift policy
 - TSes1: 50 vectors applied to CLB1 and CLB2
 - TSes2: 250 vectors applied to CLB2
 - $SC1(TSes1) = \max\{4, 0\} = 4$, $SC2(TSes1) = \max\{2, 4\} = 4$ and $SC3(TSes1) = \max\{8, 4\} = 8 \rightarrow SC(TSes1) = \max\{4, 4, 8\} = 8$
 - $SC1(TSes2) = \max\{4, 0\} = 4$, $SC2(TSes2) = \max\{0, 4\} = 4$ and $SC3(TSes2) = 0$ (NOT ACTIVE) $\rightarrow SC(TSes2) = \max\{4, 4, 0\} = 4$
 - Hence, test application time for this order of registers
 - Time = $[50(8+1) + 250(4+1)] + (8-1) = 1607$ clock cycles

Importance of Registers Positions

- The shift-cycle depends on the position of the registers in the chain
 - $SCin(TSesi)$: The distance from ScanIn of the farthest driver that is active is $TSesi$
 - $SCout(TSesi)$: The distance from ScanOut of the farthest receiver that is active is $TSesi$
 - $SCMS(TSesi) = \max\{SCin(TSesi), SCout(TSesi)\}$

Guidelines for Register Organization

- Some simple rules
 - Place drivers closer to ScanIn than receivers
 - Place drivers with higher driving weights closer to ScanIn than drivers with lower driving weights
 - Place receivers closer to ScanOut than drivers
 - Place receivers with higher receiving weights closer to ScanOut than receivers with lower receiving weights
- These are only guidelines and do not guarantee optimality.

Guidelines for Register Organization (cont.)

- Rules conflict if some registers are drivers as well as receivers
- Hence, in general, necessary to enumerate various orders of registers
- Complexity can be reduced by using interchange property
 - If any scan chain contains R_i closer to *ScanIn* than R_j , where $DRW_i \leq DRW_j$ **and** $RCW_i \geq RCW_j$, then interchange R_i and R_j , provided
 - R_i is adjacent to R_j in the chain, or
 - $LReg_i = LReg_j$


Special Cases

- Optimal ordering for special cases
 - No driver-receivers
 - Order drivers in decreasing weights, followed by receivers in increasing weights
 - All kernels require equal number of vectors
 - Pure drivers, followed by driver-receivers, followed by pure receivers
- For the general case, implicitly search all orders (utilize interchange property)

Guidelines for Multiple Scan Chains


- Organization of multiple scan chains
 - Under the flush policy
 - Order of registers within a chain does not matter
 - The shift-cycle for any session is equal to the length of the longest chain
 - Hence, partition registers into multiple chains
 - + Of equal lengths (if possible)
 - + Or, if above not possible, then in such a manner that the length of the longest chain is minimized
 - Under active flush methodology
 - Registers may be assigned in such a manner that one or more longer chains become inactive after the first few sessions

Example - Impact of Register Ordering

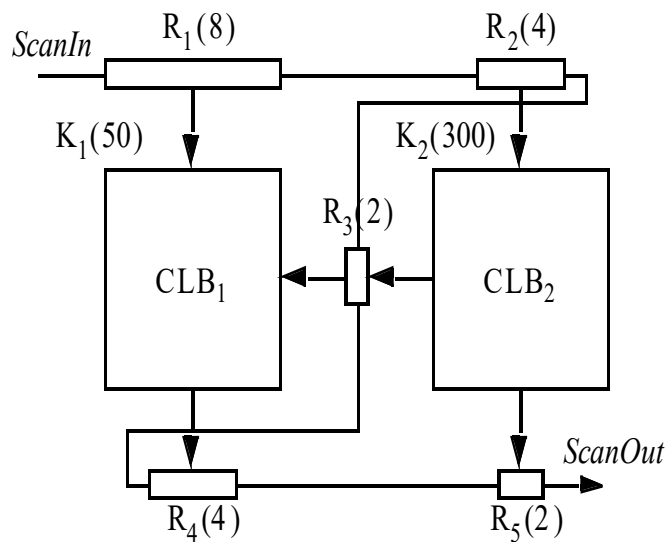

- Better Order
- Pure Drivers
 - DRW(R1)=50
 - DRW(R2)=300
 - Pure Receivers
 - RCW(R4)=50
 - RCW(R5)=300
 - Driver & Receiver
 - DRW(R3)=50
 - RCW(R3)=300


Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

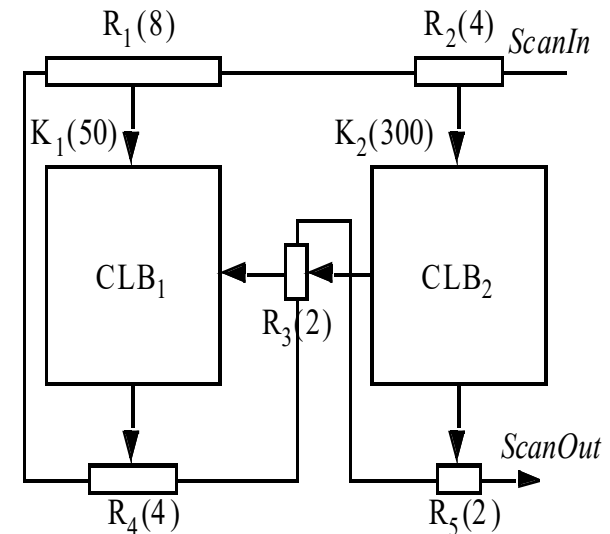


- Organization: overlapped test application and minimum-shift policy
 - In TSes1, 50 vectors applied to CLB1 and CLB2 (Kernels K1 and K2)
 - In TSes2, 250 vectors applied to CLB2 (Kernel K2)
 - $SC(TSes1) = \max\{14, 8\} = 14$ and $SC(TSes2) = \max\{12, 8\} = 12$
- Hence, test application time for this order of registers
 - Time = $[50(14 + 1) + 250(12 + 1)] + (14 - 1) = 4013$ clock cycles
- Organization: overlapped test application and minimum-shift policy
 - In TSes1, 50 vectors applied to CLB1 and CLB2
 - In TSes2, 250 vectors applied to CLB2
 - $SC(TSes1) = \max\{18, 8\} = 18$ and $SC(TSes2) = \max\{4, 4\} = 4$
- Hence, test application time for this order of registers
 - Time = $[50(18 + 1) + 250(4 + 1)] + (18 - 1) = 2217$ clock cycles

Reconfigurable Chain

Reg.	Bits	Type	DRW	RCW
R1	8	Dri	50	0
R2	4	Dri	300	0
R3	2	Dri/Rec	50	300
R4	4	Rec	0	50
R5	2	Rec	0	300

 

 - The chains can be reconfigured to bypass inactive registers
 - This chain minimizes the shift cycle for $TSes_1$



- R_4 is inactive in $TSes_2$ but prevents minimization of shift cycle in $TSes_2$
- This reconfigurable chain minimizes shift cycle for every session

