

---

# EEDG/CE 6303: Testing and Testable Design

*Mehrdad Nourani*

**Dept. of ECE  
Univ. of Texas at Dallas**

---

# Session 10


## **Built-In Self-Test (BIST)**

---

# **Various LFSR Architectures**

 
## Exhaustive-Pattern LFSR

- Binary counter can be used to generate all  $2^n$  patterns
- Example: 4-bit binary counter



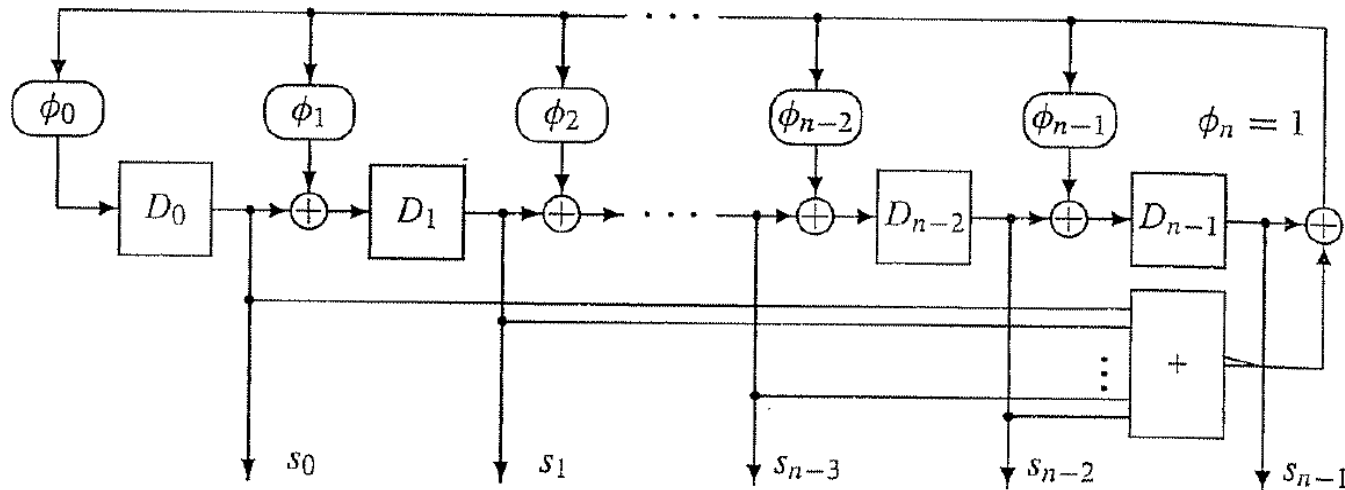
# Complete LFSR

- We can easily modify the LFSR to generate the complete sequence that includes all-zero pattern
  - When LFSR has 0...001, the output of NOR is 1 and the last XOR injects a 0. So, the next state will be all zero 0...000.
  - When LFSR has 0...000, the output of NOR is 1 again but the last XOR injects a 1. So, the next state will be out of all-zero state.



 
# Examples of Complete LFSR


- Further optimization would be possible by optimizing NOR and XOR gates together.




*(a) 4-stage standard CFSR*

 

*(b) 4-stage modular CFSR*

 

*(c) A minimized version of (a)*

 

*(d) A minimized version of (b)*

# Reverse-Order Sequence

- In some test scenarios, a pair of test sequences are required where one contains vectors in the reverse order of the other.
- The reverse-order sequence can be generated using polynomial:  $\varphi(x)=x^n \varphi(1/x)$
- Example: 5-stage internal XOR LFSR with
  - (a)  $\varphi(x)=x^5+x^2+1$
  - (b)  $\varphi(x)=x^5+x^3+1$

| (a)      |                     |   |   |   |   | (b)      |                     |   |   |   |   |
|----------|---------------------|---|---|---|---|----------|---------------------|---|---|---|---|
| $i$      | $i^{\text{th}}$ PTV |   |   |   |   | $i$      | $i^{\text{th}}$ PTV |   |   |   |   |
| 0        | 1                   | 0 | 0 | 0 | 0 | 0        | 1                   | 0 | 0 | 0 | 0 |
| 1        | 0                   | 1 | 0 | 0 | 0 | 1        | 0                   | 1 | 0 | 0 | 0 |
| 2        | 0                   | 0 | 1 | 0 | 0 | 2        | 0                   | 0 | 1 | 0 | 0 |
| 3        | 0                   | 0 | 0 | 1 | 0 | 3        | 0                   | 0 | 0 | 1 | 0 |
| 4        | 0                   | 0 | 0 | 0 | 1 | 4        | 0                   | 0 | 0 | 0 | 1 |
| 5        | 1                   | 0 | 1 | 0 | 0 | 5        | 1                   | 0 | 0 | 1 | 0 |
| 6        | 0                   | 1 | 0 | 1 | 0 | 6        | 0                   | 1 | 0 | 0 | 1 |
| 7        | 0                   | 0 | 1 | 0 | 1 | 7        | 1                   | 0 | 1 | 1 | 0 |
| 8        | 1                   | 0 | 1 | 1 | 0 | 8        | 0                   | 1 | 0 | 1 | 1 |
| 9        | 0                   | 1 | 0 | 1 | 1 | 9        | 1                   | 0 | 1 | 1 | 1 |
| 10       | 1                   | 0 | 0 | 0 | 1 | 10       | 1                   | 1 | 0 | 0 | 1 |
| 11       | 1                   | 1 | 1 | 0 | 0 | 11       | 1                   | 1 | 1 | 1 | 0 |
| 12       | 0                   | 1 | 1 | 1 | 0 | 12       | 0                   | 1 | 1 | 1 | 1 |
| 13       | 0                   | 0 | 1 | 1 | 1 | 13       | 1                   | 0 | 1 | 0 | 1 |
| 14       | 1                   | 0 | 1 | 1 | 1 | 14       | 1                   | 1 | 0 | 0 | 0 |
| 15       | 1                   | 1 | 1 | 1 | 1 | 15       | 0                   | 1 | 1 | 0 | 0 |
| 16       | 1                   | 1 | 0 | 1 | 1 | 16       | 0                   | 0 | 1 | 1 | 0 |
| 17       | 1                   | 1 | 0 | 0 | 1 | 17       | 0                   | 0 | 0 | 1 | 1 |
| 18       | 1                   | 1 | 0 | 0 | 0 | 18       | 1                   | 0 | 0 | 1 | 1 |
| 19       | 0                   | 1 | 1 | 0 | 0 | 19       | 1                   | 1 | 0 | 1 | 1 |
| 20       | 0                   | 0 | 1 | 1 | 0 | 20       | 1                   | 1 | 1 | 1 | 1 |
| 21       | 0                   | 0 | 0 | 1 | 1 | 21       | 1                   | 1 | 1 | 0 | 1 |
| 22       | 1                   | 0 | 1 | 0 | 1 | 22       | 1                   | 1 | 1 | 0 | 0 |
| 23       | 1                   | 1 | 1 | 1 | 0 | 23       | 0                   | 1 | 1 | 1 | 0 |
| 24       | 0                   | 1 | 1 | 1 | 1 | 24       | 0                   | 0 | 1 | 1 | 1 |
| 25       | 1                   | 0 | 0 | 1 | 1 | 25       | 1                   | 0 | 0 | 0 | 1 |
| 26       | 1                   | 1 | 1 | 0 | 1 | 26       | 1                   | 1 | 0 | 1 | 0 |
| 27       | 1                   | 1 | 0 | 1 | 0 | 27       | 0                   | 1 | 1 | 0 | 1 |
| 28       | 0                   | 1 | 1 | 0 | 1 | 28       | 1                   | 0 | 1 | 0 | 0 |
| 29       | 1                   | 0 | 0 | 1 | 0 | 29       | 0                   | 1 | 0 | 1 | 0 |
| 30       | 0                   | 1 | 0 | 0 | 1 | 30       | 0                   | 0 | 1 | 0 | 1 |
| $\vdots$ | $\vdots$            |   |   |   |   | $\vdots$ | $\vdots$            |   |   |   |   |

# Hybrid LFSR

---


- Polynomial  $f(x)=1+b(x)+c(x)$  is **fully decomposable** iff both  $b(x)$  and  $c(x)$  have no common terms and there exists an integer  $j$  such that  $c(x)=x^j b(x)$ ,  $j \geq 1$
- If  $f(x)$  is fully decomposable, then we have  $f(x)=1+b(x)+x^j b(x)$
- A hybrid (top-bottom) LFSR can be constructed using polynomial  $s(x)=1+\wedge x^j +x^j b(x)$ 
  - The term  $\wedge x^j$  indicates the XOR gate with one input is connected to the feedback path, not between stages


 
# 5-Stage Hybrid LFSRs


- Compared to a standard LFSR with  $m$  XOR, a hybrid LFSR can be realized using  $(m+1)/2$  XORs and can achieve full-length  $2^n-1$  cycle.
  - Details in: L. Wang and E. McCluskey, "Hybrid Design Generating Maximum-Length Sequences," Trans. CAD, 1988.
- (a) 5-stage top-bottom LFSR

**Internal XOR part:**  $s(x) = 1 + x^2 + x^4 + x^5$  for  $f(x) = 1 + x^2 + x^3 + x^4 + x^5$   
 $\phi(x) = 1 + x^4 + x^5$



 - (b) 5-stage bottom-top LFSR


**Internal XOR part:**  $s(x) = 1 + x^2 + x^4 + x^5$  for  $f(x) = 1 + x + x^2 + x^3 + x^5$   
 $\phi(x) = 1 + x^2 + x^5$


 
# Weighted Pseudo-Random Pattern

---

- Consider an AND gate with large fan-in:




- If  $p(1)$  at all PIs is 0.5,  $p_F(1) = 0.5^8 = 1/256$   
and  $p_F(0) = 1 - (1/256) = 255/256$
- Will need enormous # of random patterns to test a stuck-at 0 fault on  $F$ -- LFSR  $p(1) = 0.5$ 
  - We must not use an ordinary LFSR to test this
- IBM — holds patents on weighted pseudo-random pattern generator in ATE

# Weighted LFSR

---

- For a regular LFSR  $p(1) = 0.5$
- Solution to get a weighted LFSR
  - Add programmable weight selection and complement LFSR bits to get  $p(1)$ 's other than 0.5
- Need 2-3 weight sets for a typical circuit
- Weighted pattern generator drastically shortens pattern length for pseudo-random patterns

# Weighted Pattern Generator

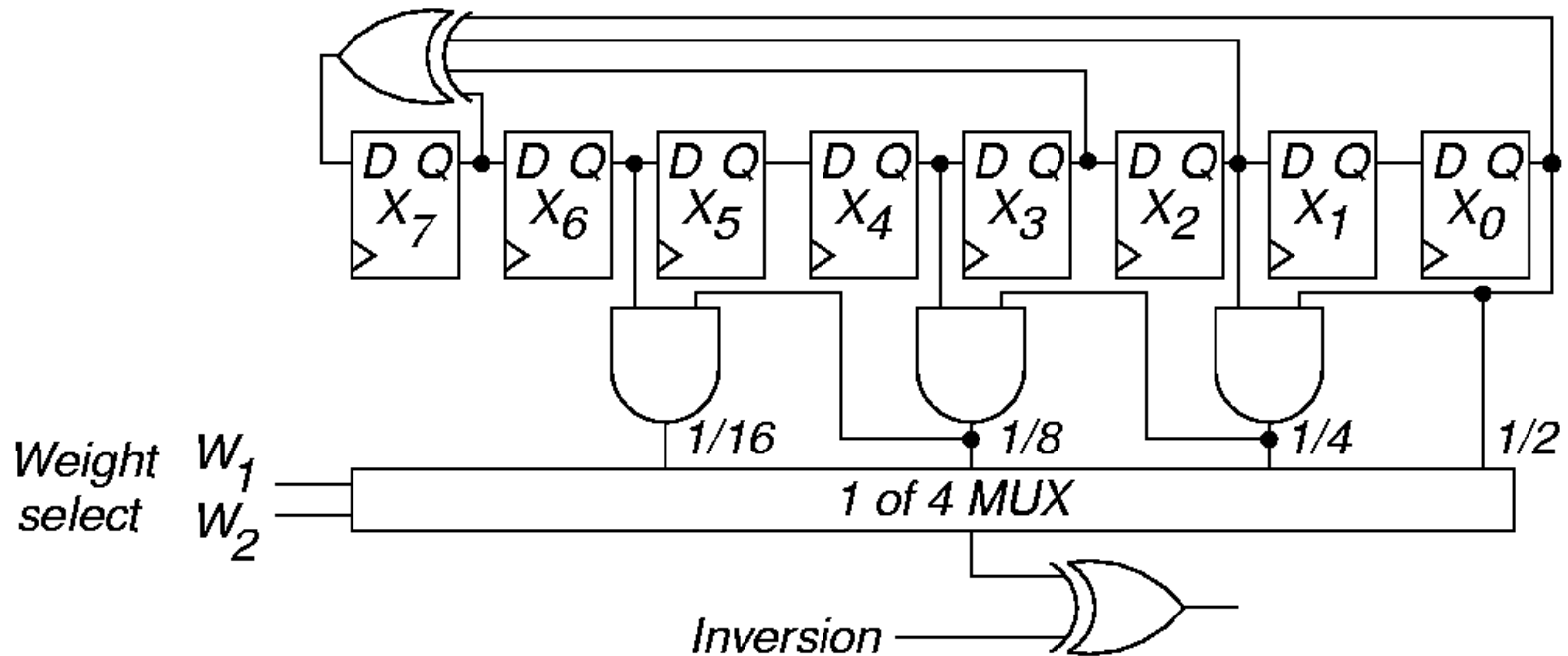

| $w_1$ | $w_2$ | $Inv.$ | $p$ (output) | $w_1$ | $w_2$ | $Inv$ | $p$ (output) |
|-------|-------|--------|--------------|-------|-------|-------|--------------|
| 0     | 0     | 0      | 1/2          | 1     | 0     | 0     | 1/8          |
| 0     | 0     | 1      | 1/2          | 1     | 0     | 1     | 7/8          |
| 0     | 1     | 0      | 1/4          | 1     | 1     | 0     | 1/16         |
| 0     | 1     | 1      | 3/4          | 1     | 1     | 1     | 15/16        |

---

# **Response Compaction**

# Motivation for Test Data Compaction

---

- Huge amount of data in CUT response to LFSR patterns – example:
  - Generate 5 million random patterns
  - CUT has 200 outputs
  - Leads to:  $5 \text{ million} \times 200 = 1 \text{ billion bits response}$
- Uneconomical to store and check all of these responses on chip
- Responses must be compacted

# Definitions

---

- ***Aliasing*** – Due to information loss, signatures of good and some bad machines match
- ***Compaction*** – Drastically reduce # bits in original circuit response – **information is lost**
- ***Compression*** – Reduce # bits in original circuit response – **no information loss** – fully invertible (can get back original response)
- ***Signature analysis*** – Compact good machine response into *good machine signature*. Actual signature generated during testing, and compared with good machine signature
- ***Transition Count Response Compaction*** – Count # transitions from  $0 \rightarrow 1$  and  $1 \rightarrow 0$  as a signature

# **Response Analysis Mechanisms**


---

- Ones count testing
- Transition count testing
- LFSR-based signature compaction/analysis
  - Serial
  - parallel



 
# Ones Counting


- Ones count testing will need a counter to count the number of 1s in the bit stream.
- Assume the CUT has one output and the output contains a stream of  $L$  bits. Let the fault-free output response be  $\{r_0, r_1, \dots, r_{L-1}\}$ .
- Aliasing probability [Savir 1985] for  $L$  bit stream when the fault-free response should have  $m$  1s
  - $P_{OC}(m) = [C(L, m) - 1] / (2^L - 1)$



# Transition Counting

 

 
(a) Logic simulation of good machine and fault a stuck-at-1.



(b) Transition counts of good and failing machines.
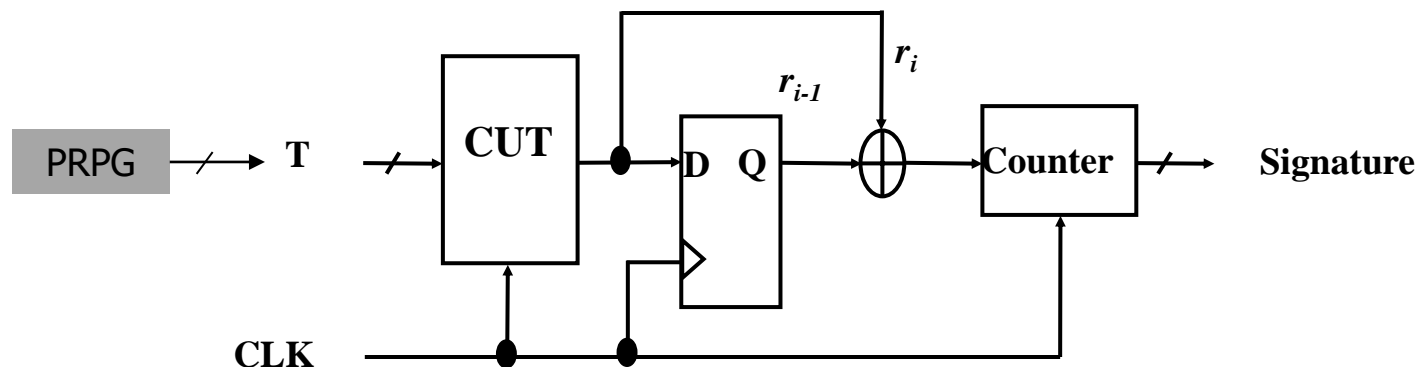
# Transition Counting Details

- Transition count when L bit test sequence is applied to CUT:  $C(R) = \sum_{i=1 \text{ to } L-1} (r_i \oplus r_{i-1})$
- To maximize fault coverage:
  - Make  $C(R_{\text{fault-free}})$  – good machine transition count – as large or as small as possible
- Aliasing probability [Hays 1976] for L bit stream when the fault-free response should have m transitions
  - $P_{\text{TC}}(m) = [2C(L-1, m) - 1] / (2^L - 1)$



# Problems with OC and TC Methods

---

- The aliasing probability in both OC and TC methods depends on the fault-free response
- The aliasing probability is minimum (or maximum) when the fault-free response is in its minimum (or maximum) value of its respective parameter
  - $P_{TC}$  is maximum when #of transitions  $m \approx L/2$
  - $P_{TC}$  is minimum when #of transitions  $m = 0$  or  $L-1$

# **LFSR for Response Compaction**

---


- Use *cyclic redundancy check code* (CRCC) generator (LFSR) for response compacter
- Treat data bits from circuit POs to be compacted as a decreasing order coefficient polynomial
- CRCC divides the PO polynomial by its characteristic polynomial
  - Leaves remainder of division in LFSR
  - Must initialize LFSR to *seed value* (usually 0) before testing
- After testing – compare signature in LFSR to known good machine signature
- Critical: Must compute good machine signature

---

# **Serial LFSR Compaction**

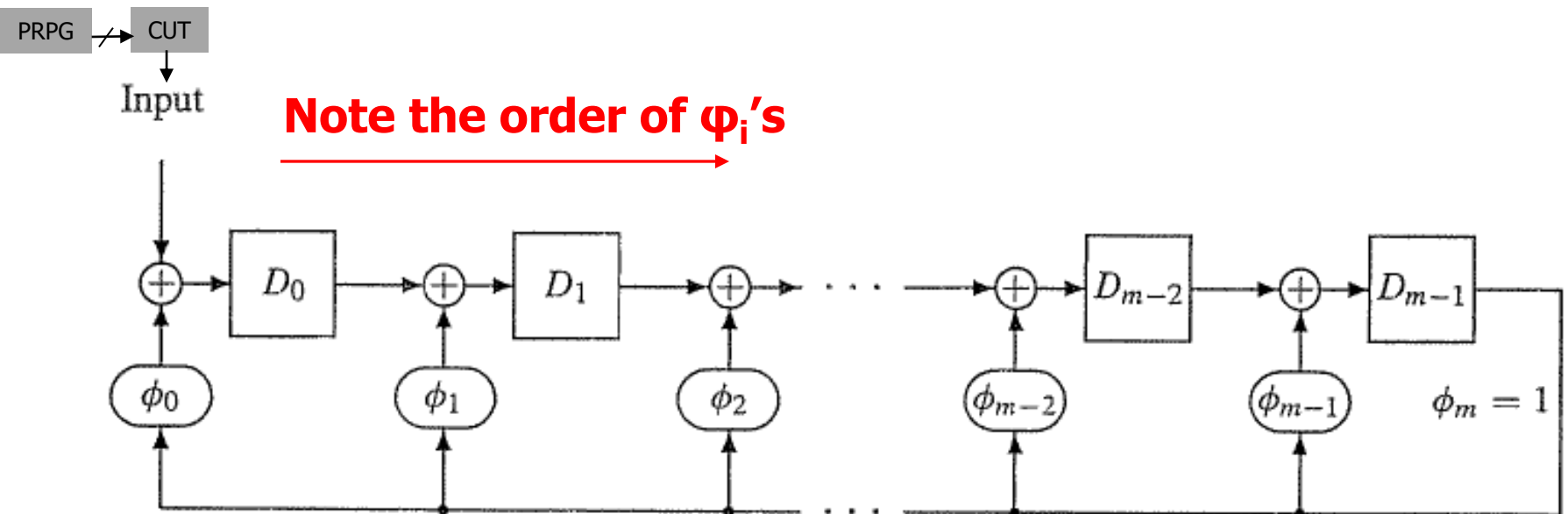
# Serial LFSR Compactor

- The polynomial  $\phi(x) = \phi_m x^m + \dots + \phi_1 x + \phi_0$
- The polynomial relationship
  - L-bit sequence coming to compactor:  $m_0 m_1 m_2 \dots m_{L-1}$  ( $m_{L-1}$  is the first bit arriving at compactor)
  - The input polynomial:  $M(x) = m_0 + m_1 x + m_2 x^2 + \dots + m_{L-1} x^{L-1}$
  - $M(x) = q(x) \phi(x) + r(x)$  where  $r(x)$  the polynomial remainder of  $M(x)/\phi(x)$  will be the final compactor's response


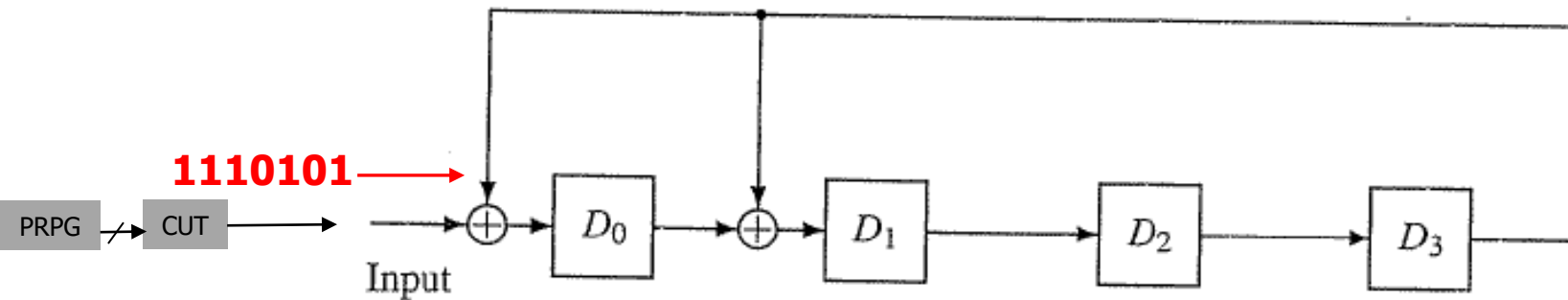
# LFSR Compactor Example I

- The polynomial:  $\phi(x) = x^4 + x + 1$
- The sequence: 1110101 that is  $M(x) = 1 + x + x^2 + x^4 + x^6$
- Initial state: 0000



## Polynomial Division Method

$$\begin{array}{r}
 x^4 + x + 1 \overline{) x^6 + x^4 + x^3 + x^2 + x + 1} \\
 \underline{x^6 +} \phantom{x^4 +} \phantom{x^3 +} \phantom{x^2 +} \phantom{x +} \phantom{1} \\
 \phantom{x^6 +} x^4 + \phantom{x^3 +} \phantom{x^2 +} \phantom{x +} \phantom{1} \\
 \underline{\phantom{x^6 +} x^4 +} \phantom{x^3 +} \phantom{x^2 +} \phantom{x +} \phantom{1} \\
 \phantom{x^6 +} \phantom{x^4 +} x^3 + \phantom{x^2 +} \phantom{x +} \phantom{1} \\
 \phantom{x^6 +} \phantom{x^4 +} \underline{x^3 +} \phantom{x^2 +} \phantom{x +} \phantom{1} \\
 \phantom{x^6 +} \phantom{x^4 +} \phantom{x^3 +} x^2 + \phantom{x +} \phantom{1} \\
 \phantom{x^6 +} \phantom{x^4 +} \phantom{x^3 +} \underline{x^2 +} \phantom{x +} \phantom{1} \\
 \phantom{x^6 +} \phantom{x^4 +} \phantom{x^3 +} \phantom{x^2 +} x + 1 \\
 \phantom{x^6 +} \phantom{x^4 +} \phantom{x^3 +} \phantom{x^2 +} \underline{x +} 1 \\
 \phantom{x^6 +} \phantom{x^4 +} \phantom{x^3 +} \phantom{x^2 +} \phantom{x +} 0 \\
 \text{Signature} \rightarrow \boxed{x^3}
 \end{array}$$

← Quotient:  $x^2 + 1$


**Final signature (remainder):**  
 $D_0 D_1 D_2 D_3 = 0001$

## Tabular Method

| Time | Input     | LFSR state |   |   |   |
|------|-----------|------------|---|---|---|
| -    | -         | 0          | 0 | 0 | 0 |
| 0    | $r_1 = 1$ | 1          | 0 | 0 | 0 |
| 1    | $r_2 = 0$ | 0          | 1 | 0 | 0 |
| 2    | $r_3 = 1$ | 1          | 0 | 1 | 0 |
| 3    | $r_4 = 0$ | 0          | 1 | 0 | 1 |
| 4    | $r_5 = 1$ | 0          | 1 | 1 | 0 |
| 5    | $r_6 = 1$ | 1          | 0 | 1 | 1 |
| 6    | $r_7 = 1$ | 0          | 0 | 0 | 1 |



# LFSR Compactor Example I (cont.)

 

| Fault Free Sequence | $M$ | $r_0$ | $r_1$ | $r_2$ | $r_3$ | Faulty Sequence | $M'$ | $r_0$ | $r_1$ | $r_2$ | $r_3$ | Faulty Sequence  | $M''$ | $r_0$ | $r_1$ | $r_2$ | $r_3$ |   |                    |
|---------------------|-----|-------|-------|-------|-------|-----------------|------|-------|-------|-------|-------|------------------|-------|-------|-------|-------|-------|---|--------------------|
|                     | 1   | 0     | 0     | 0     | 0     |                 | 1    | 0     | 0     | 0     | 0     |                  | 1     | 0     | 0     | 0     | 0     |   |                    |
|                     | 1   | 1     | 0     | 0     | 0     |                 | 1    | 1     | 0     | 0     | 0     |                  | 0     | 1     | 0     | 0     | 0     |   |                    |
|                     | 0   | 1     | 1     | 0     | 0     |                 | 0    | 1     | 1     | 0     | 0     |                  | 1     | 0     | 1     | 0     | 0     |   |                    |
|                     | 1   | 0     | 1     | 1     | 0     |                 | 1    | 0     | 1     | 1     | 0     |                  | 1     | 1     | 0     | 1     | 0     |   |                    |
|                     | 1   | 1     | 0     | 1     | 1     |                 | 0    | 1     | 0     | 1     | 1     |                  | 0     | 1     | 1     | 0     | 1     |   |                    |
|                     | 0   | 0     | 0     | 0     | 1     |                 | 0    | 1     | 0     | 0     | 1     |                  | 0     | 1     | 0     | 1     | 0     |   |                    |
|                     | 0   | 1     | 1     | 0     | 0     |                 | 1    | 1     | 0     | 0     | 0     |                  | 1     | 0     | 1     | 0     | 1     |   |                    |
|                     | 1   | 0     | 1     | 1     | 0     |                 | 1    | 1     | 1     | 0     | 0     |                  | 1     | 0     | 1     | 1     | 0     |   |                    |
| $R$                 |     | 1     | 0     | 1     | 1     | $R'$            |      | 1     | 1     | 1     | 0     | Will be detected | $R''$ |       | 1     | 0     | 1     | 1 | Cannot be detected |


(a) Fault-free signature

(b) Signature for fault  $f_1$

(c) Signature for fault  $f_2$
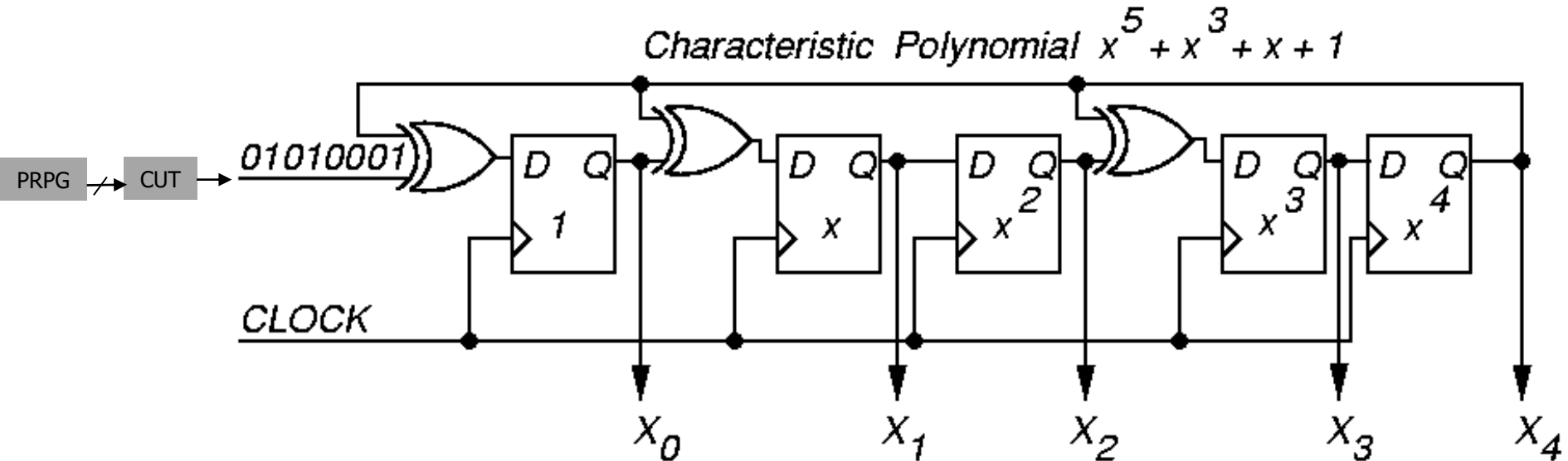
# LFSR Compactor Example II

- LFSR seed value is "00000"
- Input sequence: 0 1 0 1 0 0 0 1
- Symbolic polynomial:  $0x^0 + 1x^1 + 0x^2 + 1x^3 + 0x^4 + 0x^5 + 0x^6 + 1x^7$
- Logic simulation: *Remainder* =  $1 + x^2 + x^3$  (i.e. 10110)



# LFSR Compactor Example II (cont.)

$$\begin{array}{r}
 x^5 + x^3 + x + 1 \quad \left| \begin{array}{l}
 \overline{x^2 + 1} \\
 x^7 \phantom{+ x^5} + x^3 \phantom{+ x^2} + x \\
 \hline
 x^7 + x^5 + x^3 + x^2 \\
 \hline
 \phantom{x^7} x^5 \phantom{+ x^3} + x^2 + x \\
 \hline
 \phantom{x^7} x^5 + x^3 \phantom{+ x^2} + x + 1 \\
 \hline
 \phantom{x^7} \phantom{x^5} x^3 + x^2 + 1
 \end{array} \right.
 \end{array}$$


*remainder* →

| Inputs               |               | $x^0$ | $x^1$ | $x^2$ | $x^3$ | $x^4$ |
|----------------------|---------------|-------|-------|-------|-------|-------|
| Logic<br>Simulation: | Initial State | 0     | 0     | 0     | 0     | 0     |
|                      | 1             | 1     | 0     | 0     | 0     | 0     |
|                      | 0             | 0     | 1     | 0     | 0     | 0     |
|                      | 0             | 0     | 0     | 1     | 0     | 0     |
|                      | 0             | 0     | 0     | 0     | 1     | 0     |
|                      | 1             | 1     | 0     | 0     | 0     | 1     |
|                      | 0             | 1     | 0     | 0     | 1     | 0     |
|                      | 1             | 1     | 1     | 0     | 0     | 1     |
|                      | 0             | 1     | 0     | 1     | 1     | 0     |

Logic simulation: *Remainder* =  $1 + x^2 + x^3$
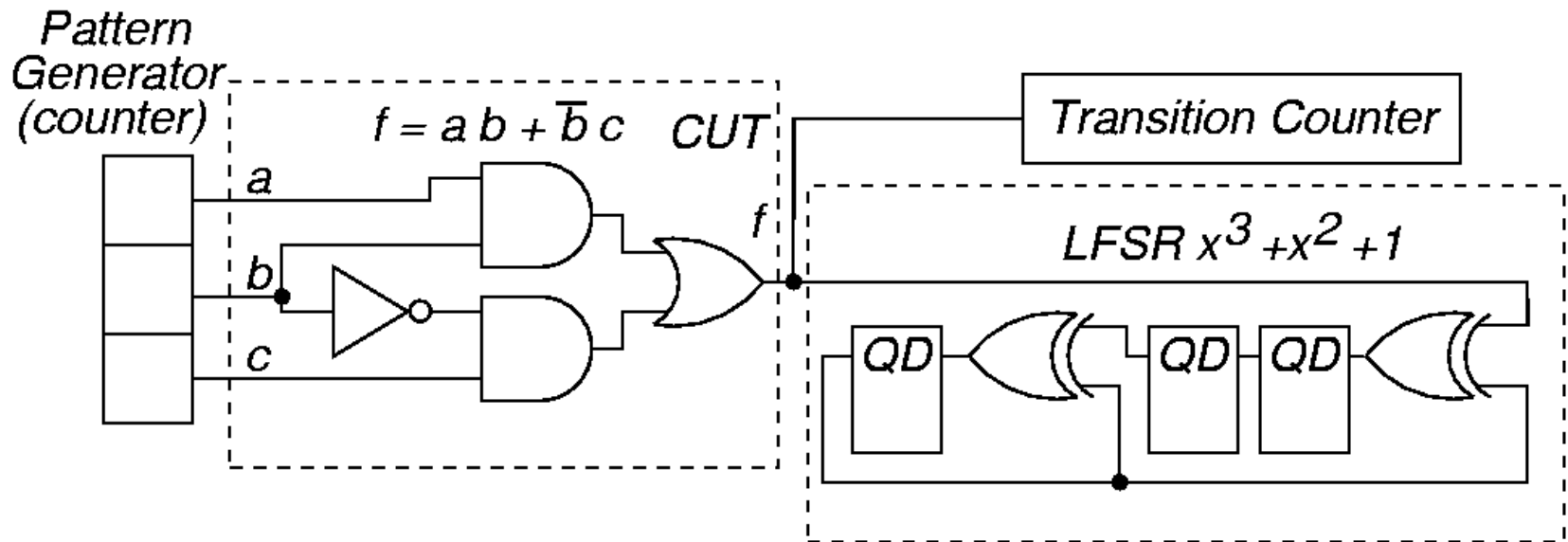
# **LFSR Compactor Example III**

- Suppose we use a 3-bit exhaustive binary counter for pattern generator.
- Faults may be masked here too.



# LFSR Compactor Example III (cont.)

- LFSR aliases for *f*sa1, transition counter for *a*sa1

| <i>Pattern</i>    | <i>Responses</i> |              |              |              |
|-------------------|------------------|--------------|--------------|--------------|
| <i>abc</i>        | <i>Good</i>      | <i>a</i> sa1 | <i>f</i> sa1 | <i>b</i> sa1 |
| 000               | 0                | 0            | 1            | 0            |
| 001               | 1                | 1            | 1            | 0            |
| 010               | 0                | 1            | 1            | 0            |
| 011               | 0                | 1            | 1            | 0            |
| 100               | 0                | 0            | 1            | 1            |
| 101               | 1                | 1            | 1            | 1            |
| 110               | 1                | 1            | 1            | 1            |
| 111               | 1                | 1            | 1            | 1            |
| <i>Signatures</i> |                  |              |              |              |
| Transition Count  | 3                | 3            | 0            | 1            |
| LFSR              | 001              | 101          | 001          | 010          |

# Probability of Aliasing

---

- Consider polynomial operations (equivalent to mod 2 where multiplication and addition are the same as AND and XOR).
  - Fault-free circuit response:  $M^*(x) = q^*(x) \varphi(x) + r^*(x)$
  - Faulty circuit response:  $M(x) = q(x) \varphi(x) + r(x)$
- Aliasing occurs when  $r^*(x) = r(x)$  while  $M^*(x) \neq M(x)$ 
  - $M^*(x) + M(x) = [q^*(x) + q(x)] \varphi(x) + (r^*(x) + r(x))$   
 $= [q^*(x) + q(x)] \varphi(x)$
  - Aliasing occurs when the error polynomial  $E(x) = M^*(x) + M(x)$  (i.e. a bit-by-bit XOR of fault-free and faulty responses) is divisible by the LFSR feedback polynomial  $\varphi(x)$ .
  - Aliasing is independent of the exact value of fault-free response.

## Probability of Aliasing (cont.)

---

- The maximum degree of  $E(x)=M^*(x)+M(x)$  is  $L-1$  (when  $L$  bit input streams is compacted).
- The maximum degree of  $\varphi(x)$  is  $m$
- So, the maximum degree of  $[q^*(x)+q(x)]$  will be  $L-1-m$ .
- For a given feedback polynomial  $\varphi(x)$ , any polynomial of degree  $\leq L-1-m$  can be used to obtain a fault-free signature.
- There exist  $2^{L-m}$  polynomials of degree  $\leq L-1-m$ . If we remove all-zero polynomial, total of  $2^{L-m}-1$  cases can cause aliasing.
  - $P_{\text{serial}}(m)=[2^{(L-m)}-1]/(2^L-1) \approx 2^{-m}$

---

## **Parallel LFSR Compaction (MISR)**




# **Multiple-Input Signature Register (MISR)**

---


- Problem with ordinary LFSR response compacter:
  - Too much hardware if one of these is put on each *primary output* (PO)
- Solution: MISR – compacts all outputs into one LFSR
  - Works because LFSR is linear – obeys *superposition principle*
  - Superimpose all responses in one LFSR – final remainder is XOR sum of remainders of polynomial divisions of each PO by the characteristic polynomial
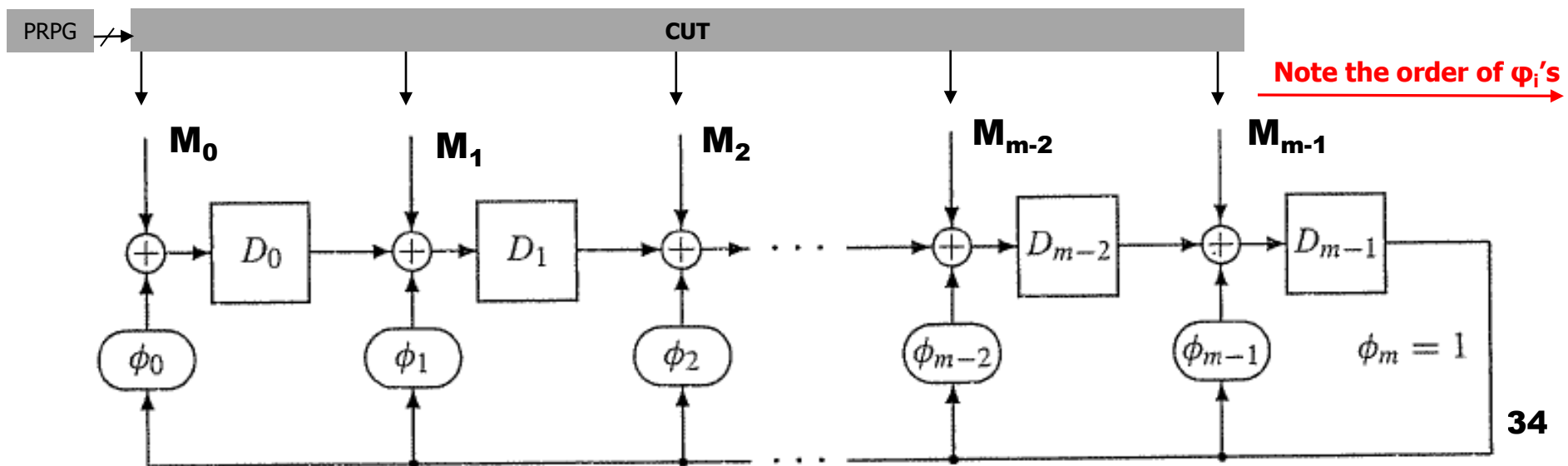
# MISR Structure

- The polynomial  $\phi(x) = \phi_m x^m + \dots + \phi_1 x + \phi_0$
- The polynomial relationship
  - Up to m number of L-bit sequences coming to each input of MISR
  - The effective input polynomial will be a combination of all input polynomials:  $M(x) = M_0(x) + x M_1(x) + x^2 M_2(x) + \dots + x^{m-1} M_{m-1}(x)$
  - $M(x) = q(x) * \phi(x) + r(x)$  where  $r(x)$  the polynomial remainder of  $M(x)/\phi(x)$  will be the final compactor's response



# A 4-Stage MISR Example

 

|       |   |   |   |   |   |   |   |   |
|-------|---|---|---|---|---|---|---|---|
| $M_0$ | 1 | 0 | 0 | 1 | 0 |   |   |   |
| $M_1$ |   | 0 | 1 | 0 | 1 | 0 |   |   |
| $M_2$ |   |   | 1 | 1 | 0 | 0 | 0 |   |
| $M_3$ |   |   |   | 1 | 0 | 0 | 1 | 1 |
| $M$   | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |


First word coming in

First word coming in

- The equivalent sequence will be:  
 $1x^0 + 0x^1 + 0x^2 + 1x^3 + 1x^4 + 0x^5 + 1x^6 + 1x^7$
- The aliasing probability when n out of m inputs are used

$$-P_{\text{MISR}}(m) = [2^{(nL-m)} - 1] / (2^{nL} - 1) \approx 2^{-m}$$

# MISR Division Example

 

$$\begin{array}{r}
 x^3 + x^2 \\
 \hline
 x^4 + x + 1 \left[ \begin{array}{r}
 x^7 + x^6 \quad + x^4 + x^3 \quad + x^0 \\
 x^7 \quad + x^4 + x^3 \\
 \hline
 x^6 \quad + x^0 \\
 x^6 \quad + x^3 + x^2 \\
 \hline
 x^3 + x^2 \quad + x^0
 \end{array} \right.
 \end{array}$$

Remainder = Signature =  $X^0 X^1 X^2 X^3 = 1011$

# MISR Matrix Equation


- The polynomial:  $\phi(x) = x^4 + x + 1$
- $M_i(t)$ : Input streams of MISR at time  $t$
- The transition matrix/relation:

Internal  
XOR  
Transition  
Matrix (A)

$$\begin{pmatrix} 0 & 0 & 0 & \dots & 0 & \phi_0 \\ 1 & 0 & 0 & \dots & 0 & \phi_1 \\ 0 & 1 & 0 & \dots & 0 & \phi_2 \\ 0 & 0 & 1 & \dots & 0 & \phi_3 \\ \vdots & \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & 1 & \phi_{n-1} \end{pmatrix}$$

$$\begin{bmatrix} s_0(t+1) \\ s_1(t+1) \\ s_2(t+1) \\ s_3(t+1) \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} s_0(t) \\ s_1(t) \\ s_2(t) \\ s_3(t) \end{bmatrix} + \begin{bmatrix} M_0(t) \\ M_1(t) \\ M_2(t) \\ M_3(t) \end{bmatrix}$$

 - Example (note that  $*$  is AND and  $+$  is XOR)



$$A \cdot \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix}$$

$$A \cdot \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} + \begin{bmatrix} 1 \\ 1 \\ 0 \\ 1 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix}$$

$$A \cdot \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ 0 \\ 0 \end{bmatrix}$$


$$A \cdot \begin{bmatrix} 1 \\ 1 \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ 1 \\ 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$A \cdot \begin{bmatrix} 0 \\ 0 \\ 0 \\ 1 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \\ 1 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 1 \\ 1 \end{bmatrix}$$

Data  
Stream

| $M_0$ | $M_1$ | $M_2$ | $M_3$ |
|-------|-------|-------|-------|
| 0     | 0     | 0     | 1     |
| 1     | 1     | 0     | 1     |
| 0     | 0     | 0     | 0     |
| 0     | 1     | 1     | 0     |
| 1     | 0     | 1     | 1     |

# Another MISR Example

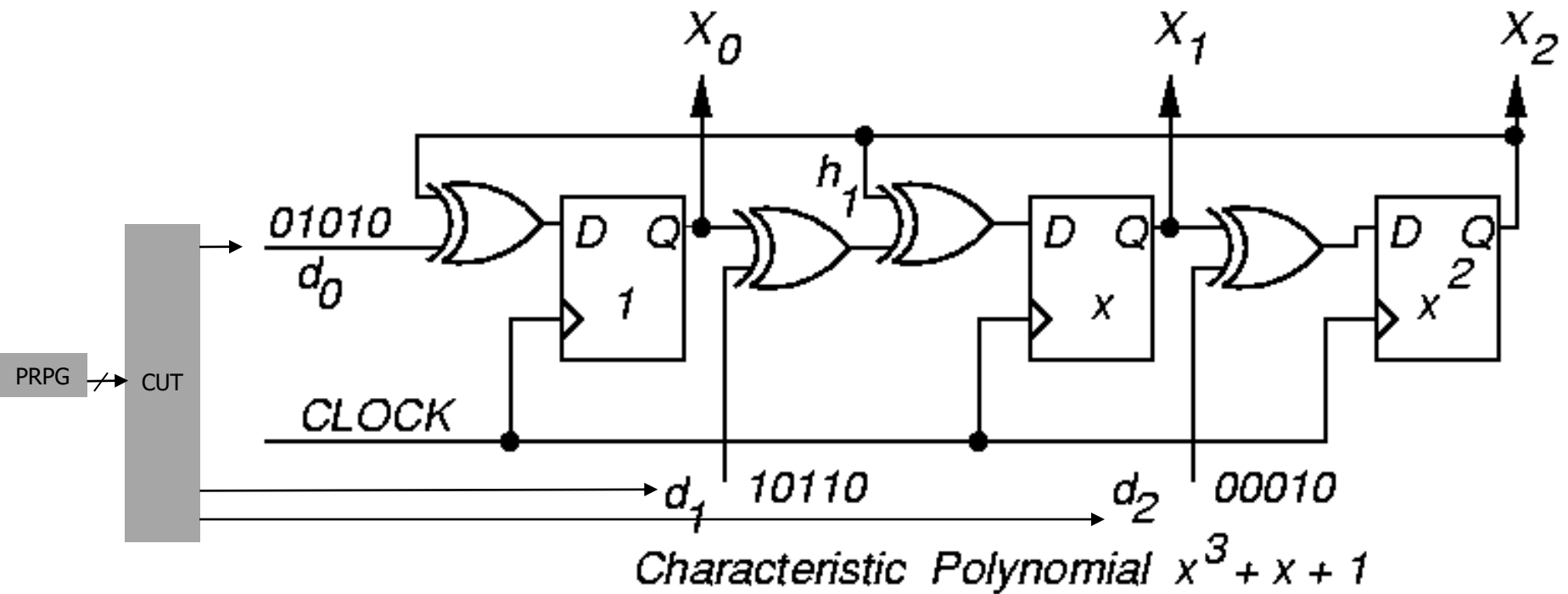

$$\begin{bmatrix} s_0(t+1) \\ s_1(t+1) \\ s_2(t+1) \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 1 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} s_0(t) \\ s_1(t) \\ s_2(t) \end{bmatrix} + \begin{bmatrix} M_0(t) \\ M_1(t) \\ M_2(t) \end{bmatrix}$$

# Multiple Signature Checking

---

- Use 2 different testing sessions:
  - 1<sup>st</sup> with MISR with polynomial  $\phi_1(x)$
  - 2<sup>nd</sup> with MISR with different polynomial  $\phi_2(x)$
- Reduces probability of aliasing –
  - Very unlikely that both polynomials will alias for the same fault
- Low hardware cost:
  - A few XOR gates for the 2<sup>nd</sup> MISR polynomial
  - A 2-1 MUX to select between two feedback polynomials